

Design of a Wide Dynamic Range Active Pixel Sensor using Self-Reset Technique

Kai Lutz

November 2009

*Project for the HEIS Lecture
of Prof. Dr.-Ing. Andreas König*



Overview

I. Introduction

1. *Motivation*
2. *Dynamic Range*
3. *Goals*

II. Parts of the Project

1. *Self-Reset Technique*
2. *The Comparator*
3. *Counter using toggle-FF's*
4. *4T DRAM Memory*
5. *Layout*
6. *Simulation Results*

III. Conclusion and Future Work

IV. Bibliography



1.Motivation

- Market for solid-state image sensors is rapidly growing.
- CCD vs. CMOS(PPS,APS or DPS).
- CMOS advantage: Integrating of sensing, analog and digital processing directly on the pixel.
 - Manufacturing with existing technology.
 - Less expensive.
 - Non-destructive readout (APS,DPS).
 - Following the CMOS scaling trend.
- Applications:
 - Consumer electronics (Digicams/Mobile Phones).
 - Machine vision.
 - Biological testing.
 - ...etc.



2. Dynamic Range

- Relation of brightest to darkest picture areas.
 - Typical CMOS image sensors Dynamic Range $\approx 60\text{dB}$.
 - Full range of real world's illumination $\approx 100\text{dB}$.
- ⇒ More or less specifics will be lost.
- ⇒ Sensor with higher DR will produce higher quality pictures.



3.Goals

- Compare different techniques to increase DR and SNR of an Active Pixel Sensors.
→ DR synonymous to sensor quality.
- Choose the one that is most promising and functional.
- Implement the technique on a pixel cell in 0.35 μ m tech.
- Consider possibilities to reduce error-proneness (FPN etc.)
- Discuss the results.



2. Dynamic Range

How to increase the DR?

Techniques to increase DR at the high end [1][2]


=> increasing i_{\max} or Q_{\max} .

1. Varying integration time:

- Shuttering.
- Well-capacity Adjusting (spiking).
- Time to saturation.
- Multiple-capture.

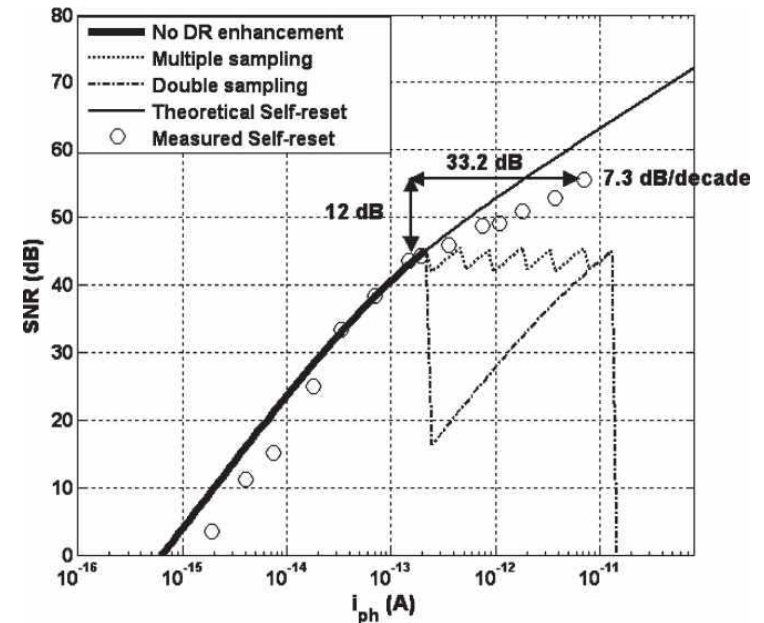2. Recycling the well using self-resetting:

- Time discrete or continuous monitoring.
- Synchronous or asynchronous reset.
- Will also increase peak SNR performance (high end).





$$DR = \frac{i_{\max}}{i_{\min}} \approx \frac{Q_{\max}}{\sigma_{\text{readout}}}$$

$$SNR_{\text{peak}} = \frac{Q_{\max}}{q}$$

 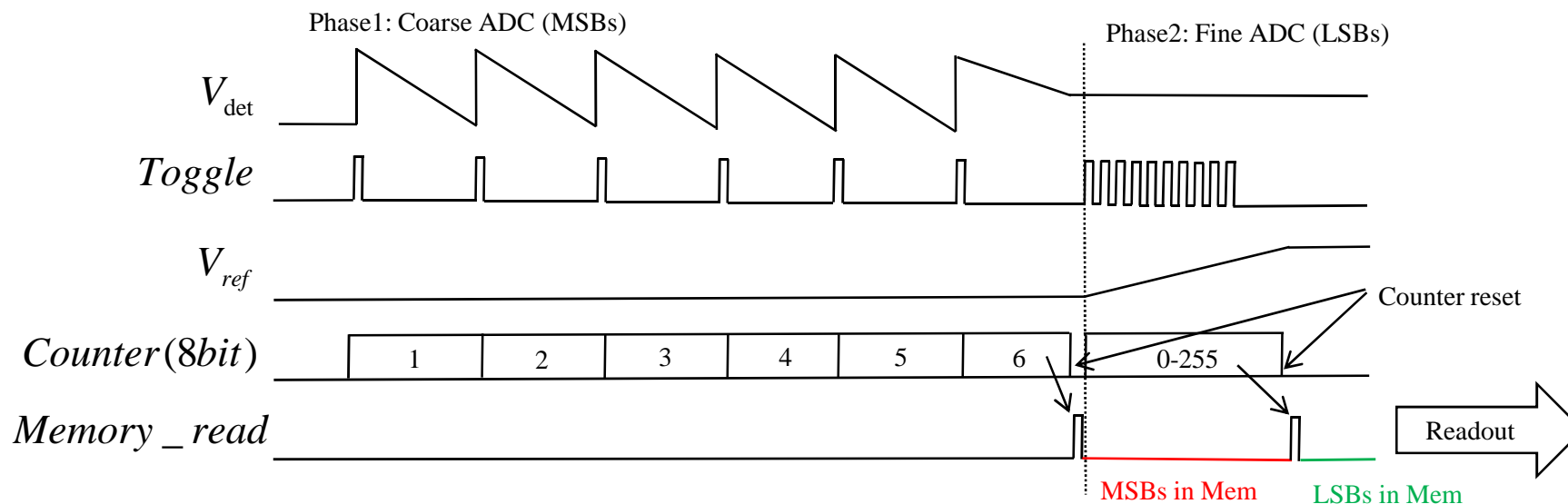
1. Self-Reset Technique

- Idea of self-reset pixel presented by Rhee and Joo[4][5].
- 2 Phases: Fine and coarse A/D conversion (counter and single slope ADC).
- Asynchronous well reset (increase effective well capacitance) .
- 8 bit DRAM to store MSBs for readout during phase 2.
- Pixel parallel ADC.




1. Self-Reset Technique

Circuit design

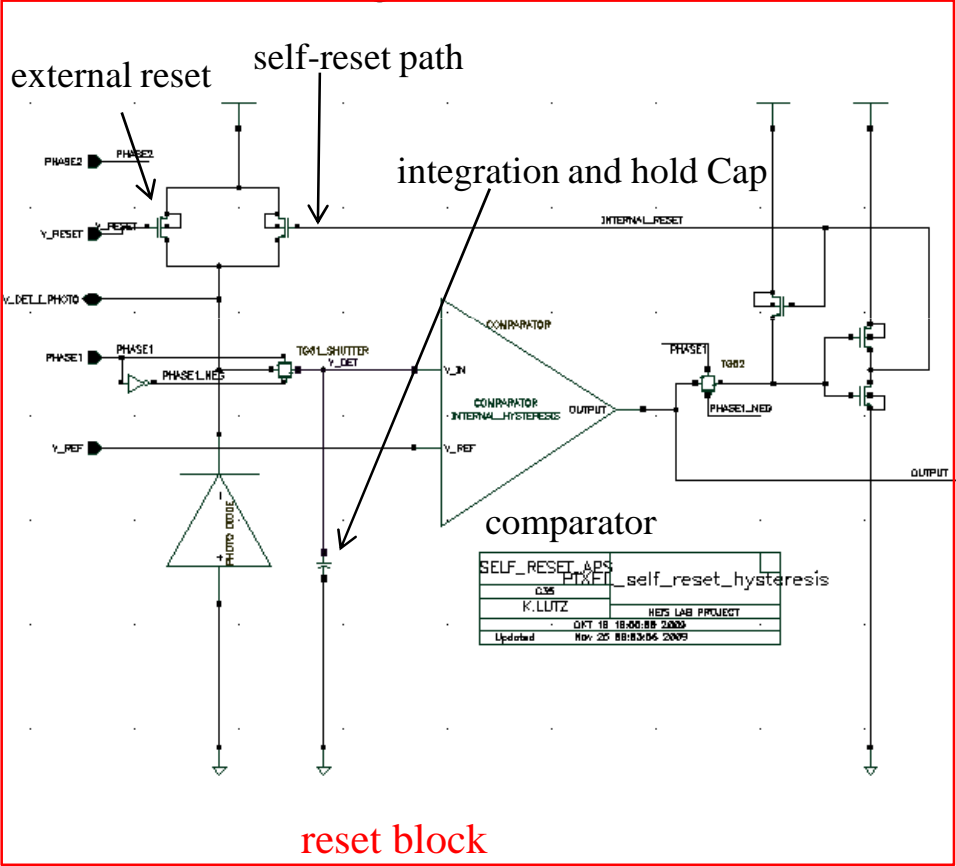

reset block

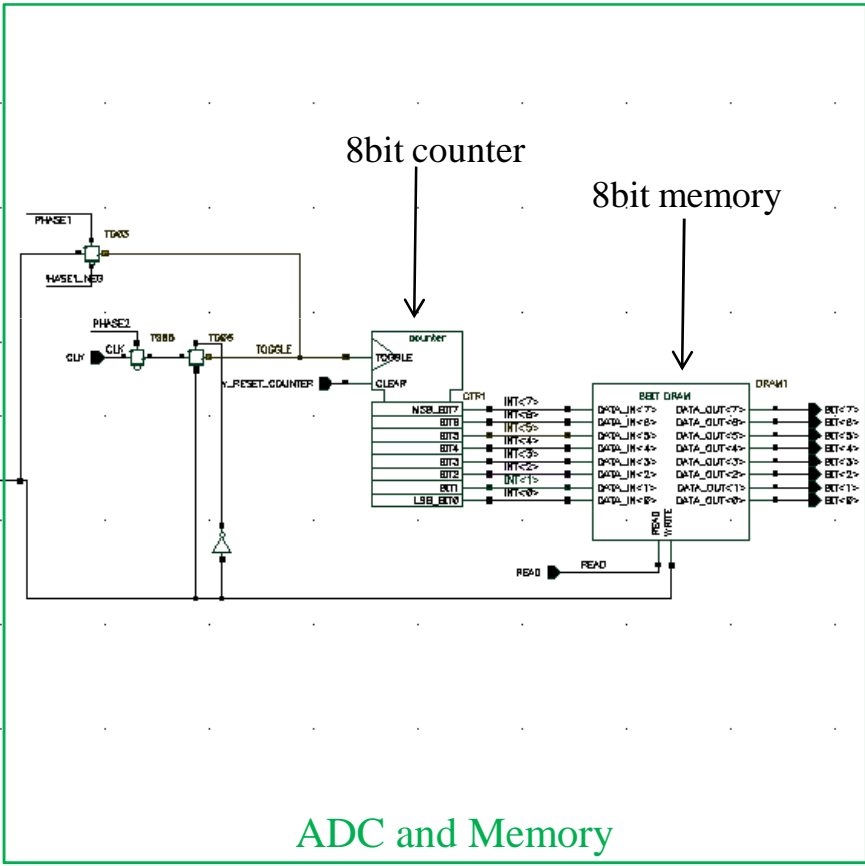


ADC and Memory



1. Self-Reset Technique

Phase 1

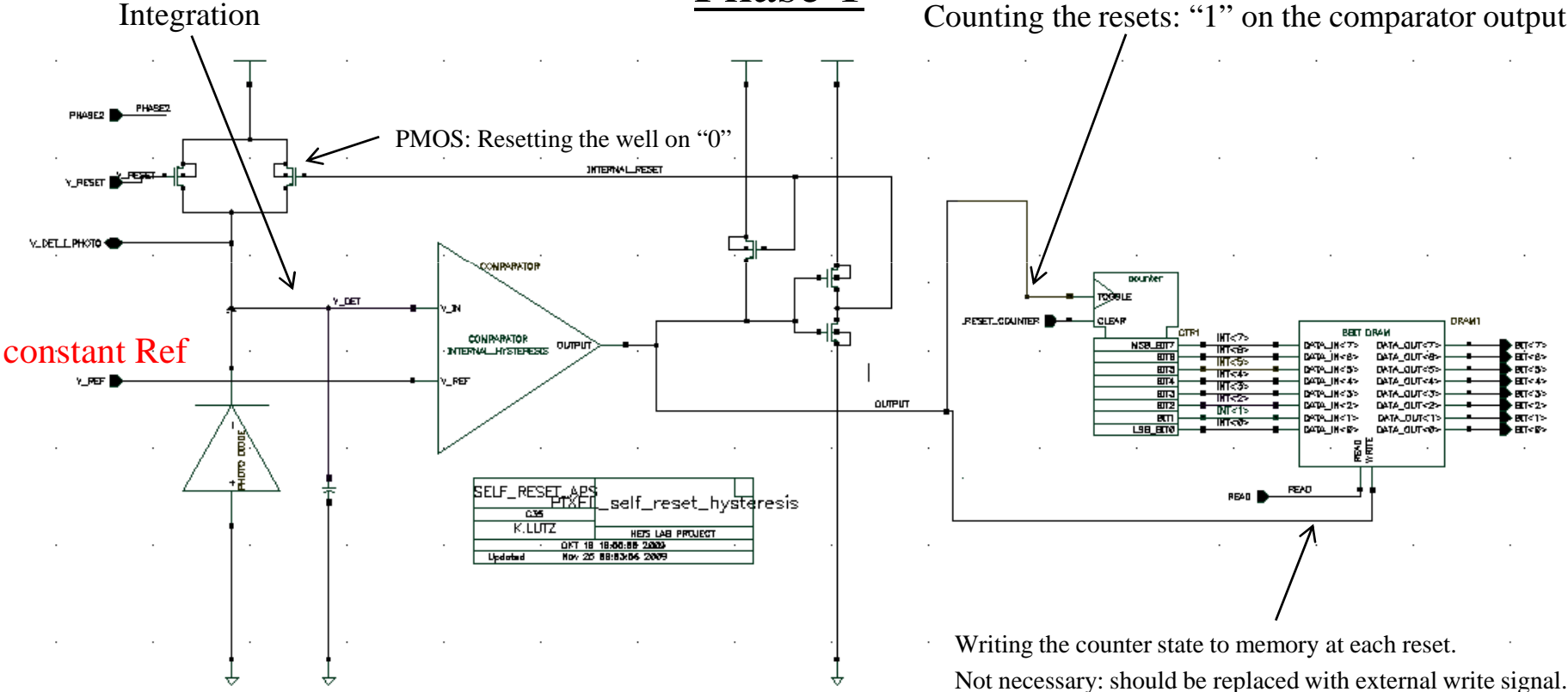


1. Self-Reset Technique


Phase 2

Counting until the ramp is equal to the value held on the capacitance.

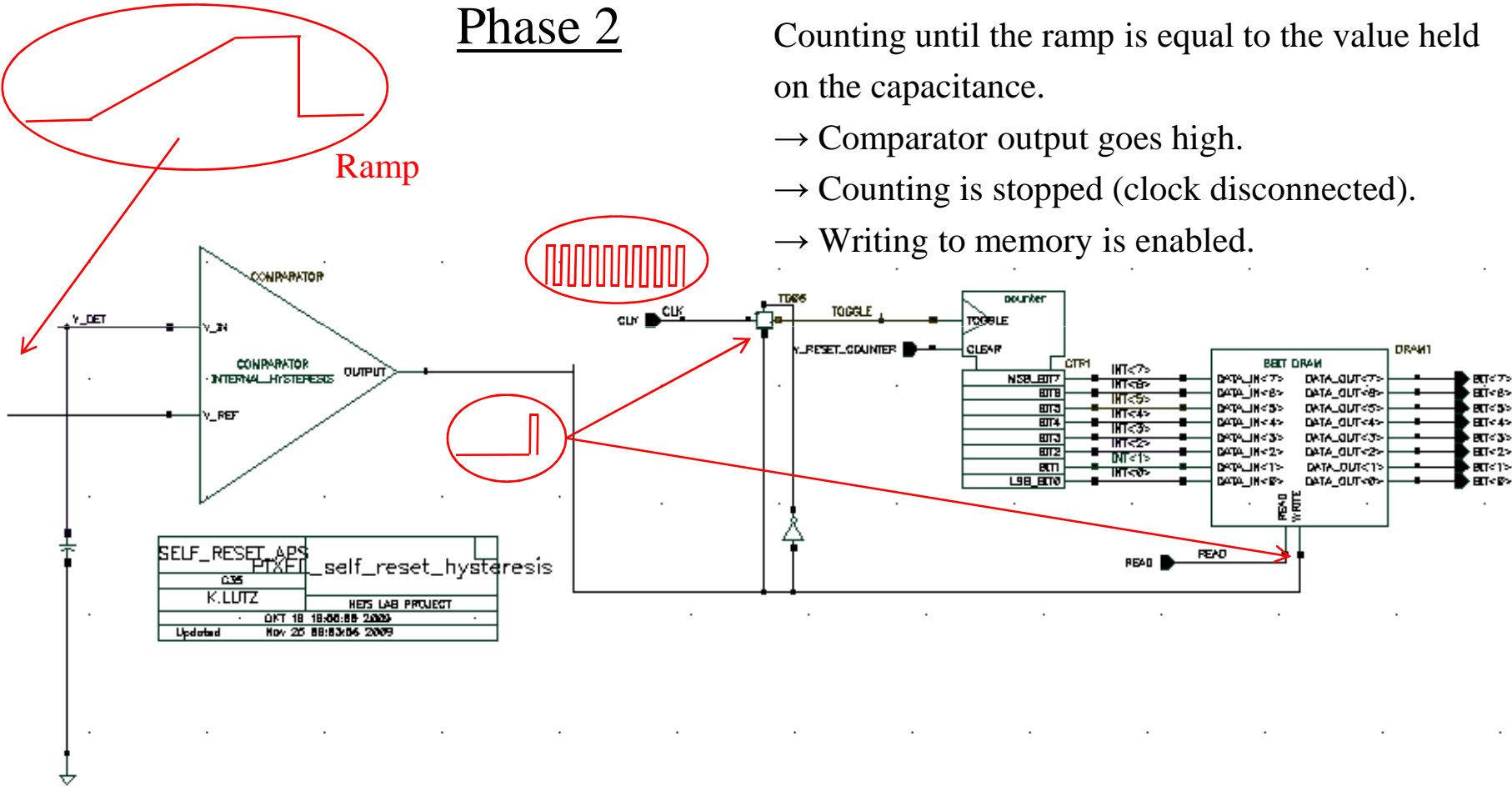
- Comparator output goes high.
- Counting is stopped (clock disconnected).
- Writing to memory is enabled.



1. Self-Reset Technique

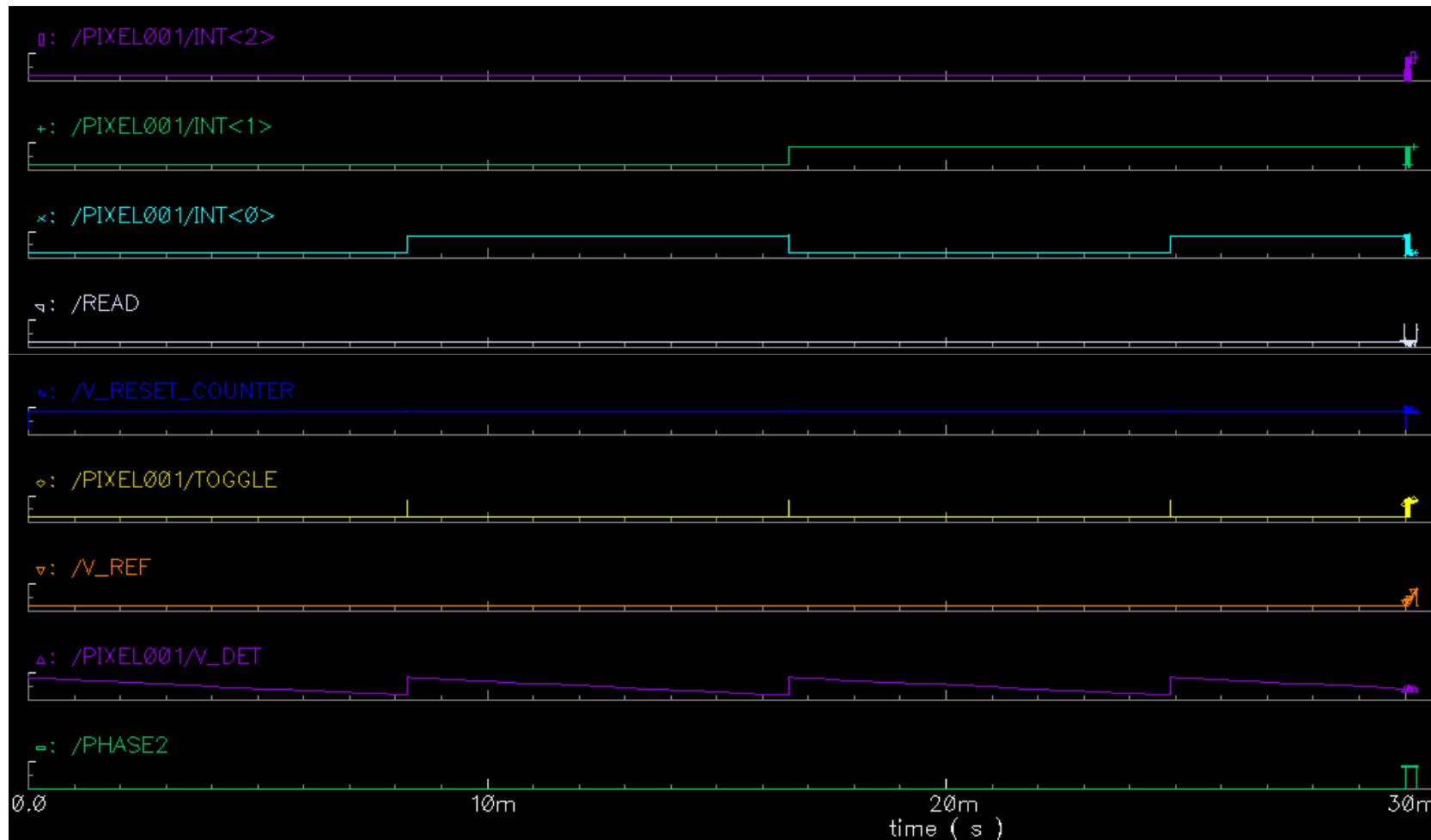

1. Self-Reset Technique

 

2. The Comparator


Design of the comparator will dominate the accuracy of the ADC conversion in phase 1 as well as in phase 2!

Requirements:

- Propagation delay as fast as possible.
- Very low offset voltage:
 - Auto-Zeroing applicable?
 - Reducing mismatch with layout techniques (common-centroid etc.).
 - Also important to **reduce the fixed pattern noise**.
- Proper quiescent point (not resetting the well in the first place).
- Low power consumption.
- **Further problem:**
Comparator will start to oscillate especially on low light intensity!



2. The Comparator

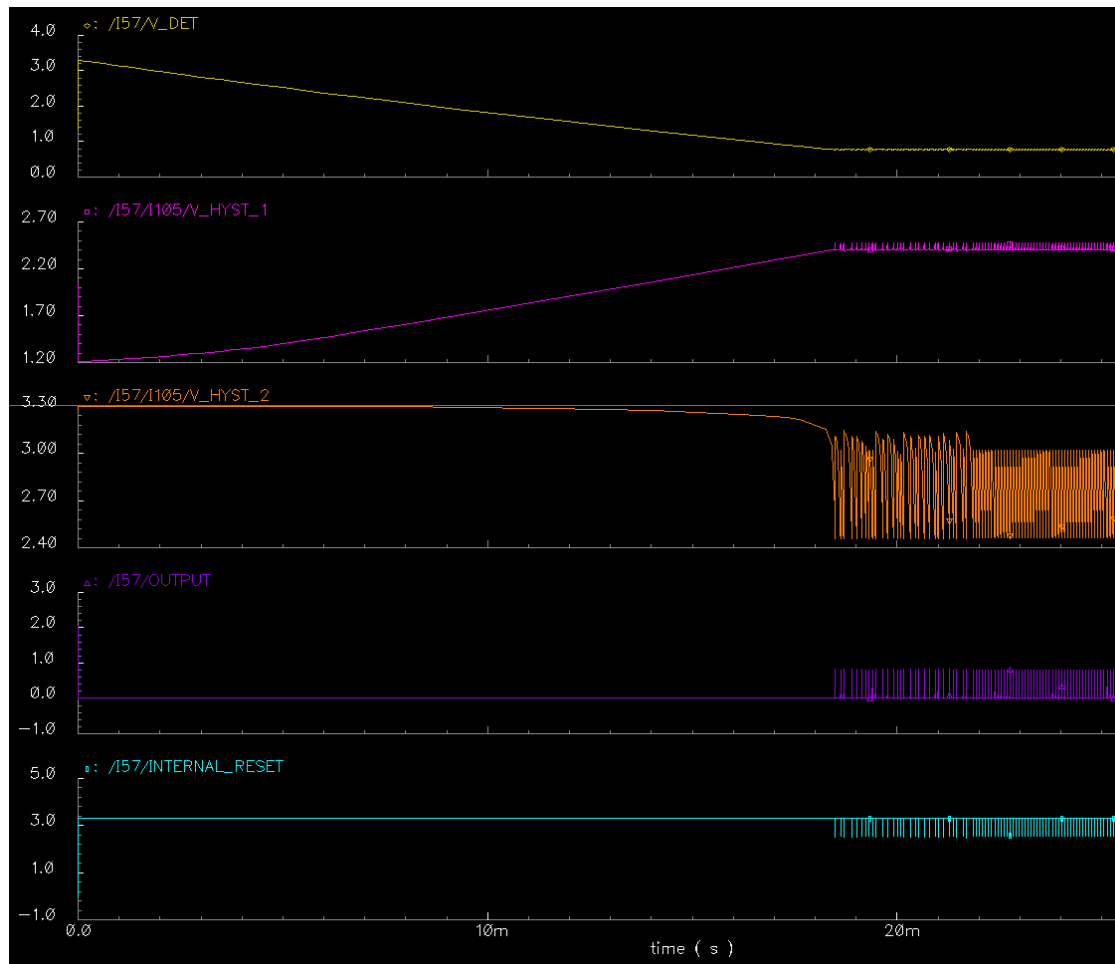

Oscillation:


- Fast switching between reset and integration.
- Well is loaded for short time (subthreshold current)
- Detector Voltage reaches an equilibrium state.

→ No well reset possible!


Solution:

Some kind of hysteresis has to be added to the comparator!

2. The Comparator

 

 A Hysteresis of 20mV turned out to be sufficient to ensure correct operation.




→ Schmitt-Trigger
(different implementations possible)


2. The Comparator

Auto-Zeroing: Phase 1

Auto-Zeroing: Phase 2

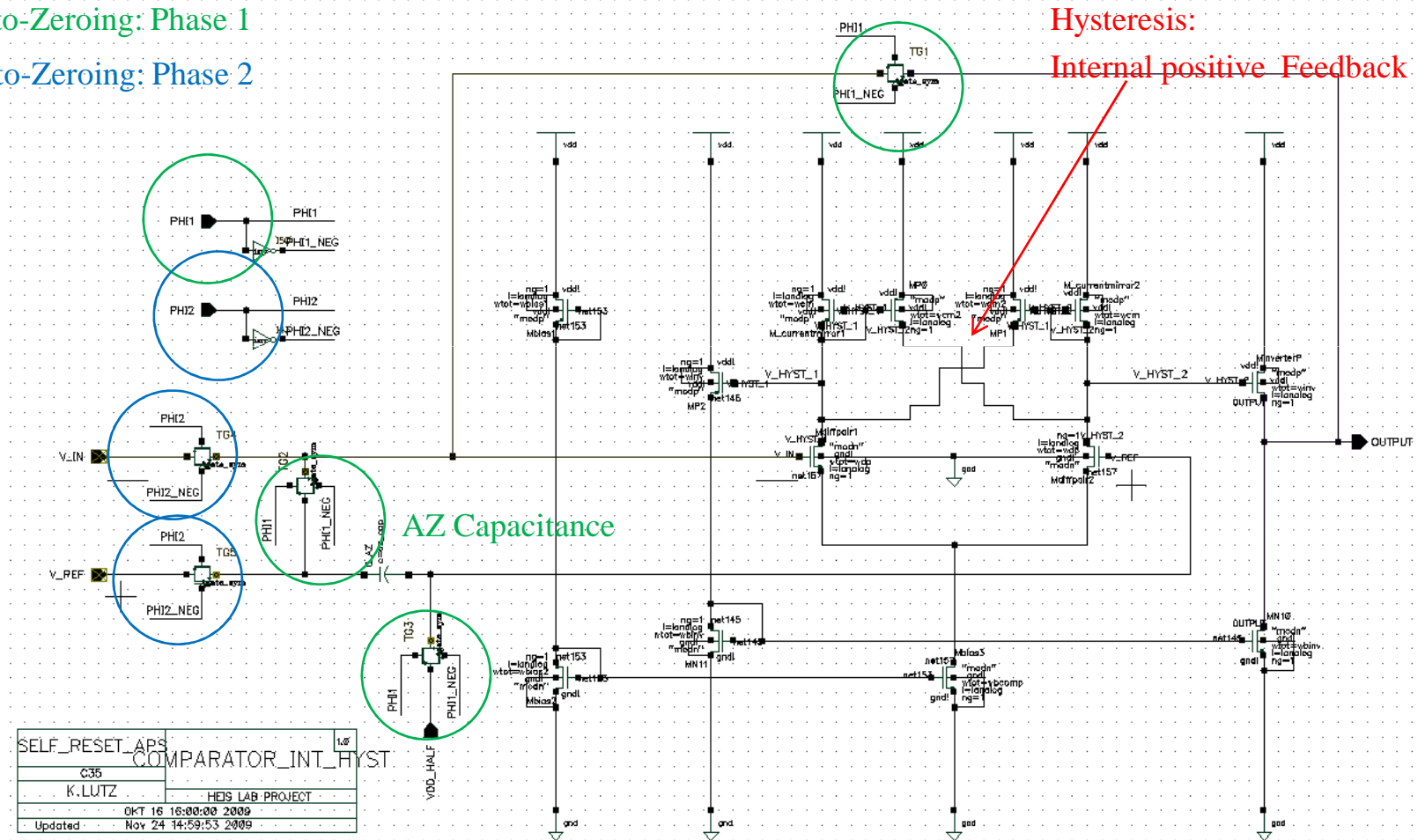


SELF_RESET_APS	COMPARATOR_INT_HYST	1.08
C36		
K.LUTZ	HEIS LAB PROJECT	
	Okt 16 16:00:00 2009	
Updated	Nov 24 14:59:53 2009	

 

Autozeroing Example

 - Also tendency to oscillation.
- Comparator needs to be compensated, or making the AZ-cap very high.
- Slows down the comp.





2. The Comparator

The problem with auto-zeroing:


- How to clock the auto-zeroing phases?
 - Coarse ADC phase is asynchronous.
 - Leakage current increases → falsifies the value in fine ADC.
 - Worst case: Offset needs to be held on the transistor for 30ms (25frames/s)
→ Capacitance will be enormous.
 - AZ only simulated in schematic (with poor results).
 - Final Layout will be without AZ → Layout techniques to reduce mismatch.
- Deeper changes have to be made to make AZ applicable to the sensor.



3. Counter using toggle-FF's

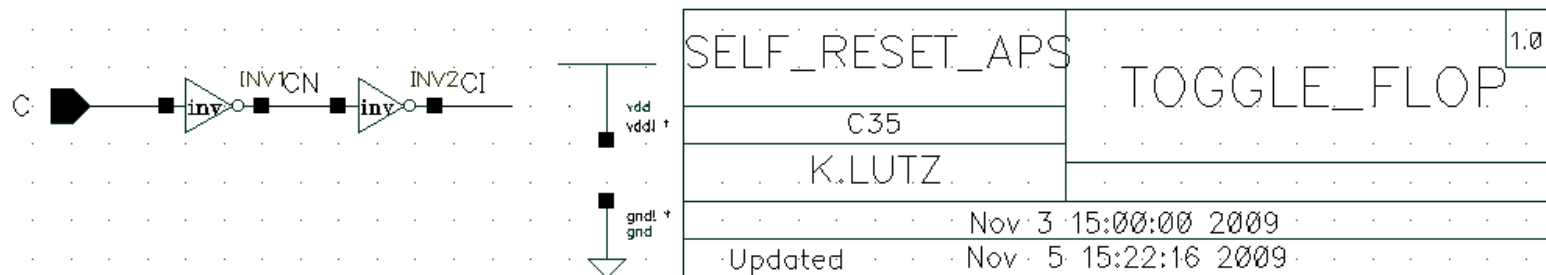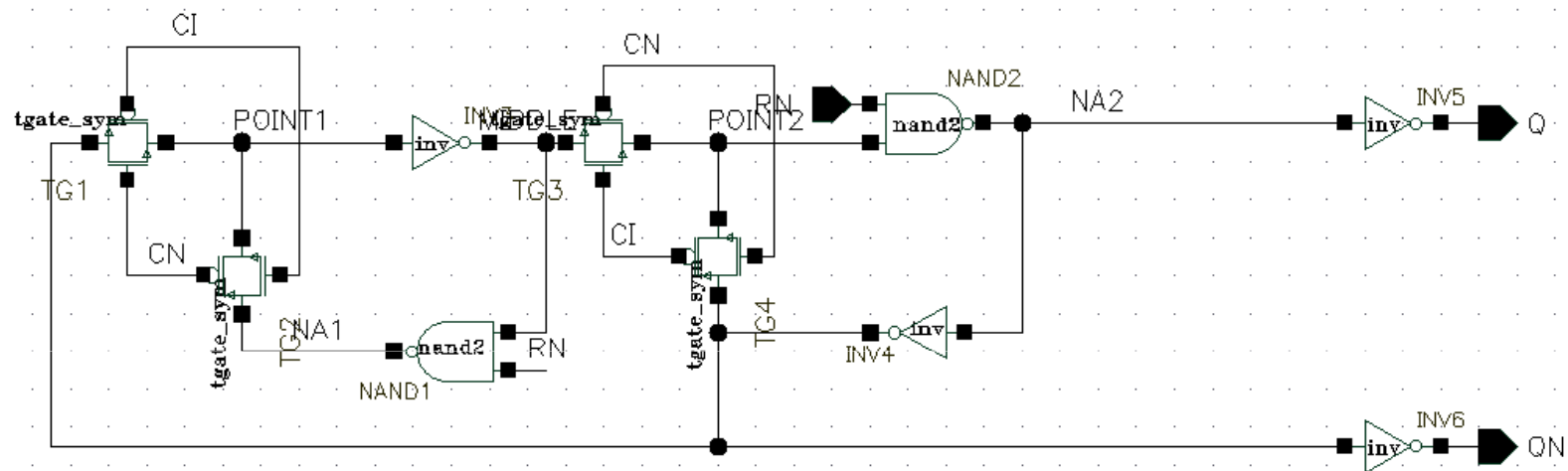


3. Counter using toggle-FF's

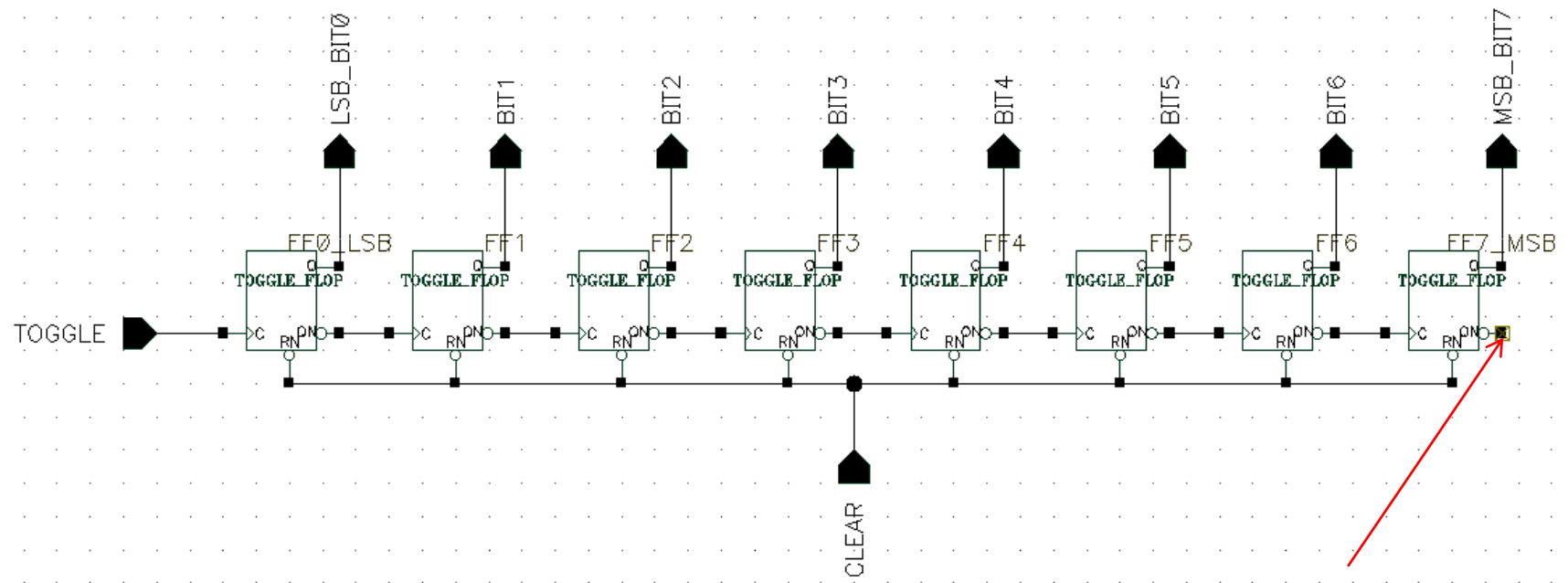

Active low reset

Can be used to detect or prevent counter overflow!

4. 4T DRAM Memory

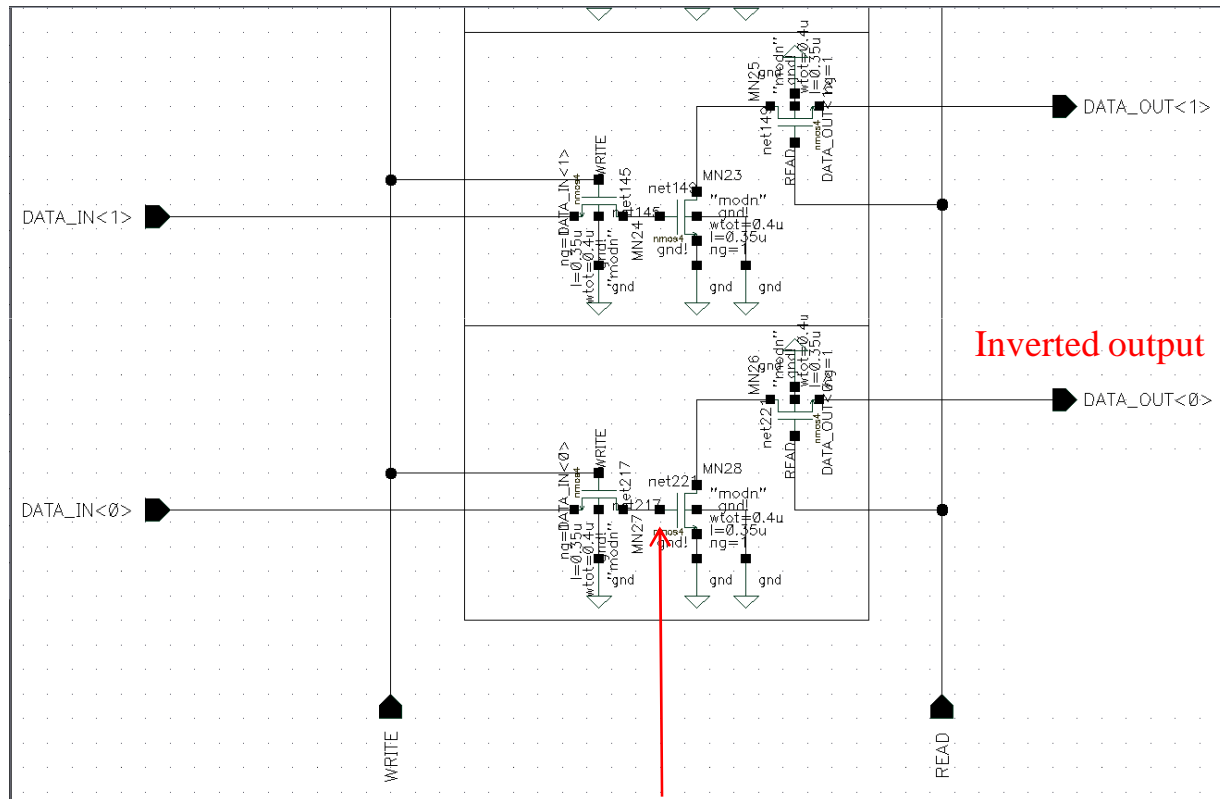

4th transistor is needed to precharge the DATA_OUT bits to high.

1. Global implementation:

Precharging the column bus for each row readout.

2. Local implementation:

Every bit needs its own precharge transistor.






Trade-off in driving strength.

Speed vs. Power consumption




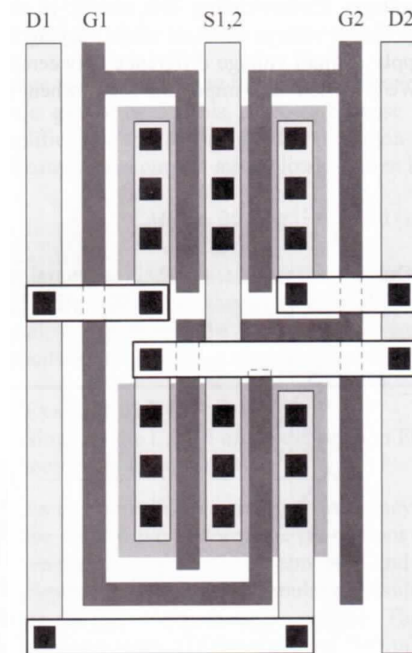   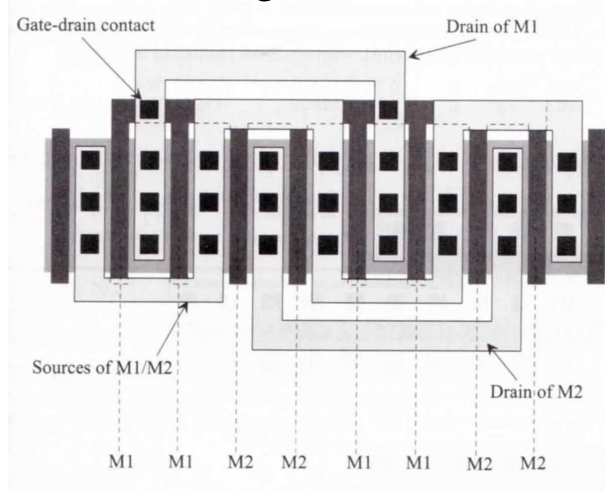5. Layout


- Apply matching techniques to avoid mismatch.
- Common centroid layout to take out manufacturing gradients in both directions.
- Length of analog part has increased to $1\mu\text{m}$ to suffer less from channel length modulation. Digital parts have (mostly) minimum dimensions.
- Dummy transistors, or dummy stripes at the end of rows.
- Separate digital and analog part.
- Shielding of the diode to avoid blooming.




5. Layout: Comparator

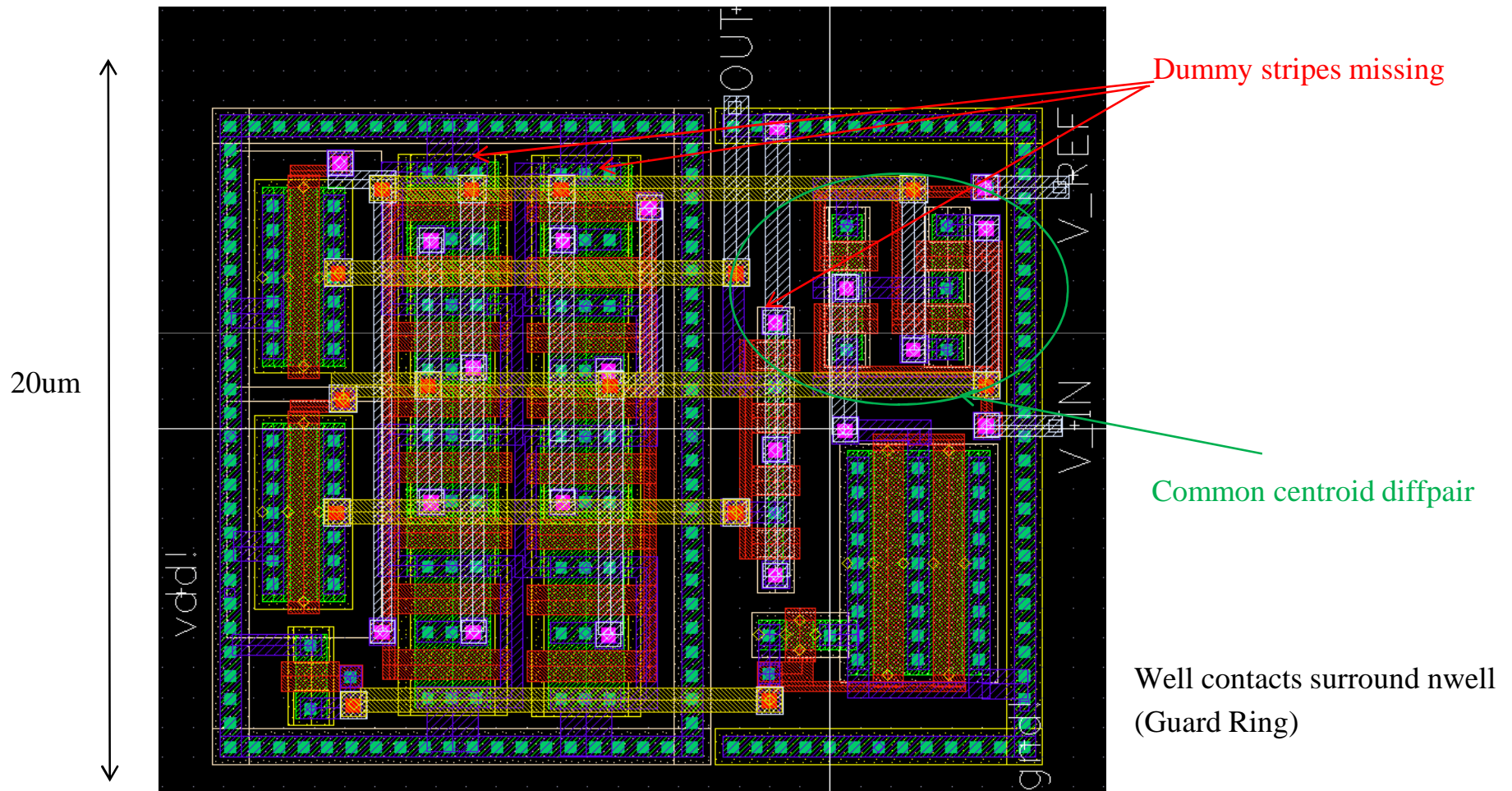



5. Layout: Toggle FF

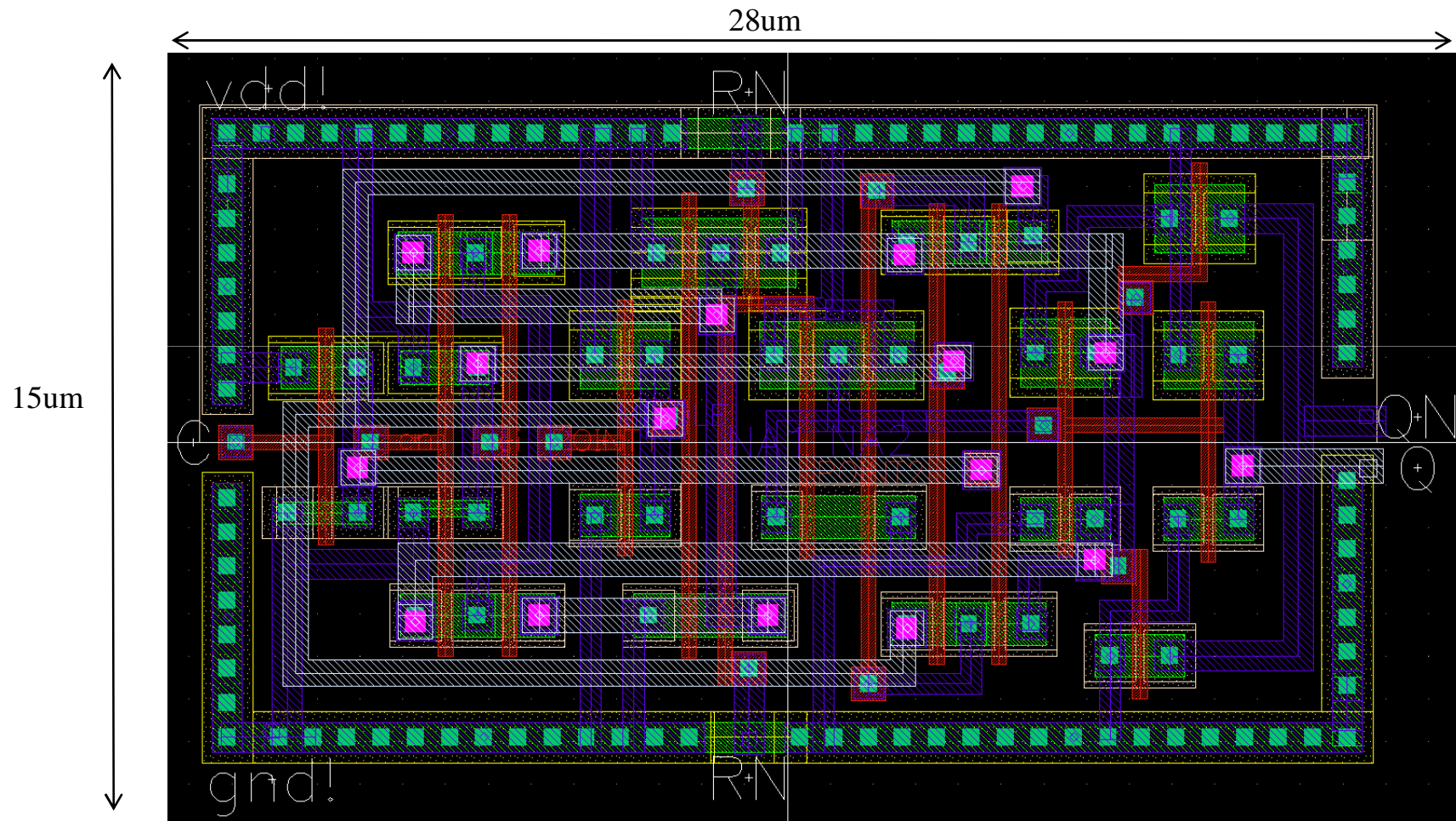


5. Layout: 8 Bit Memory Cell

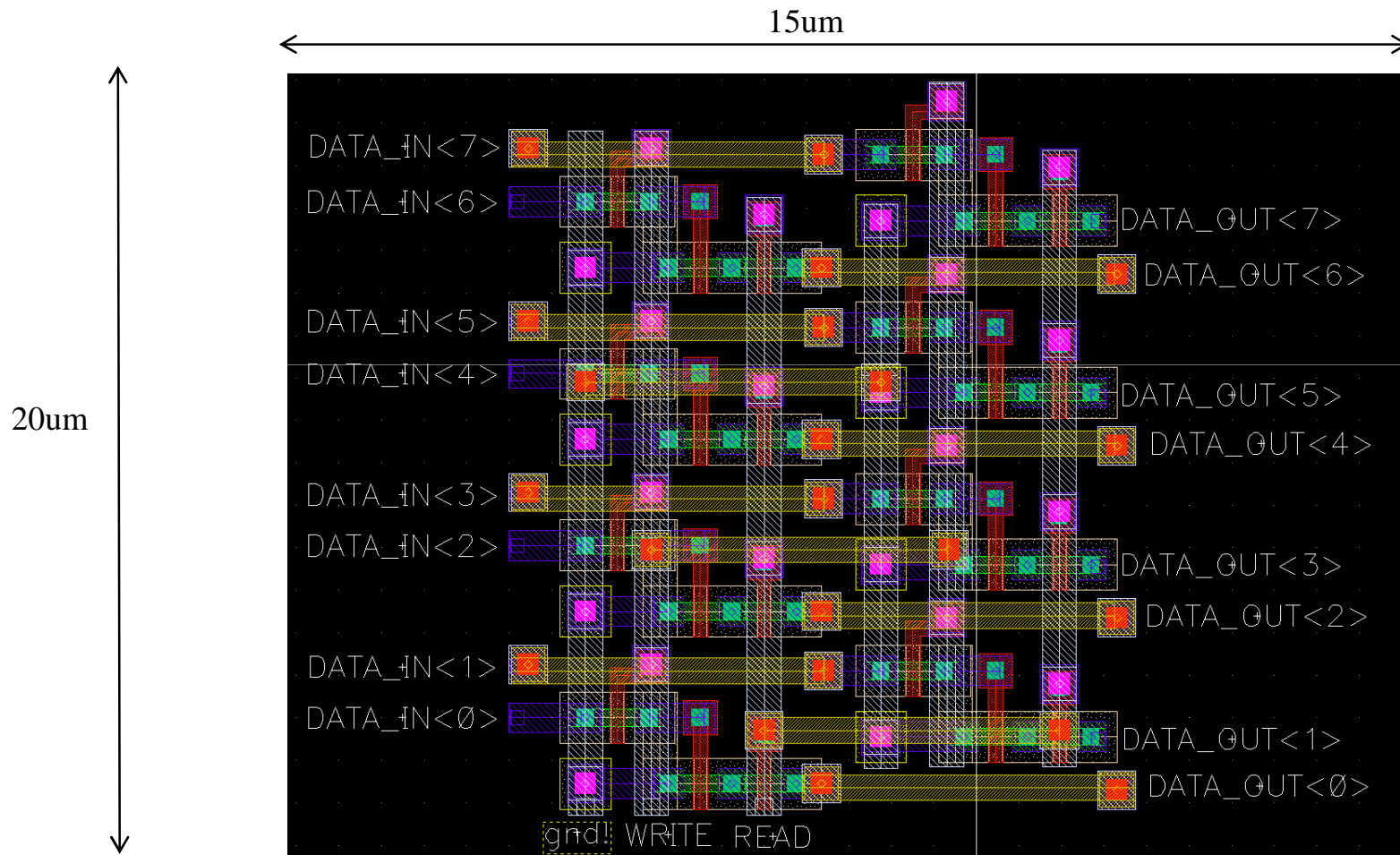

5. Layout

 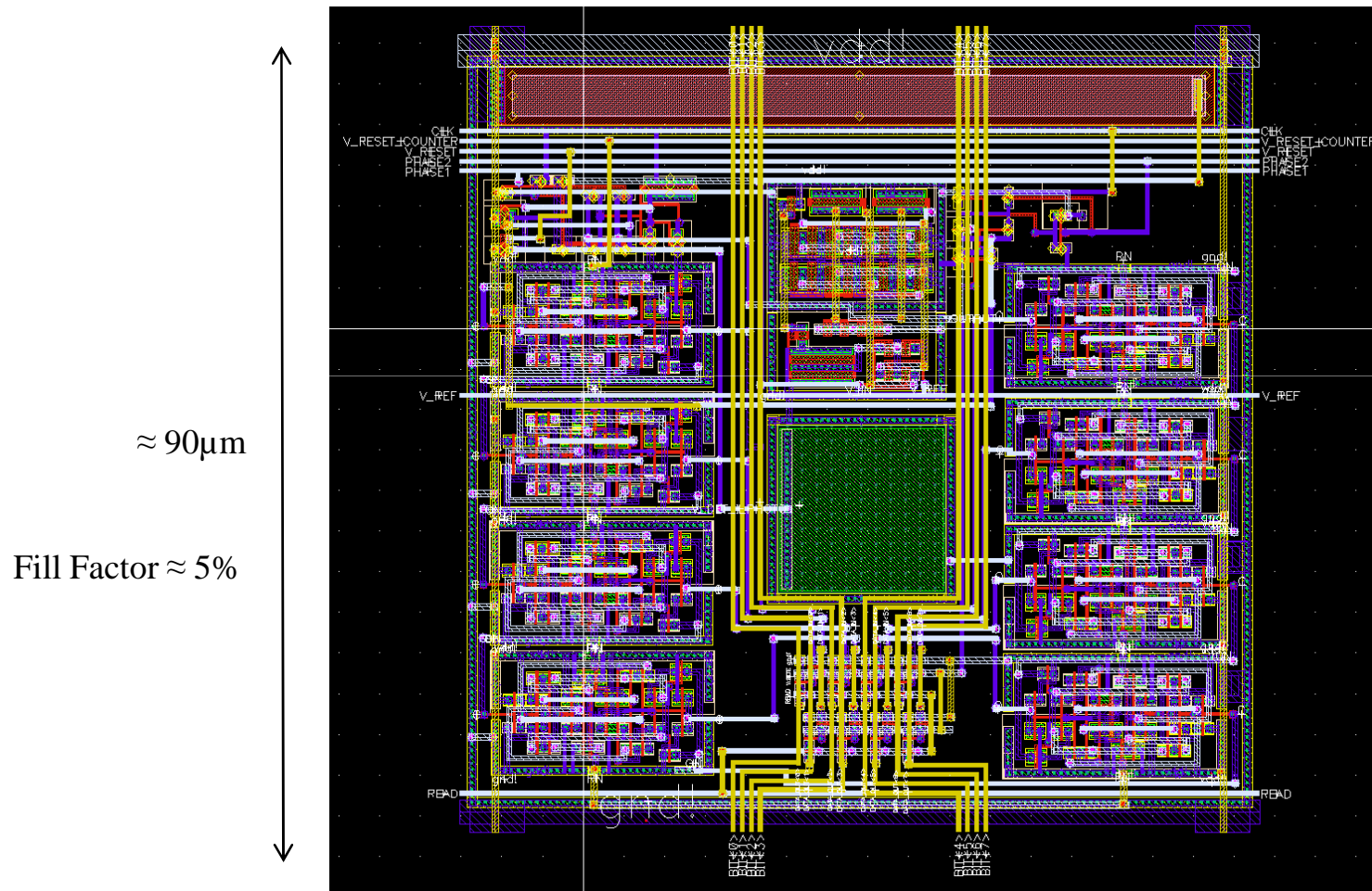


5. Layout

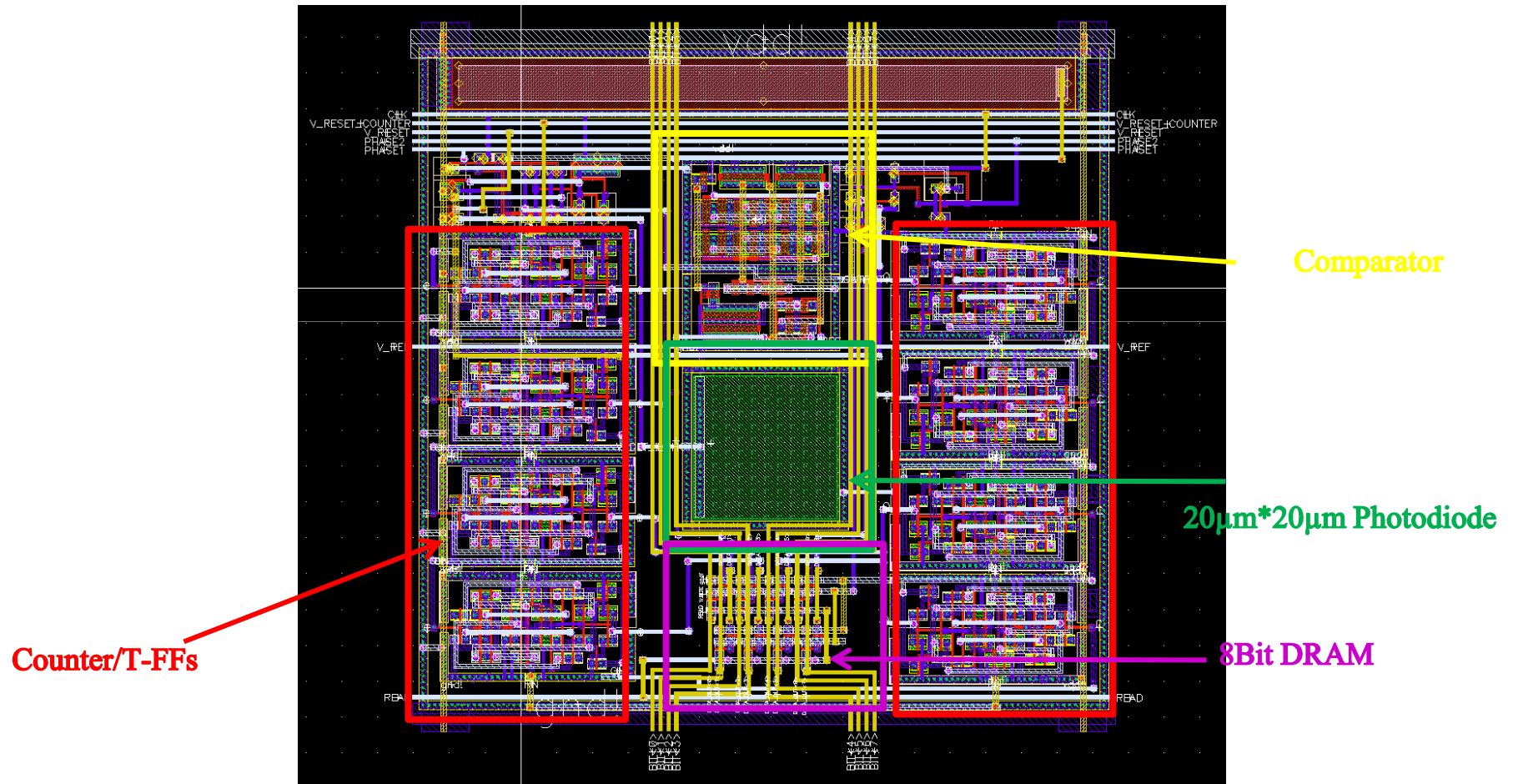

5. Layout

Extracted view:

 

5. Layout – LVS

```
File /exp
@(#)SCDS: LVS version 5.0.0 05/30/2003 19:44 (cds11939) $
Like matching is enabled.
Net swapping is enabled.
Fixed device checking is enabled.
Using terminal names as correspondence points.
Permute MOS option disabled.

Net-list summary for /export/users/sens5/LVS/layout/netlist
count
144 nets
18 terminals
156 rmos4
1 cpoly
143 pmos4
1 nd

Net-list summary for /export/users/sens5/LVS/schematic/netlist
count
144 nets
18 terminals
151 rmos4
1 cpoly
131 pmos4
1 nd

Terminal correspondence points
1 BIT<0>
2 BIT<1>
3 BIT<2>
4 BIT<3>
5 BIT<4>
6 BIT<5>
7 BIT<6>
8 BIT<7>
9 CLK
10 PHASE1
11 PHASE2
12 READ
13 V_DET_I_PHOTO
14 V_REF
15 V_RESET
16 V_RESET_COUNTER
17 gnd!
18 vdd!
```

```
The net-lists match.

                layout schematic
                instances
un-matched      0      0
rewired         0      0
size errors     0      0
pruned         0      0
active          301    284
total           301    284

                nets
un-matched      0      0
merged         0      0
pruned         0      0
active          144    144
total           144    144


                terminals
un-matched      0      0
matched but
different type  0      0
total           18     18

Probe files from /export/users/sens5/LVS/schematic
devbad.out:
```

 5. Layout

Matrix layout :

- Easy placement .
- No routing channels needed.
- Input signals (clk, v_ref, etc.) connected from the left.
- Column bus from top to bottom, routed inside the cell.
- Row_Select signals connect and disconnect the outputs to the column bus.
- Column busses will be read out with e.g. shift register.



6. Simulation Results


Phase1:

- RESET_COUNTER
- READ

Phase2:

- RESET_COUNTER
- READ

Precharging: Done outside the pixel cell

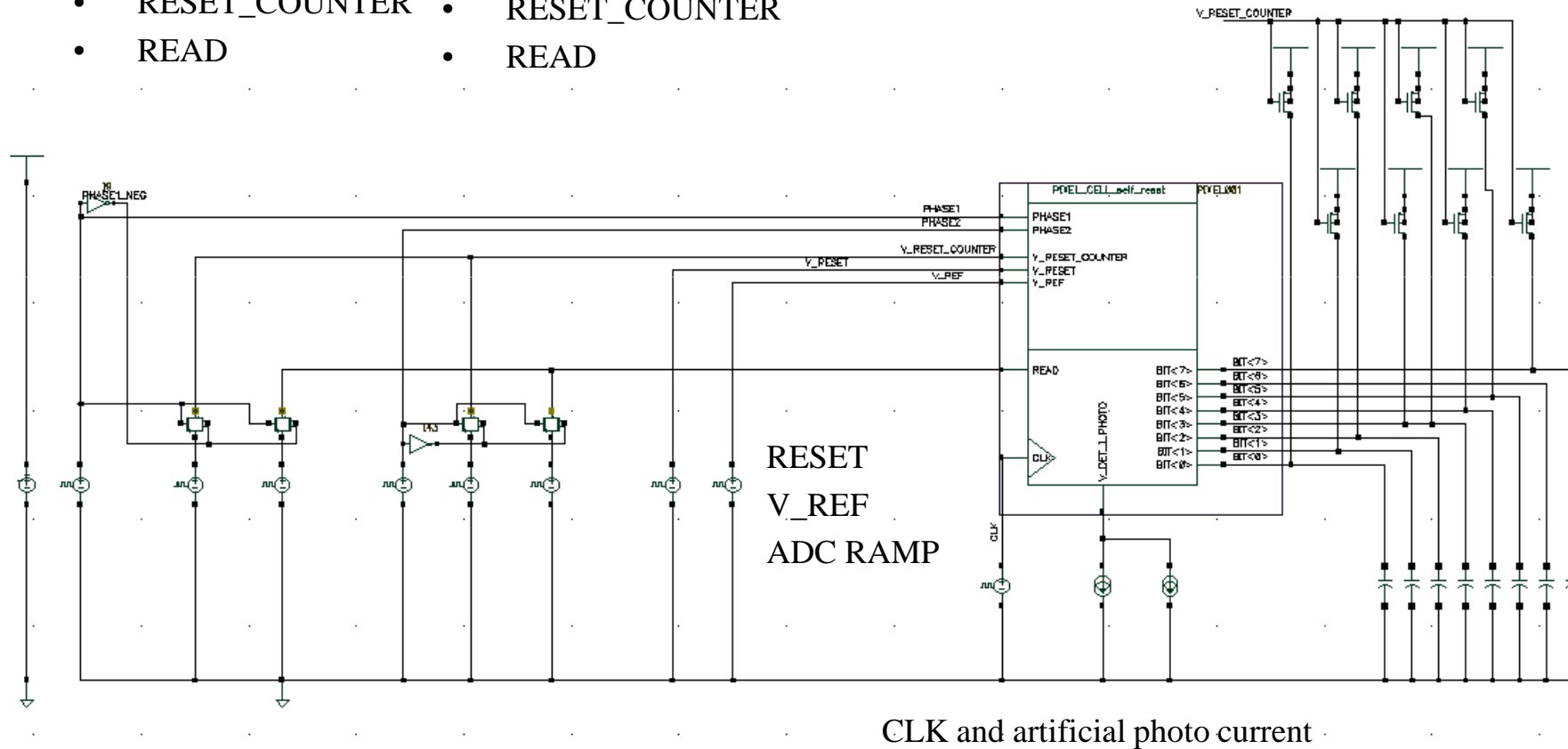

6. Simulation Results


- Photo diode with $20\mu\text{m} \times 20\mu\text{m}$. Pixel Cell $\approx 90\mu\text{m} \times 90\mu\text{m}$
→ Fill Factor $\approx 5\%$
- Dark current $\approx 4\text{fA}$.
- Resetting the well to V_{dd} (3.3v).
- Integrating down to 750mV .
- Integration time 30ms (10ms reserved for readout → 25 frames/s)
- 2.55V with a resolution of 8bit → 0.01V per step.
- Ramp raise time of $255\mu\text{s}$.
- Clock period time of $1\mu\text{s}$.
- Dynamic Range $\approx 100\text{dB}$ ($200\text{fA} - 20\text{nA}$ photocurrent) - Normal APS $\approx 60\text{dB}$

$$DR(\text{dB}) = 20 \log\left(\frac{20 \times 10^{-9}}{200 \times 10^{-15}}\right) = 20 \log(10^5) = 100\text{dB}$$




6. Simulation Results


Max. current before reset: 255

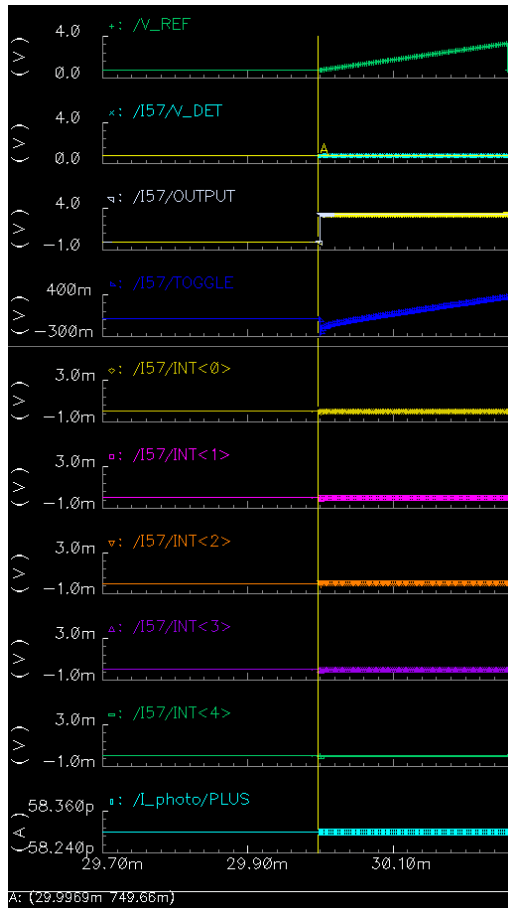


Decrease current: 760mV → 254

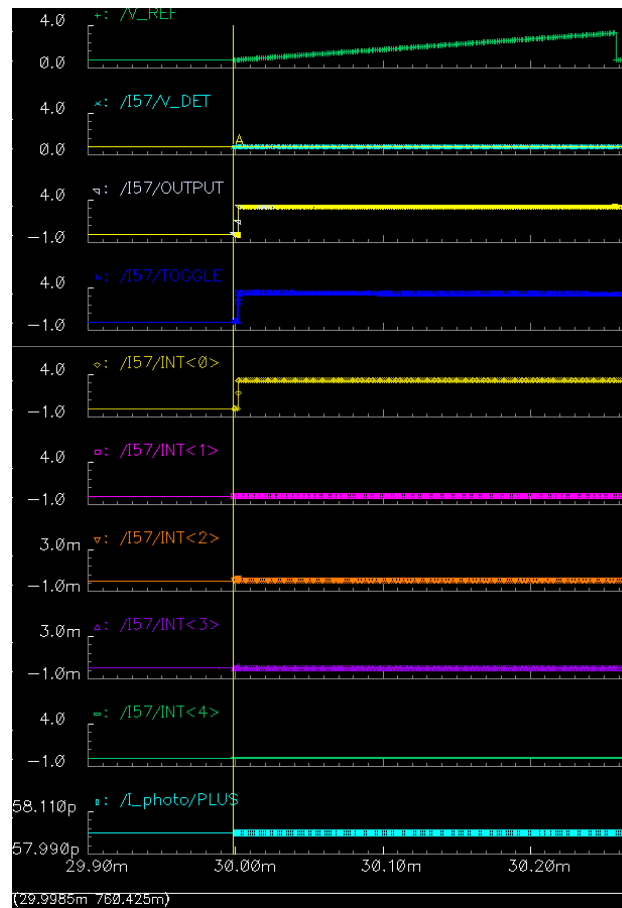

Further decrease : 1.05V → 225

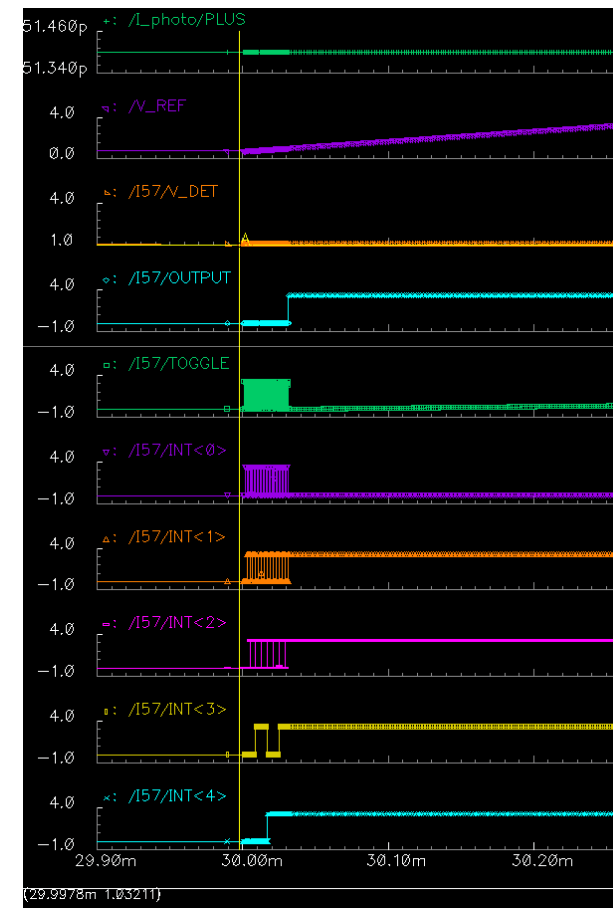


6. Simulation Results

 


- Maximum detectable current $\approx 20\text{nA}$
 - 30ms integration
- $\approx 100\mu\text{s}$ between each resets.

6. Simulation Results

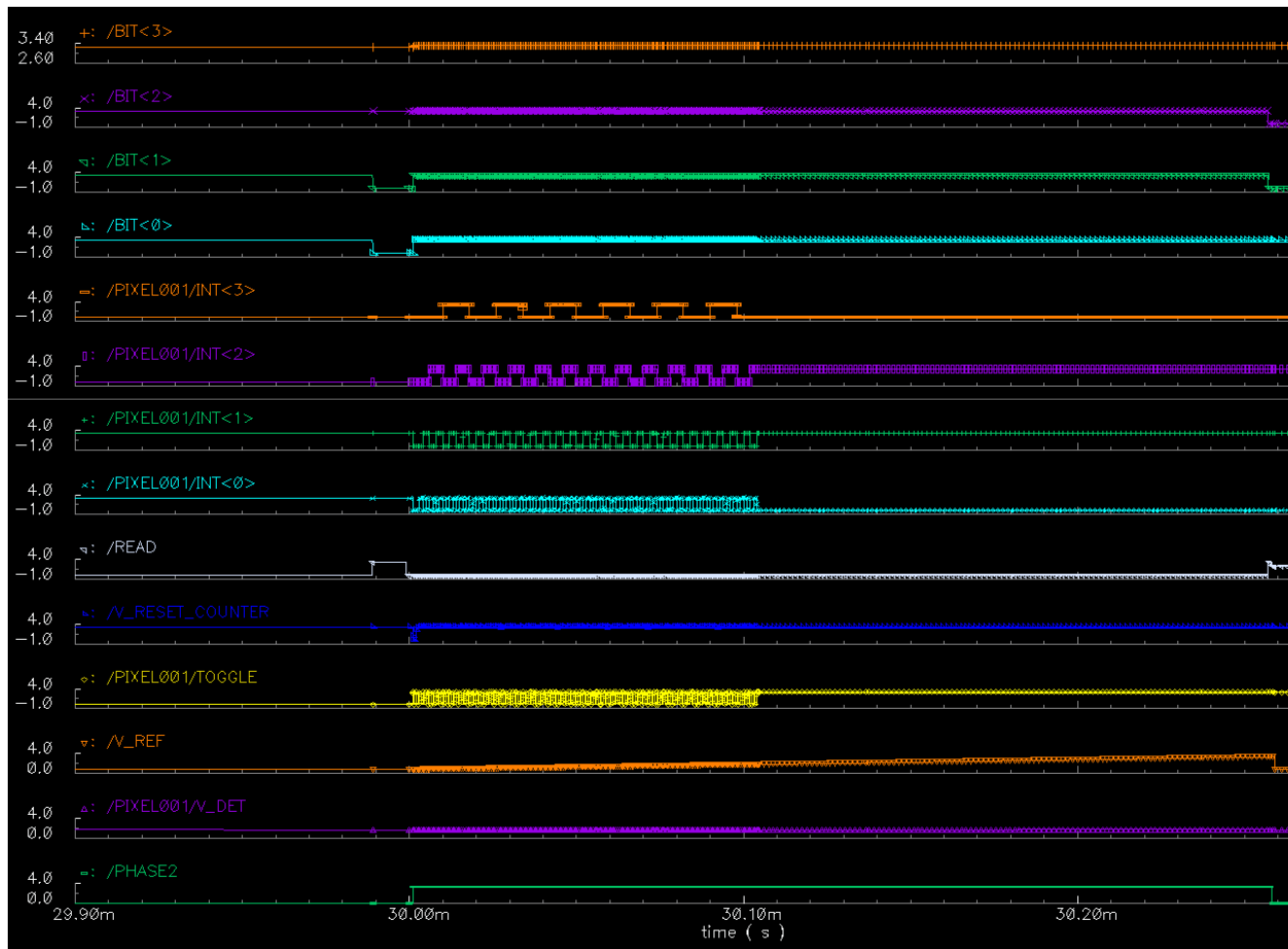


6. Simulation Results

 


6. Simulation Results

Schematic of the matrix:

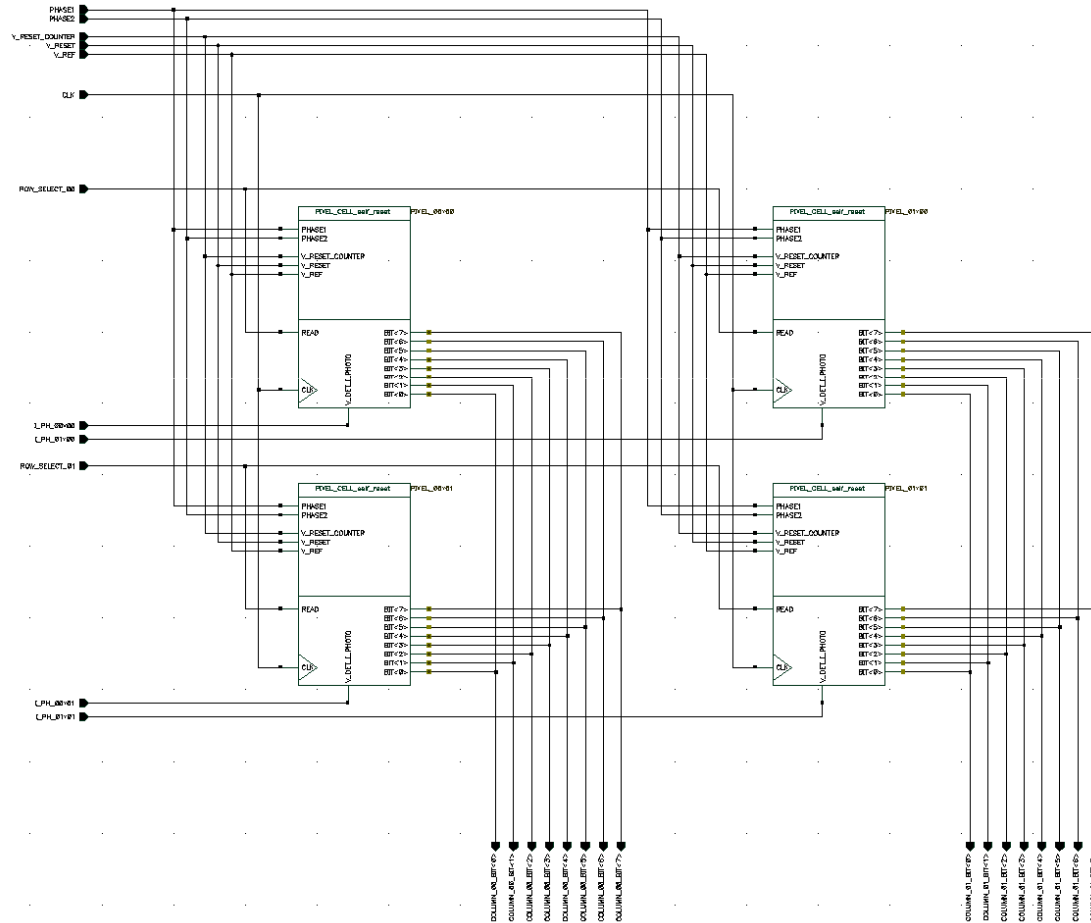

6. Simulation Results

Matrix testing environment:

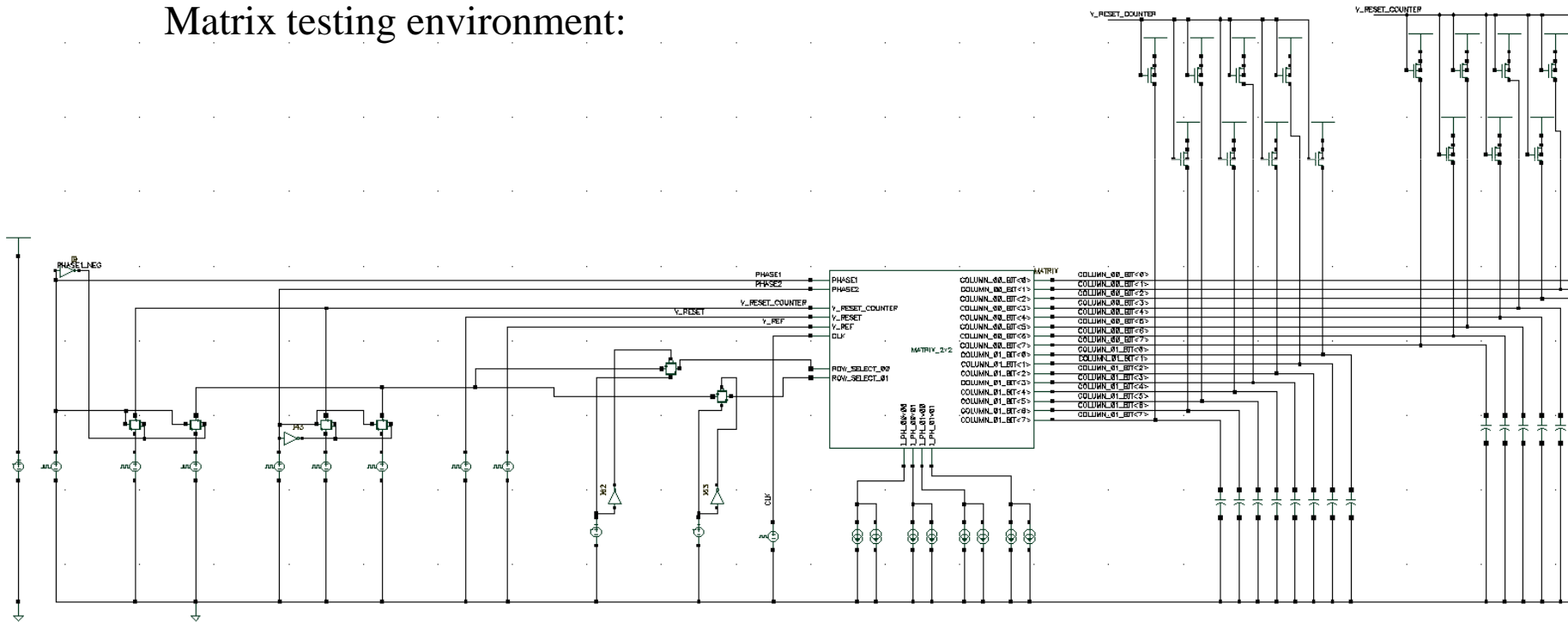


Conclusion and Future Work

- Dynamic range is increased at the cost of dramatically decreased fill factor and an increase in power consumption and complexity!
- SNR improvement makes this technique preferable over the others.
- Hysteresis is important to ensure proper operation.
- Many sources of mismatch resulting in increased FPN remain. Matching is very important when it comes to the layout.
- To apply auto-zeroing to the sensor, the offset needs to be stored in different ways (DAC) or the ADC conversion scheme has to be changed to make the behavior more predictable or synchronous.
- Readout and precharge cycles will be time and energy consuming.
Maximal frame rate should be determined (Rhee, Joo up to 1000 frames/s)



Conclusion and Future Work

 - Readout scheme has to be developed
 - 8bit coarse ADC and 8bit fine ADC.
- Investigate time discrete operation with photocurrent estimation [9].
- Reinvestigate solutions to apply auto-zeroing:
 - Add 3. phase with offset readout – store in outside memory and add/sub later from measured values.
 - Make resets synchronous (see. [1][9]).



Bibliography

- [1] Kavusi, El Gamal, „Quantitative Study of High Dynamic Range Image Sensor Architectures“, in Sensors and Camera Systems for Scientific, Industrial and Digital Photography Applications, 2004.
- [2] Yang, El Gamal. „Comparative Analysis of SNR for Image Sensors with Enhanced Dynamic Range“, Information Systems Laboratory, Stanford University, 1999.
- [3] El Gamal, Eltoukhy, „CMOS Image Sensors“, IEEE Circuits and Devices Magazine, May/June 2005.
- [4] Rhee, Joo, „A Wide Dynamic-Range CMOS Image Sensor Using Self-Reset Technique“, IEEE Electron Device Lett., Vol. 28, October 2007.
- [5] Rhee, Joo, „Wide dynamic range CMOS image sensor with pixel level ADC“, Electron. Lett., Vol. 39 (4), February 2003.
- [6] Tauschek, „17 bit für jedes Pixel“, Fachartikel für Photonik.
- [7] Kleinfelder et al., „A 10,000 Frames/s 0.18 μ m CMOS DPS with Pixel-Level-Memory“, International Solid State Circuits Conference, Feb. 2001.



Bibliography

- [8] McIlrath, „A Low-Power Low-Noise Ultrawide-Dynamic-Range CMOS Imager with Pixel-Parallel A/D Conversion“, IEEE Journal of Solid-State Circuits, May 2001.
- [9] Liu, El Gamal,“ Photocurrent Estimation for a Self-Reset CMOS Image Sensor“, Information Systems Laboratory Stanford, Jan. 2002.
- [10] Allen, Holberg,“CMOS Analog Circuit Design“, Oxford Press, Second Edition, 2002.
- [12] Baker, „CMOS: Circuit Design, Layout and Simulation“, Wiley, Second Edition, 2007.
- [13] Prof. Dr.-Ing. Andreas König, „Manufacturing Technology and Design of Integrated Sensor Systems (HEIS) lecture slides“.
- [14] Prof. Dr.-Ing. Andreas König, „TESYS lecture slides“.
- [15] Prof. Dr.-Ing. Andreas König, „Elektronik II lecture slides“.



The End

Thank you for your attention!

Questions?

