


Designing an Operational Amplifier

CAD-Laboratory
in Sensor Electronics

by Robert Freier

Goal

 - **Design of a differential amplifier: sizing and layout**
 - for given specifications
 - **0.351 μm Austria Microsystems technology**
 - **precisely adjustable for use of high-speed operation**



Overview

- **Parameter calculation according to Allen/Holberg design plan**
- **Simulation**
 - adjust values if necessary
 - optimize for high-speed operation / slew rate
- **Inclusion of scalable transistors**
 - precise adjustment / optimization
- **Simulation**
- **Layout drawing**
- **Simulation / verification**

Parameter Calculation

compensation capacitance:

$$C_C > 0.29C_L$$

tail current:

$$I_5 = SR \cdot C_C$$

Transistor M3:

$$S_3 = \frac{W_3}{L_3} = \frac{2I_3}{K'_3 [V_{DD} - V_{in}(\max) - |V_{T03}|(\max) + V_{T1}(\min)]^2} \geq 1$$

Transistors M1 + M2:

$$g_{m1} = GB \cdot C_C \Rightarrow S_1 = S_2 = \frac{g_{m2}^2}{K_2' I_5}$$

Parameter Calculation

Transistor M5:

$$V_{DS5}(sat) = V_{in}(\min) - V_{SS} - \sqrt{\frac{I_5}{\beta_1}} - V_{T1}(\max) \geq 100mV$$

$$S_5 = \frac{2I_5}{K_5' [V_{DS5}(sat)]^2}$$

Transistor M6:

$$g_{m6} = 2.9g_{m2} \frac{C_L}{C_C}$$

$$S_6 = \frac{g_{m6}}{K_6' V_{DS6}(sat)}$$

Parameter Calculation

Transistor M7:

$$I_6 = \frac{g_{m6}^2}{2K_6'V_{DS6}(sat)}$$

$$S_7 = \frac{I_6}{I_5} S_5$$

Check gain and power dissipation:

$$A_V = \frac{2g_{m2}g_{m6}}{I_5(\lambda_2 + \lambda_4)I_6(\lambda_6 + \lambda_7)}$$

$$P_{diss} = (I_5 + I_6)(V_{DD} + |V_{SS}|)$$


Simulation

Simulation delivers results far from desired specifications!


- ⇒ ***adjust values manually***
(with respect to above mentioned relations)
- ⇒ ***optimize slew rate***

	S1	S2	S3	S4	S5	S6	S7	C_c
calculated	1	1	1	1	1	2	63	1,43pF
adjusted	11	11	2	2	1	115	30	1,2pF


Circuit

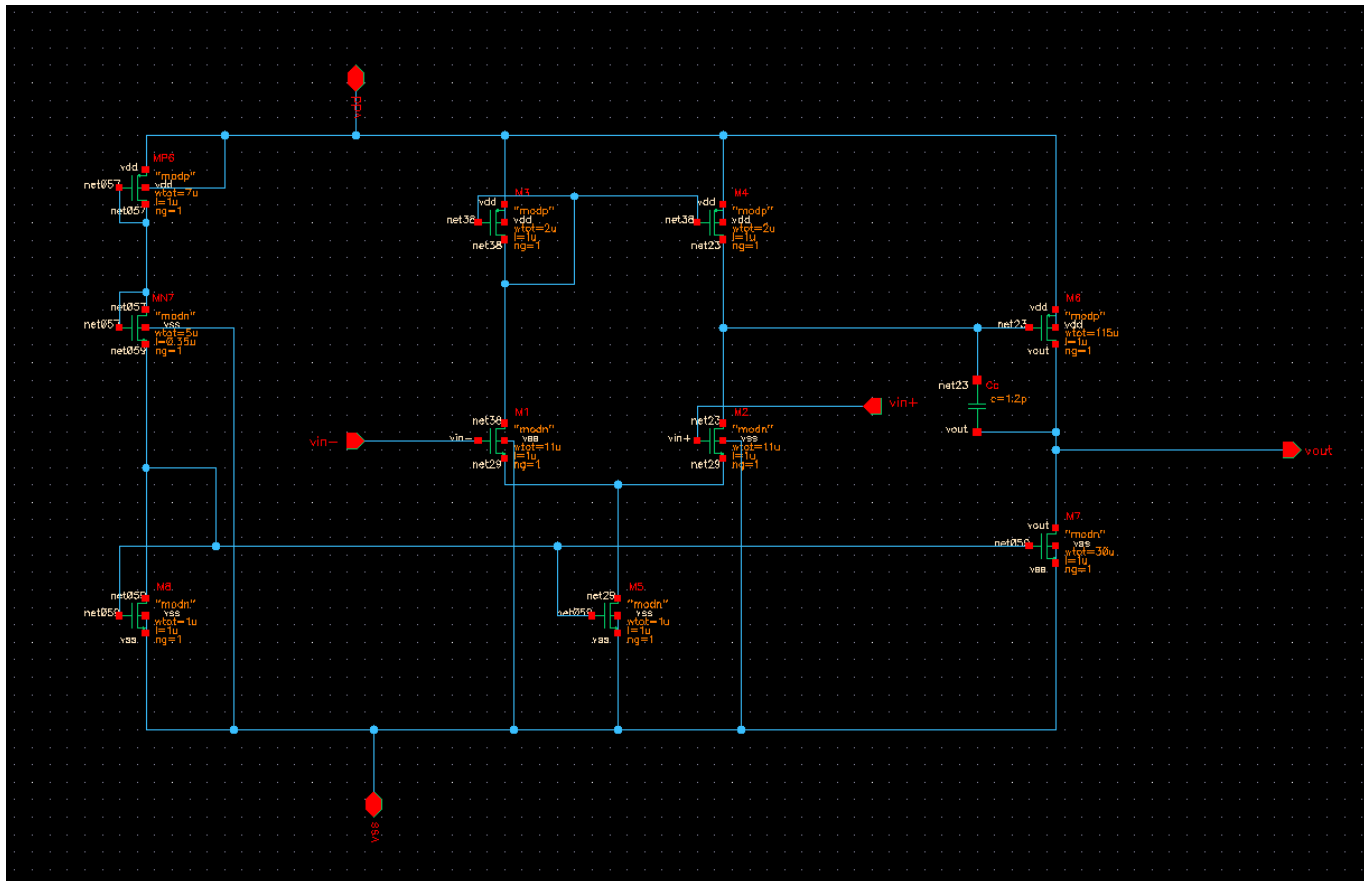


Bode plot

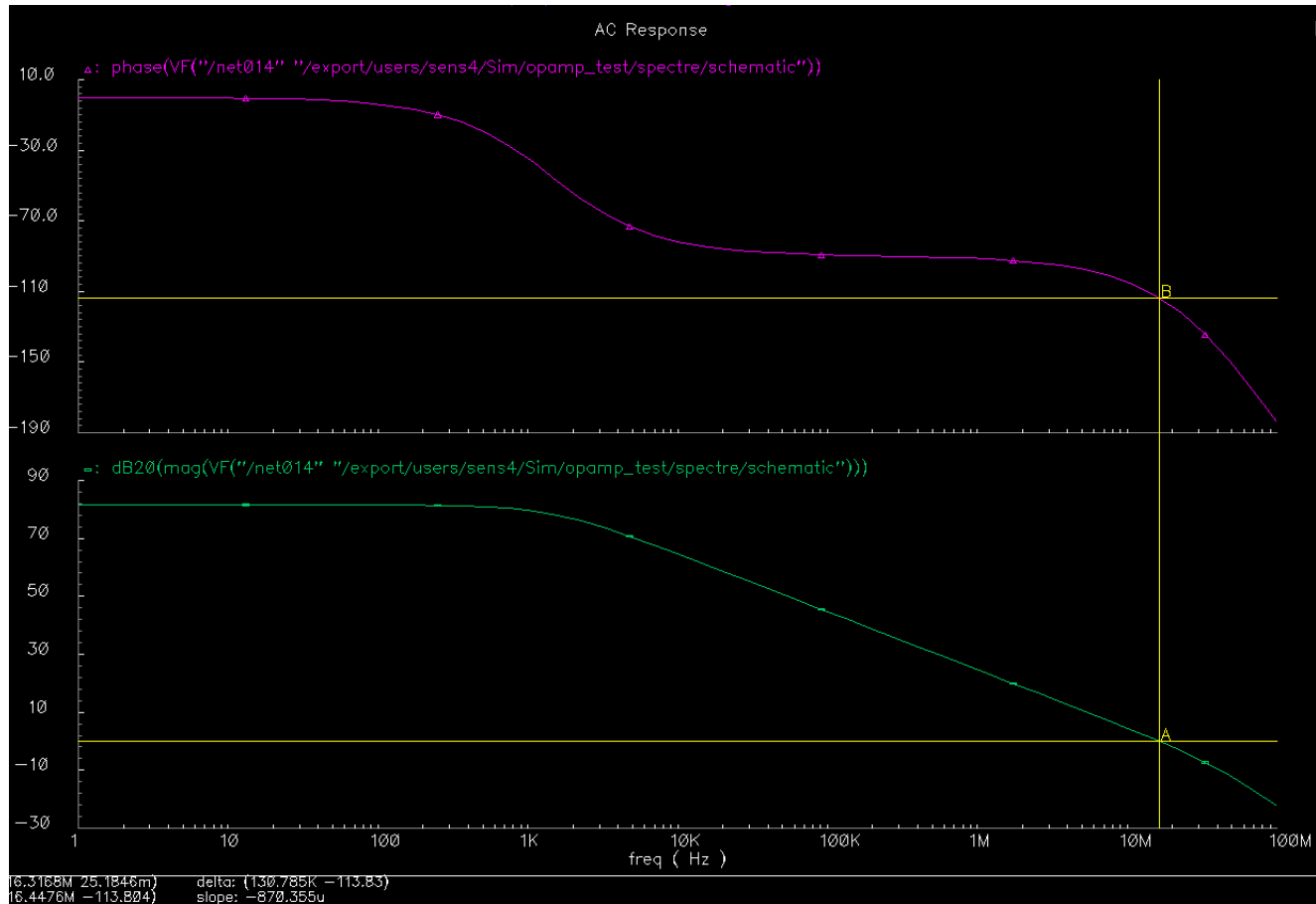

Offset

 


CMRR

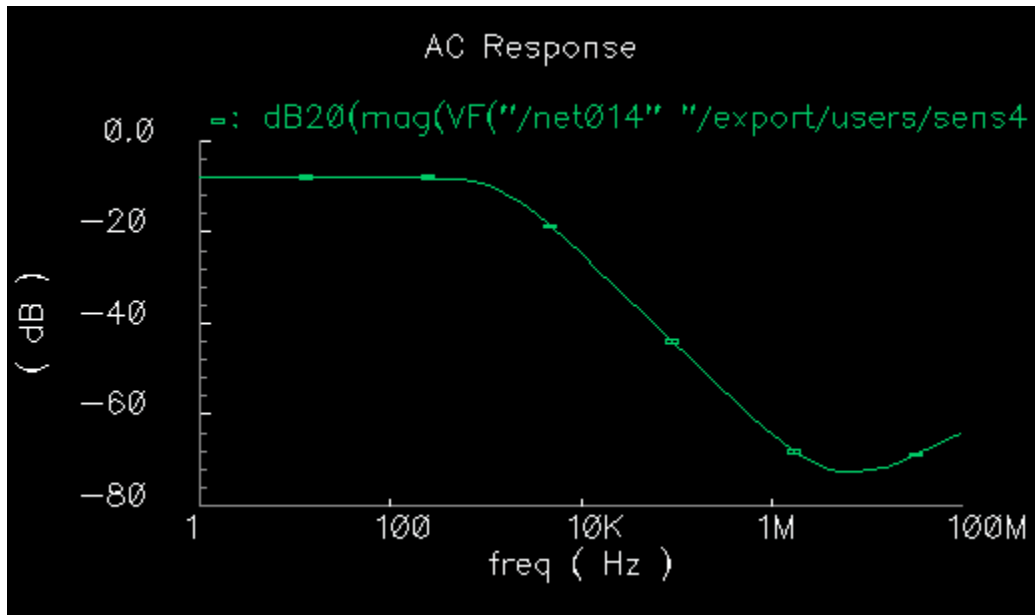


common mode gain

CMRR = (differential-mode gain) – (common-mode gain)


Input CMR

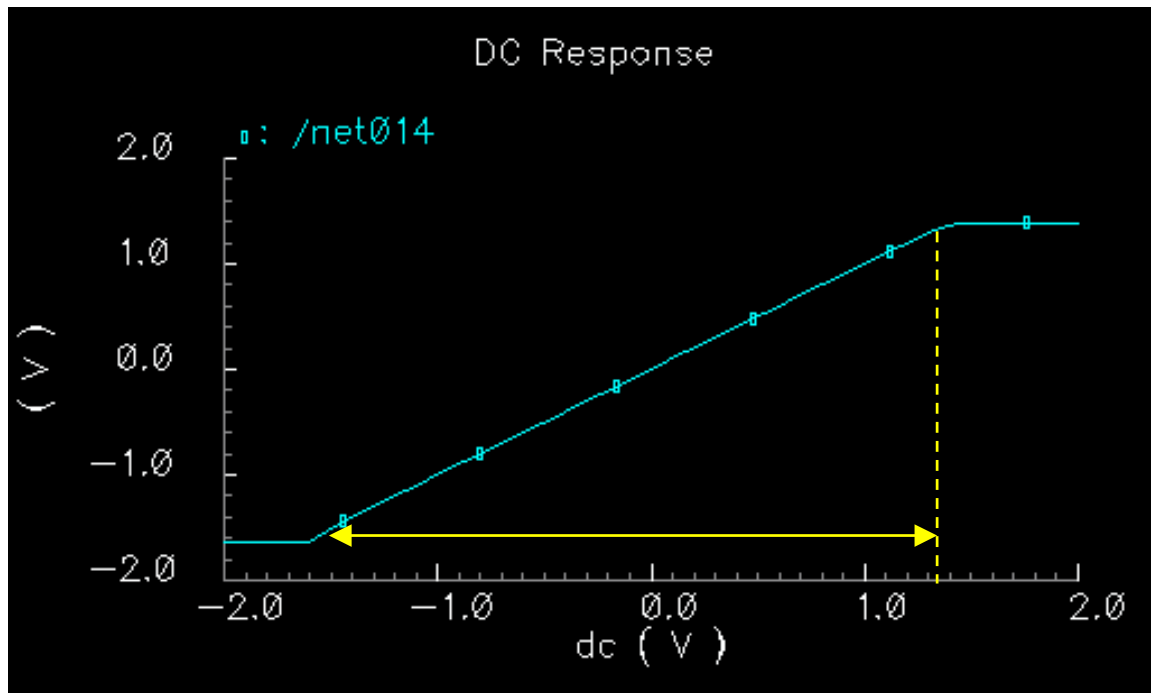


Output Swing

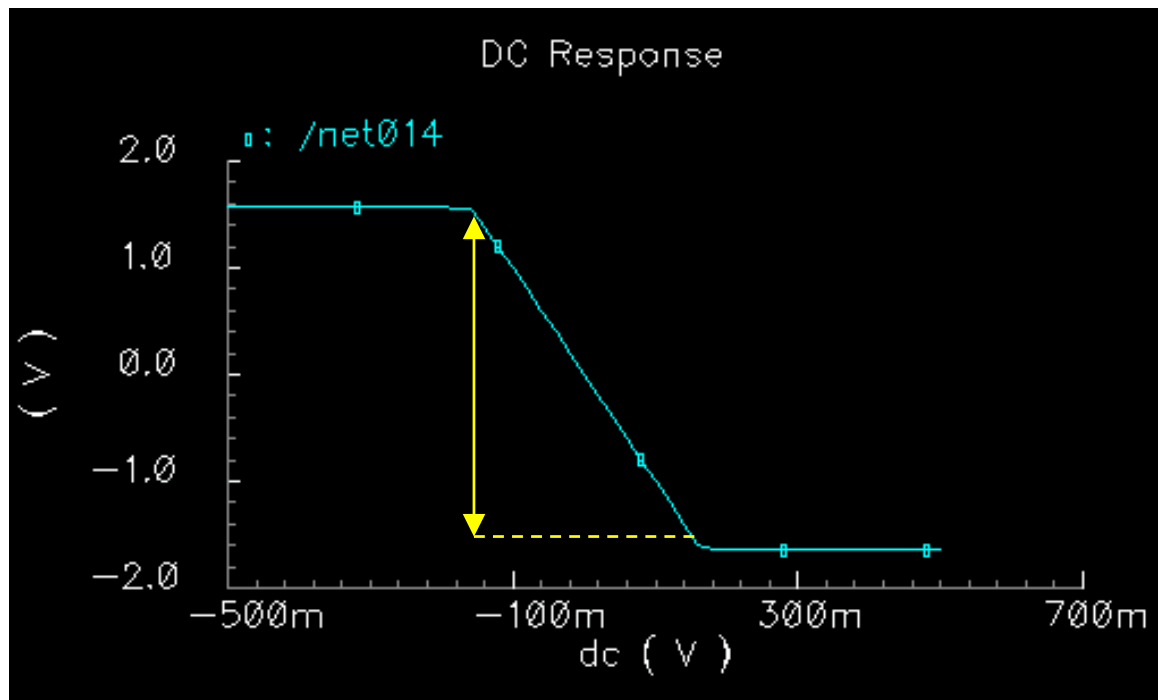


Settling Time

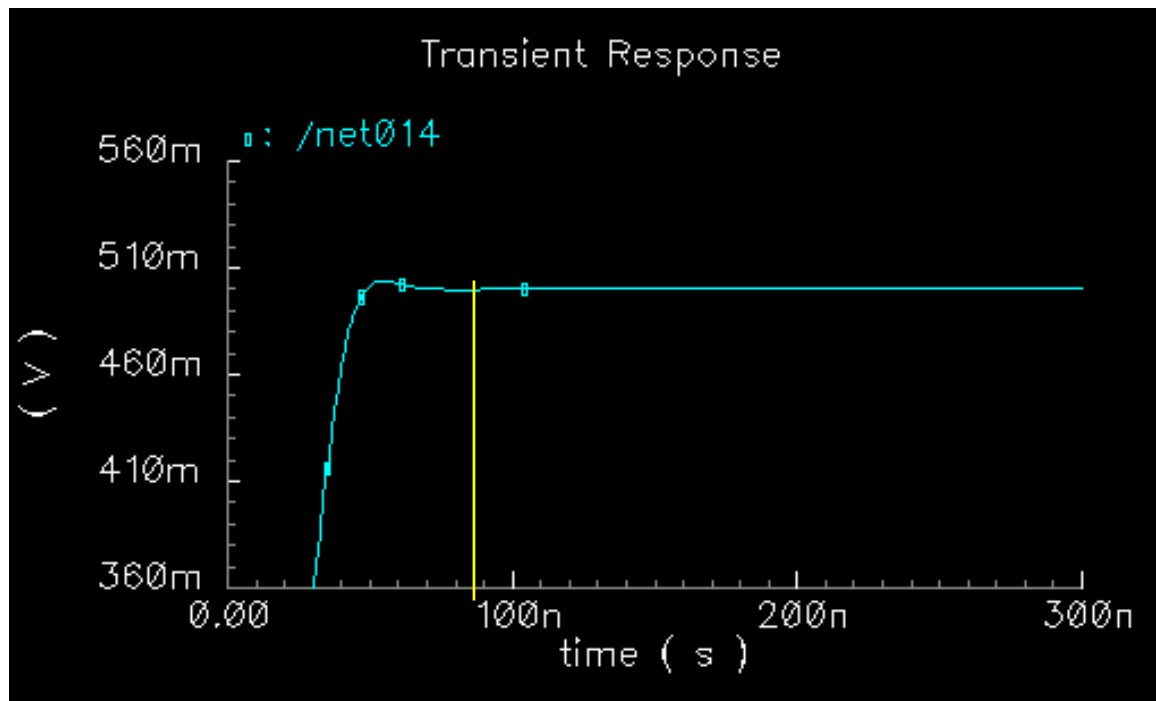

Slew Rate

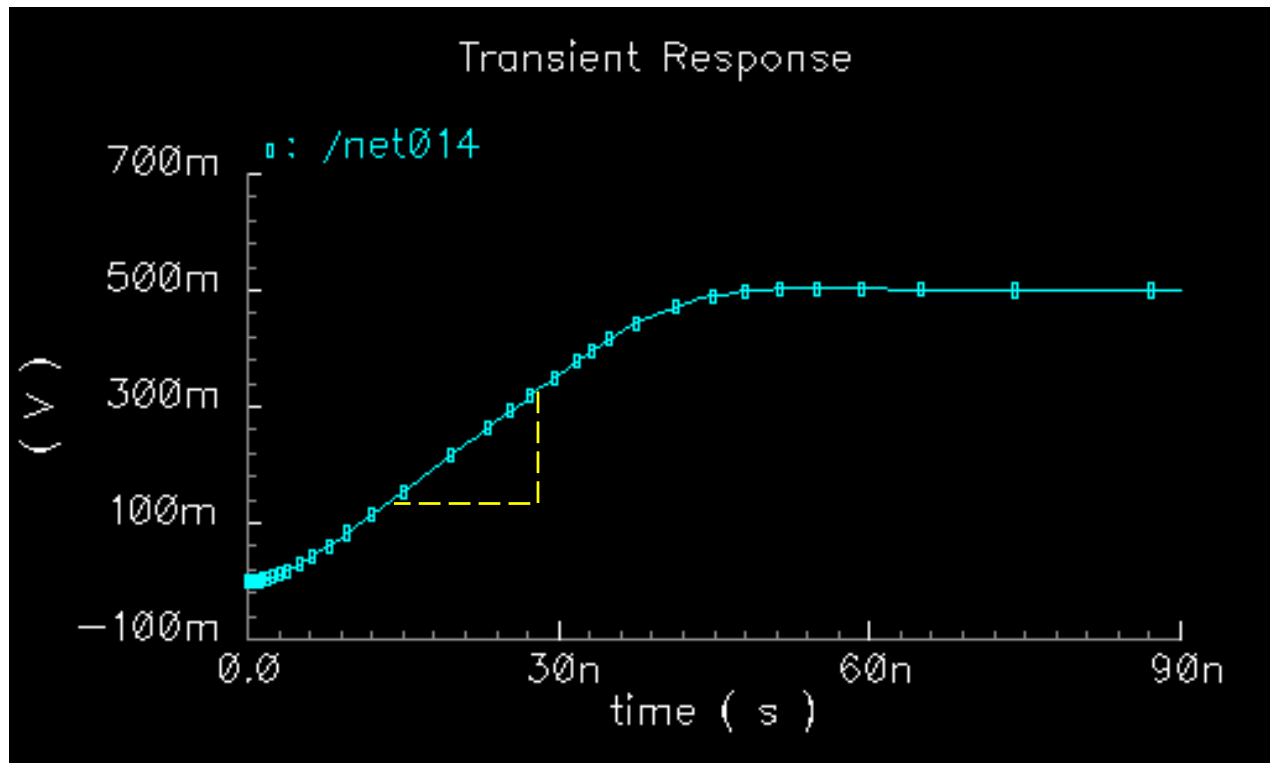

Power dissipation

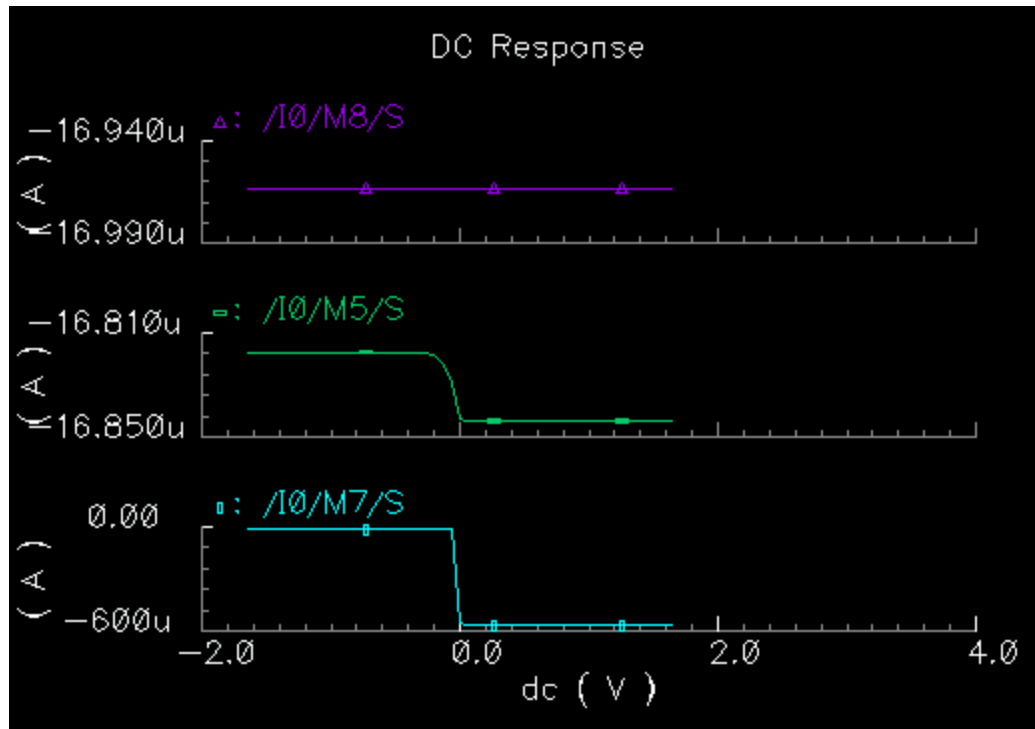


$$P_{diss} = 3.3V \cdot I_{diss}$$


Integration of scalable transistors

- **Integration of two scalable transistors**
 - ⇒ *leads to poor simulation results*
 - ⇒ *unable to achieve requirements*
- **Integration of only one scalable transistor**
 - ⇒ *readjust values*


Circuit with scalable device

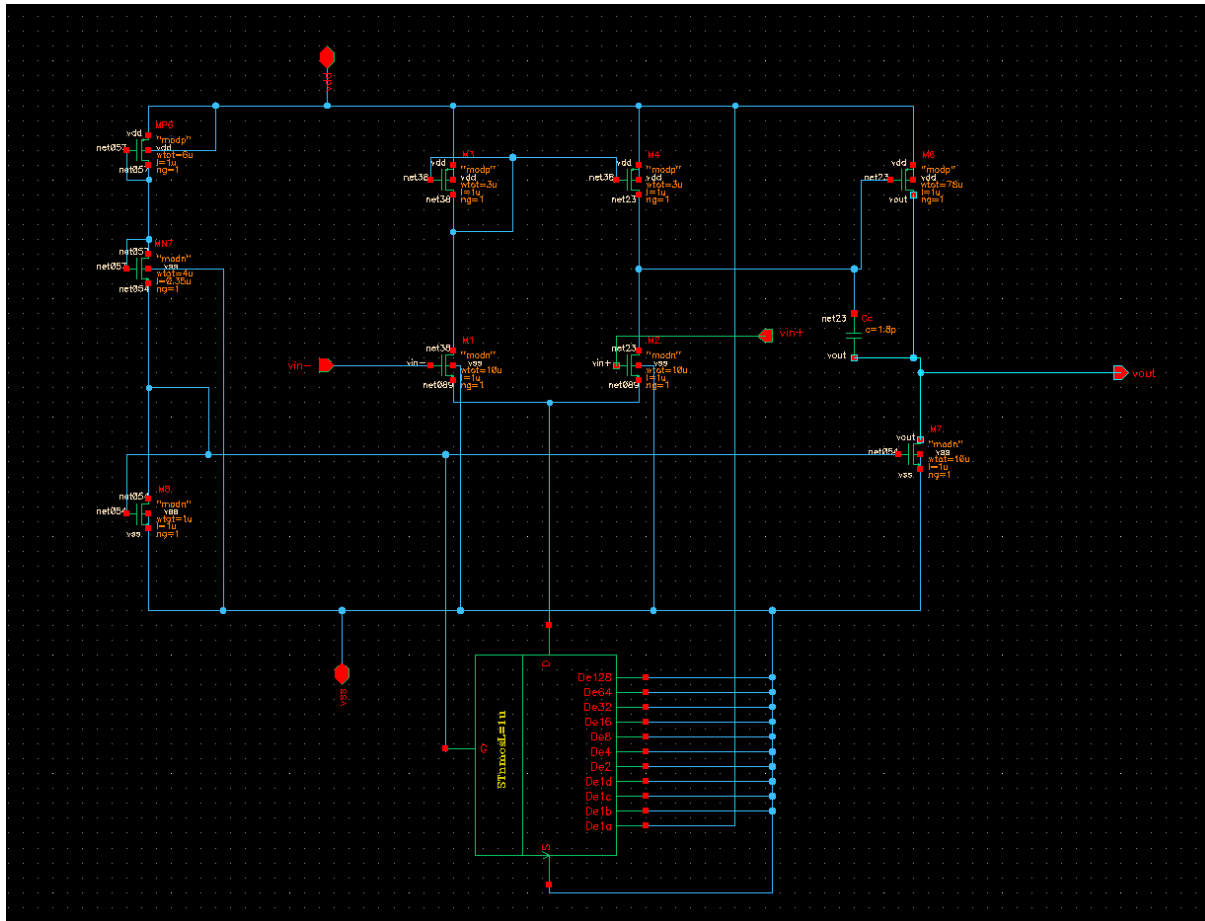


Bode plot

 

Offset

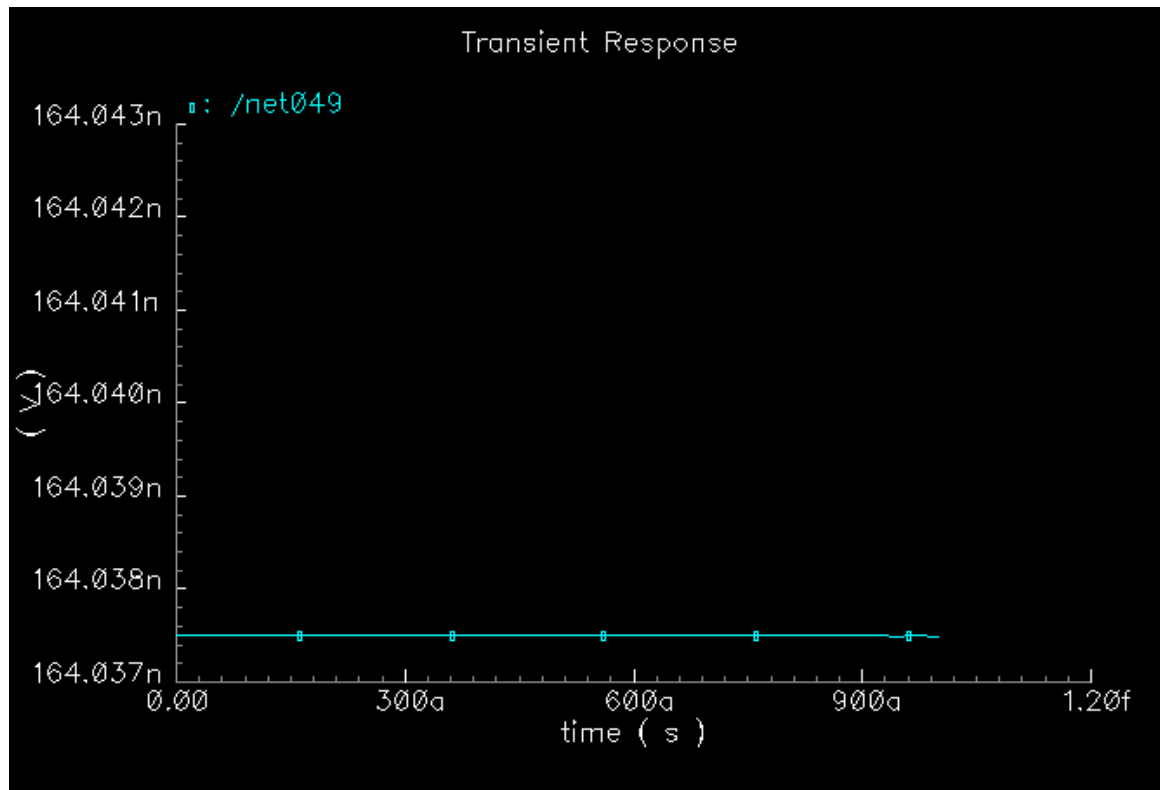


CMRR

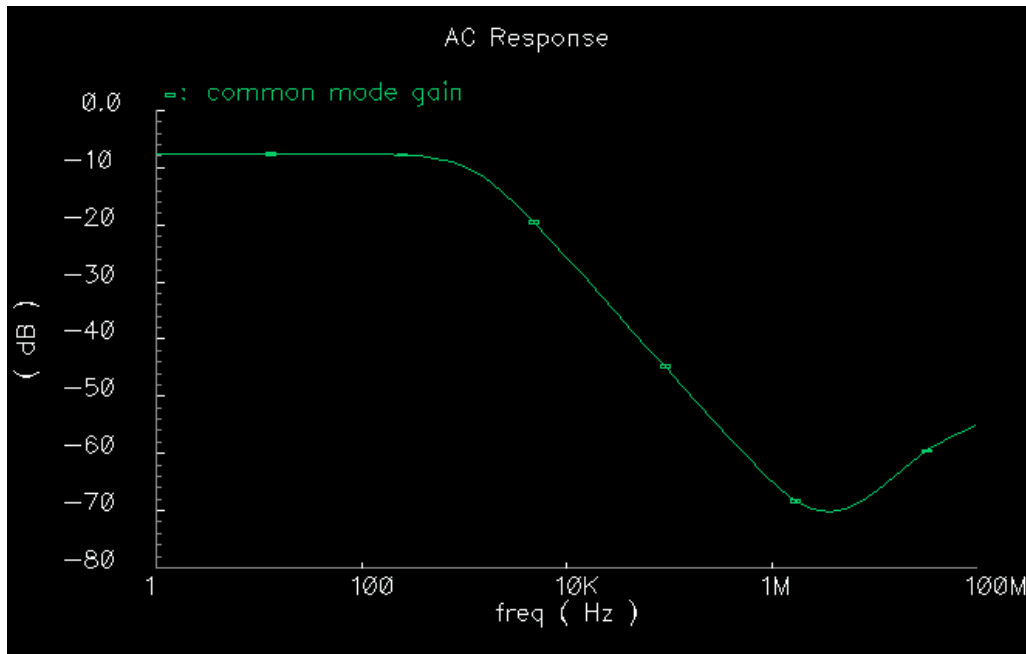


common mode gain

CMRR = (differential-mode gain) – (common-mode gain)


Input CMR

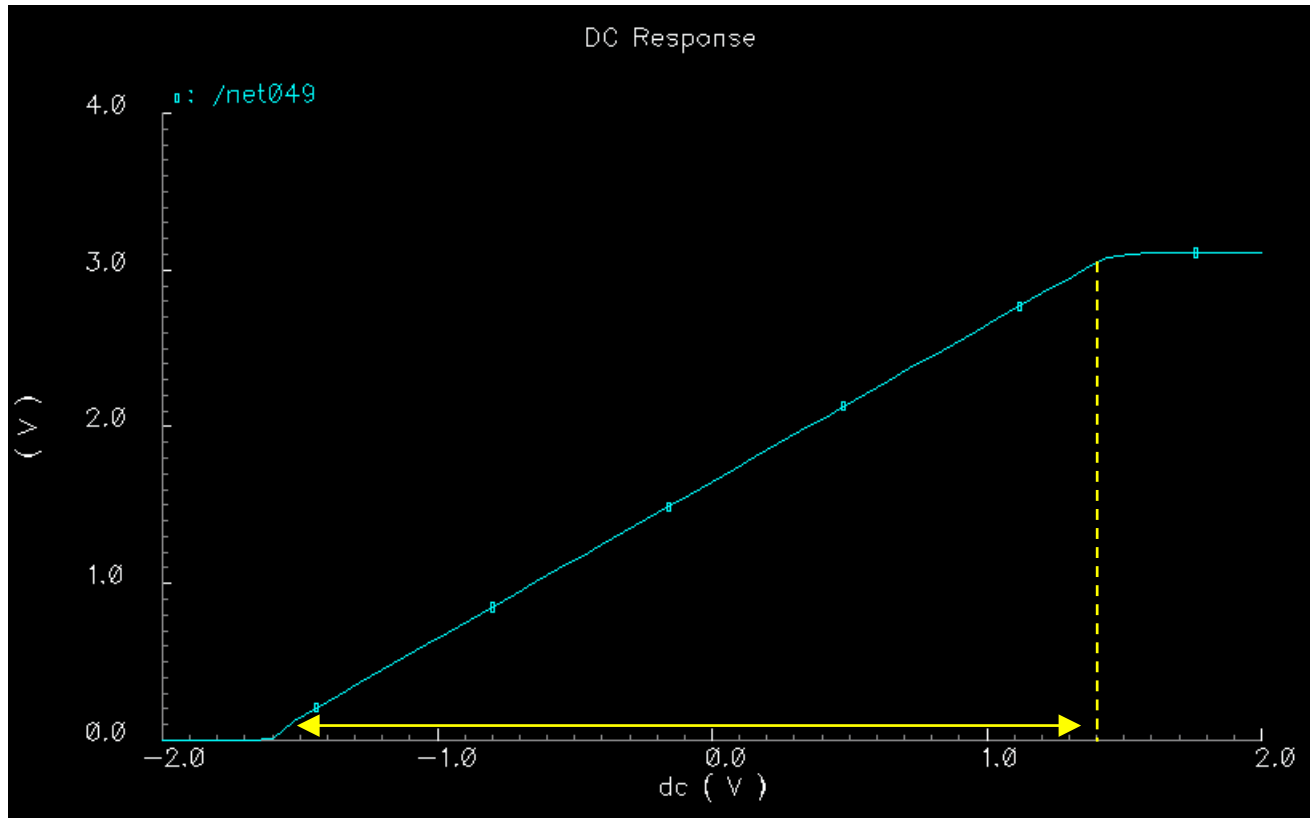


Output Swing

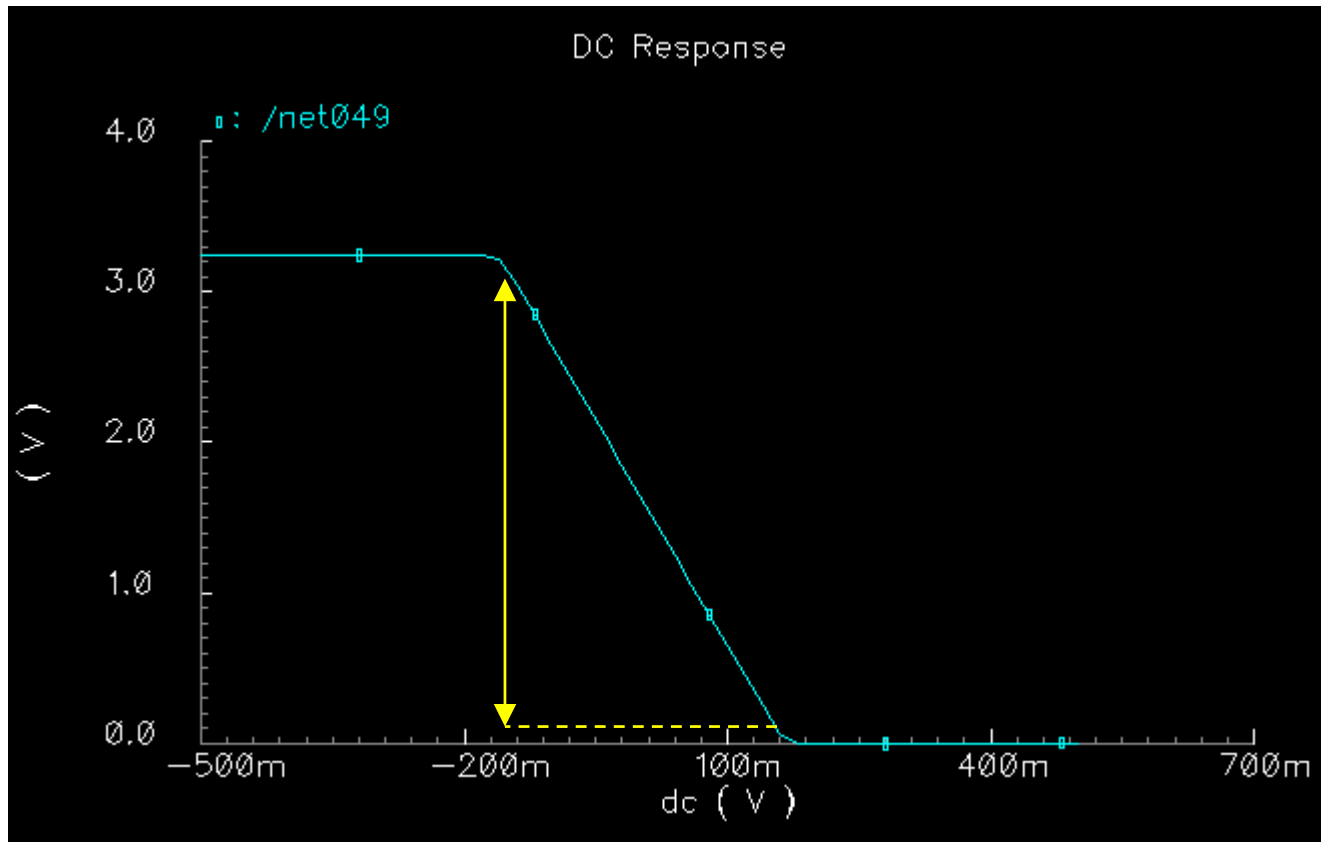


Settling Time

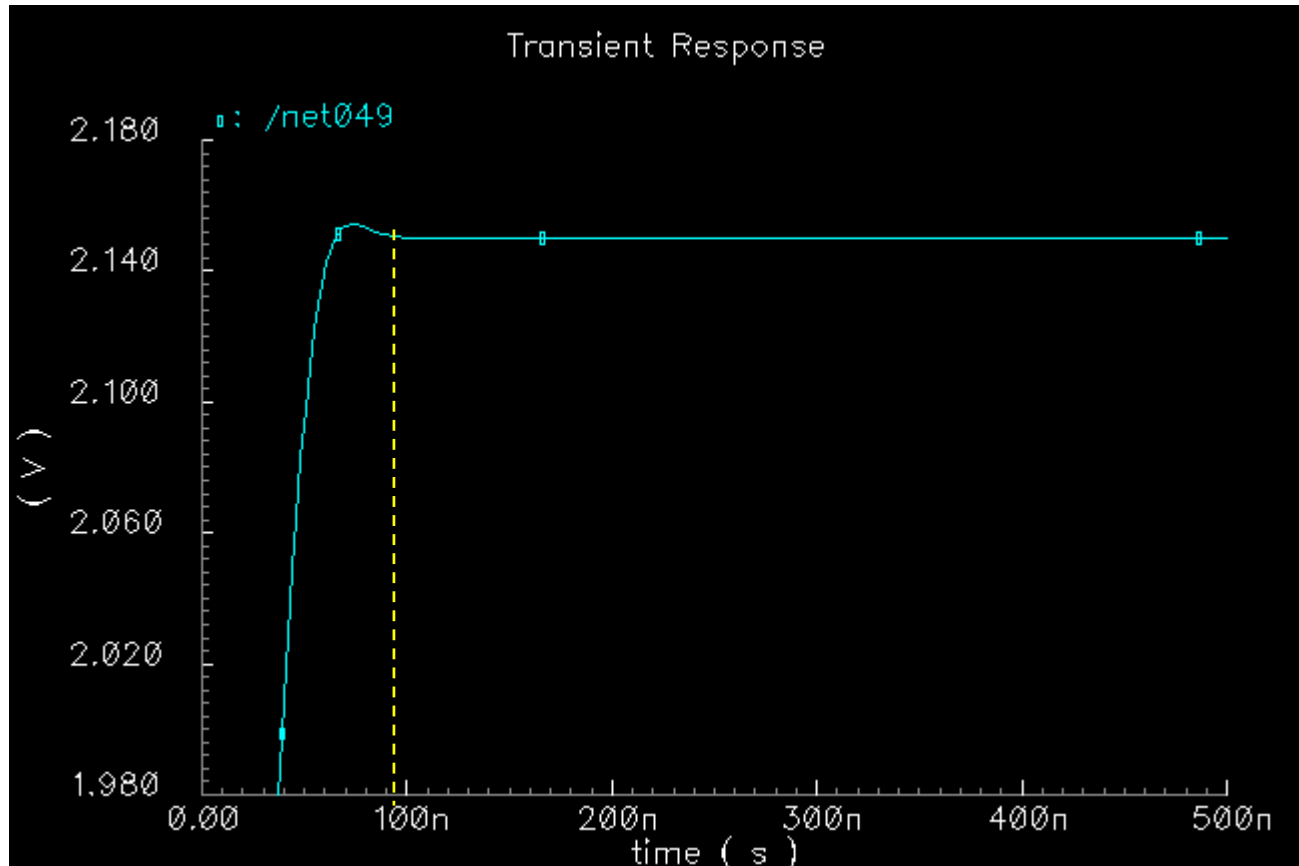

Slew Rate

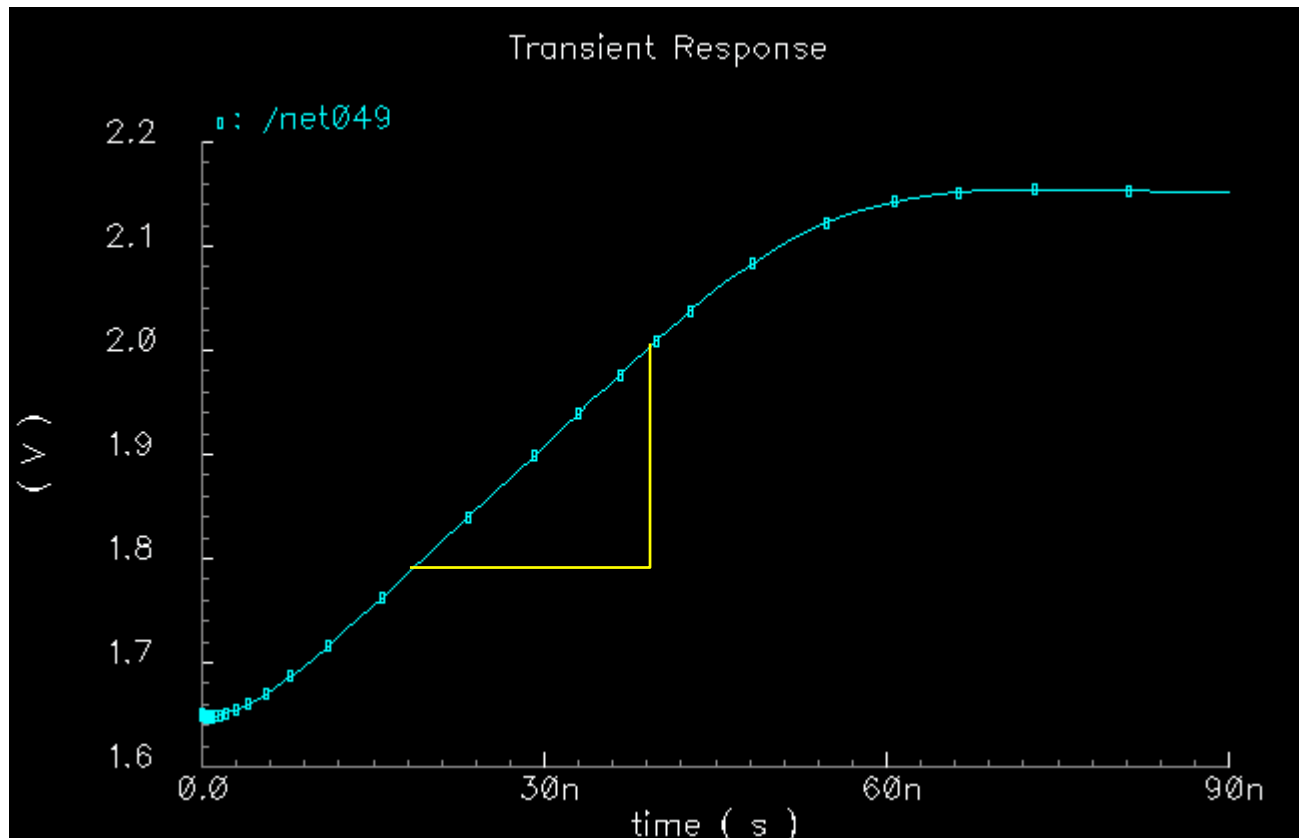


Power dissipation

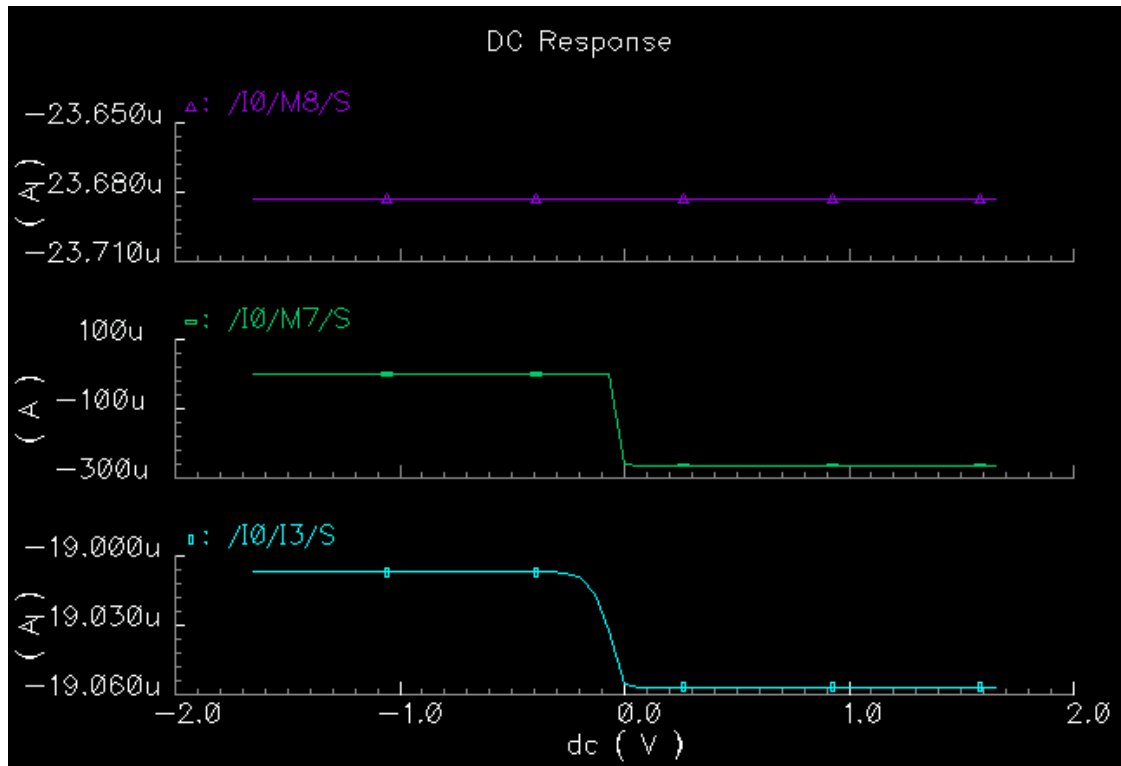


$$P_{diss} = 3.3V \cdot I_{diss}$$

Layout

 

Layout detail

 

LVS check

Running simulation in directory: "/export/users/sens4/LVS".

Loading all available p-cell functions
ROD pcell code loaded

```
Begin netlist:      Nov  7 12:06:14 2007
  view name list   = {"auLvs" "extracted" "schematic" "symbol")
  stop name list   = {"auLvs"}
  library name     = "Course_rf"
  cell name        = "opamp"-
  view name        = "extracted"
  globals lib     = "basic"
Running Artist Flat Netlisting ..2007
End netlist:      Nov  7 12:06:14 2007
```

```
Moving original netlist to extNetlist
Removing parasitic components from netlist
  presistors removed: 0
  pcapacitors removed: 0
  pinductors removed: 0
  pdiodes removed: 9
  trans lines removed: 0
  55 nodes merged into 55 nodes
```

```
Begin netlist:      Nov  7 12:06:15 2007
  view name list   = {"auLvs" "schematic" "cmos_sch" "netlist" "symbol")
  stop name list   = {"auLvs"}
  library name     = "Course_rf"
  cell name        = "opamp"-
  view name        = "schematic"
  globals lib     = "basic"
Running Artist Flat Netlisting ..2007
End netlist:      Nov  7 12:06:15 2007
```

```
Moving original netlist to extNetlist
Removing parasitic components from netlist
  presistors removed: 0
  pcapacitors removed: 0
  pinductors removed: 0
  pdiodes removed: 9
  trans lines removed: 0
  55 nodes merged into 55 nodes
```

LVS check

```
Running netlist comparison program: LVS
Begin comparison: Nov 7 12:06:15 2007
@(#)SCDS: LVS version 5.0.0 05/30/2003 19:44 (cds11939) $
Warning: Unknown device "zd2sm24" on a compareDeviceProperty command.
[....]
Warning: Unknown device "nd" on a permuteDevice command.
```

The net-lists match.


```

                                layout  schematic
                                instances
un-matched                      0          0
rewired                          0          0
size errors                      0          0
pruned                           0          0
active                          135        109
total                            135        109


                                nets
un-matched                      0          0
merged                          0          0
pruned                           0          0
active                          55         55
total                            55         55

                                terminals
un-matched                      0          0
matched but
different type                   0          0
total                            16         16
End comparison: Nov 7 12:06:15 2007
Comparison program completed successfully.
```


Bode plot

 

Offset

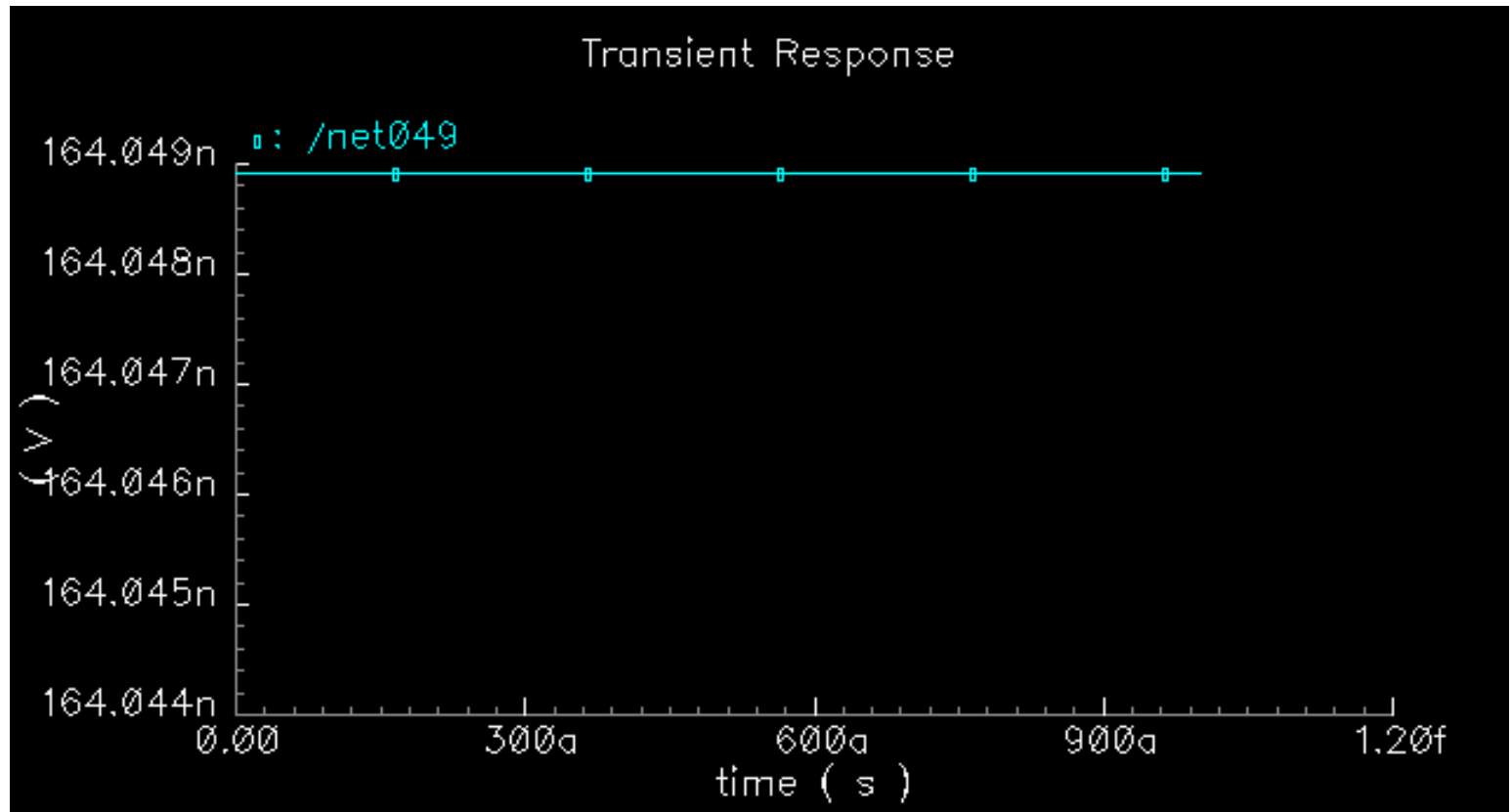


CMRR

 


common mode gain

CMRR = (differential-mode gain) – (common-mode gain)


Input CMR

 


Output Swing

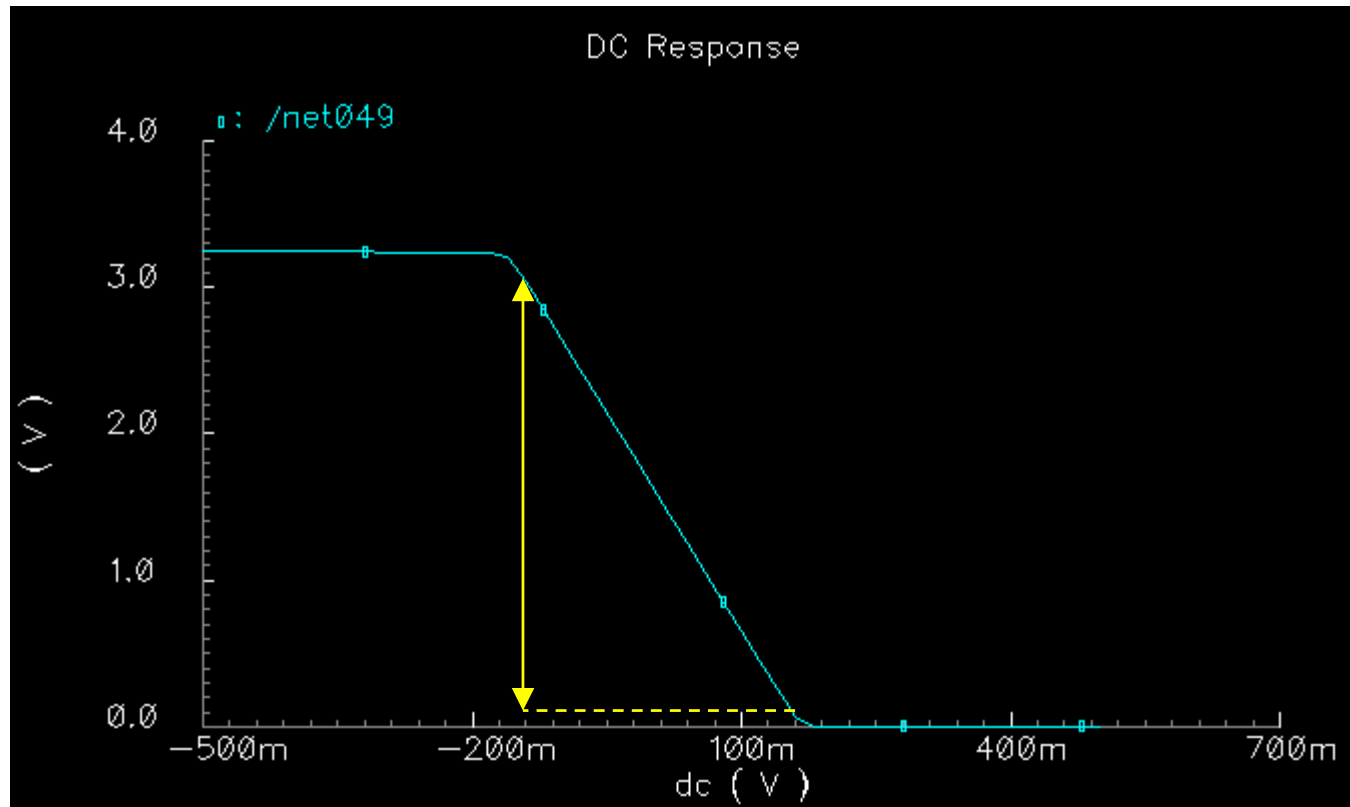


Settling Time

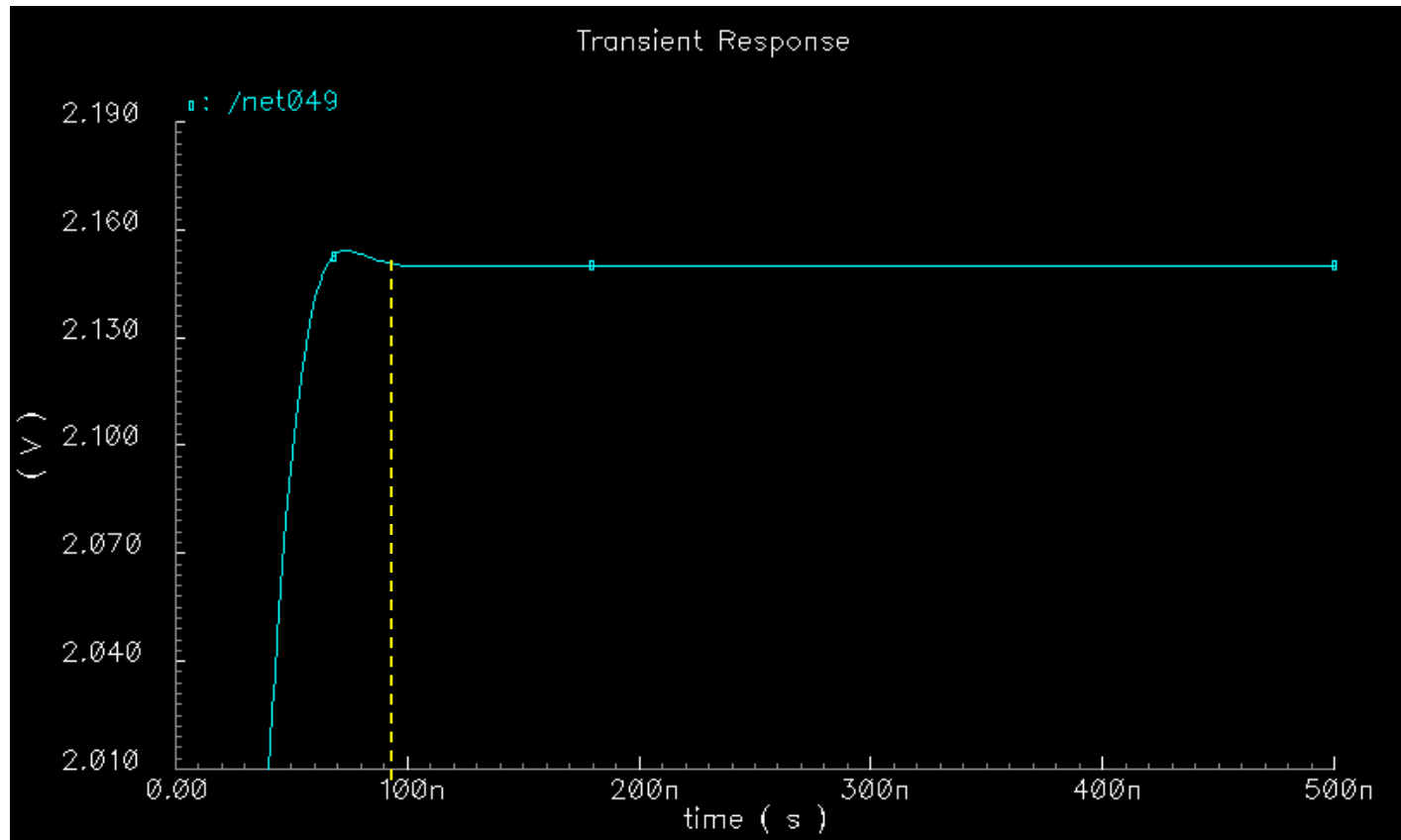

Slew Rate

 


Power dissipation

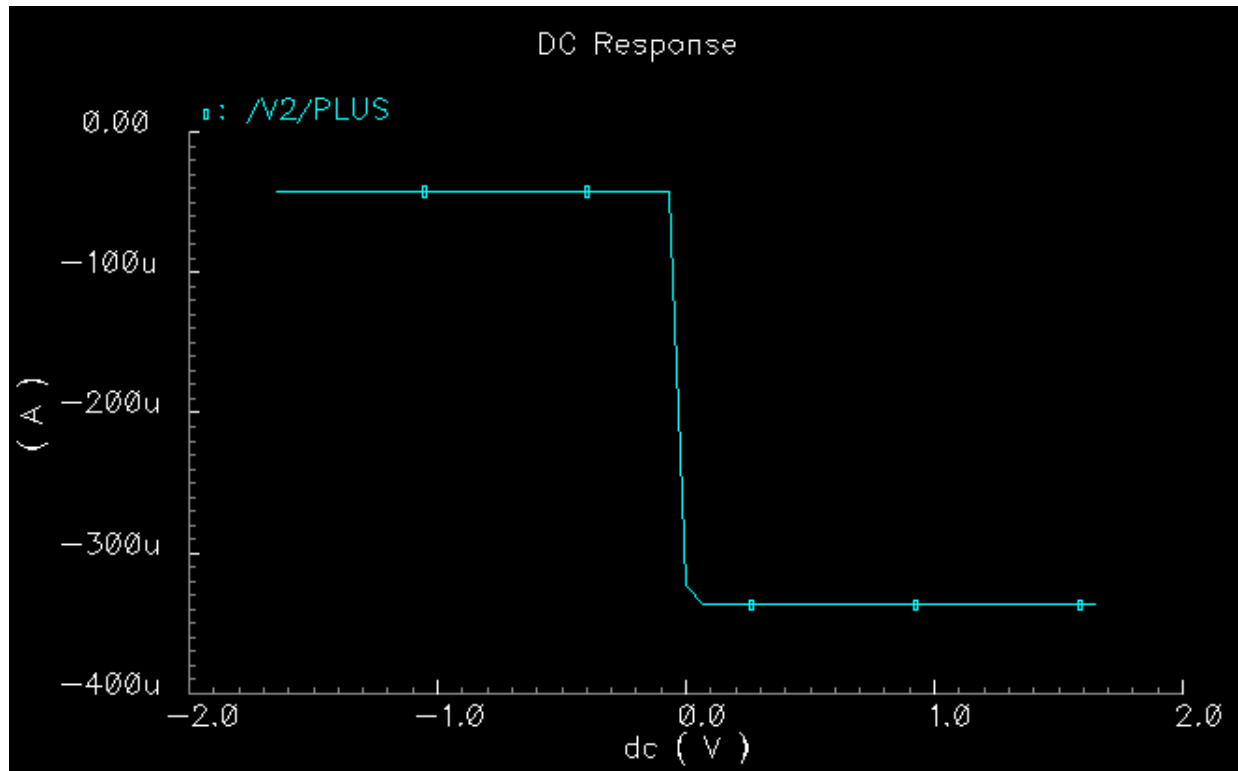


$$P_{diss} = 3.3V \cdot I_{diss}$$


Testing circuit for bode plot

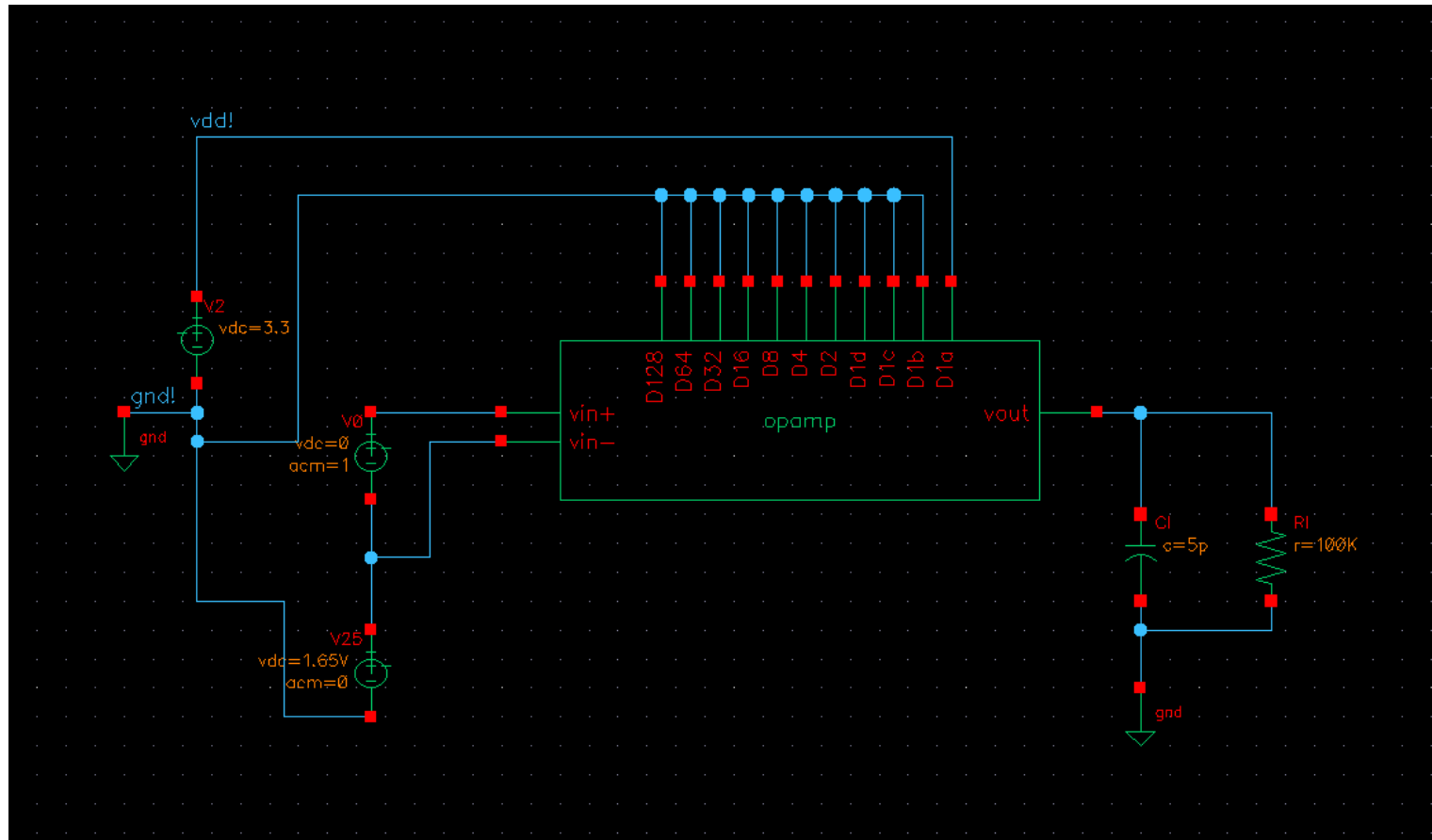

Testing circuit for offset, CMRR

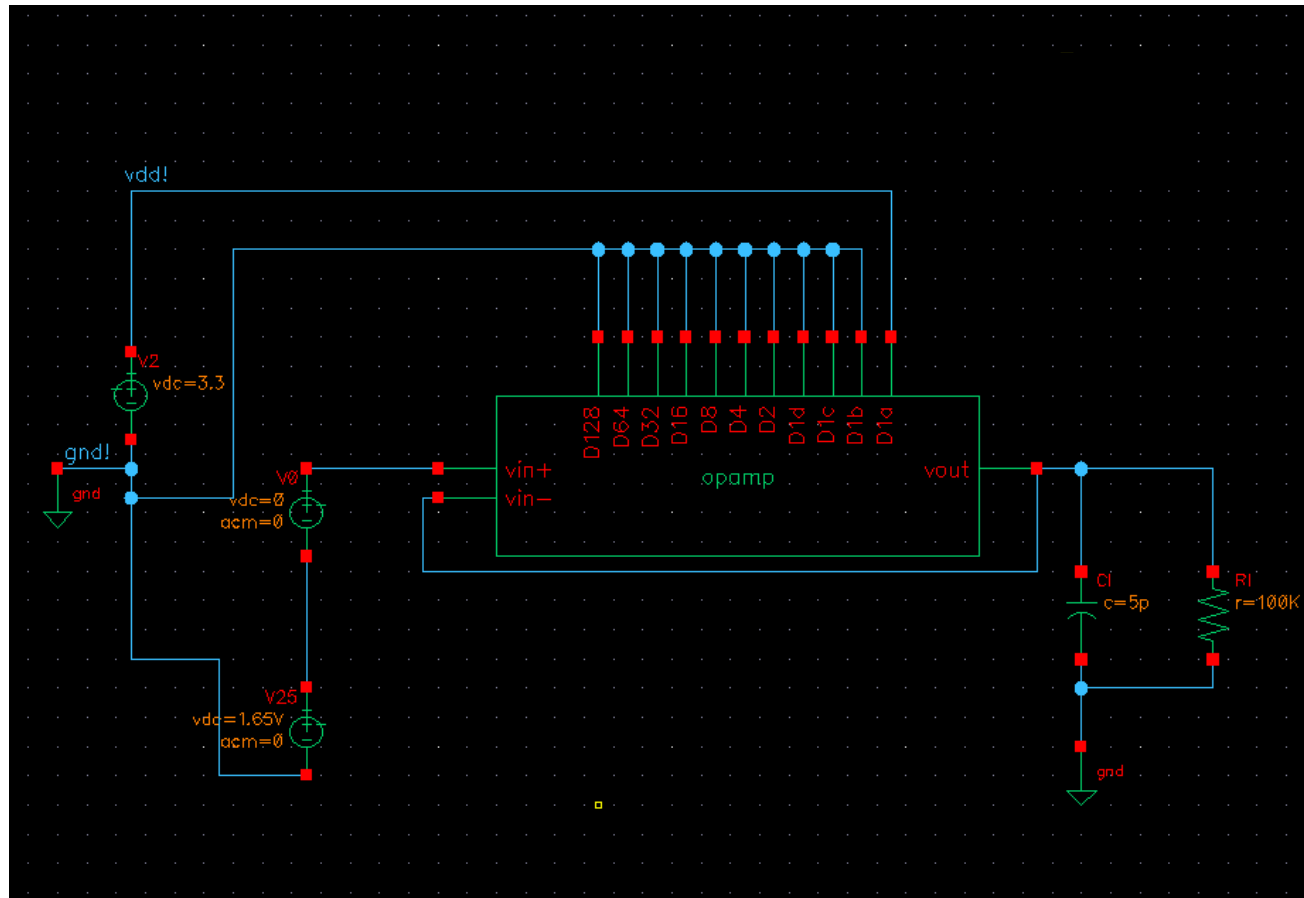

Testing circuit for output swing

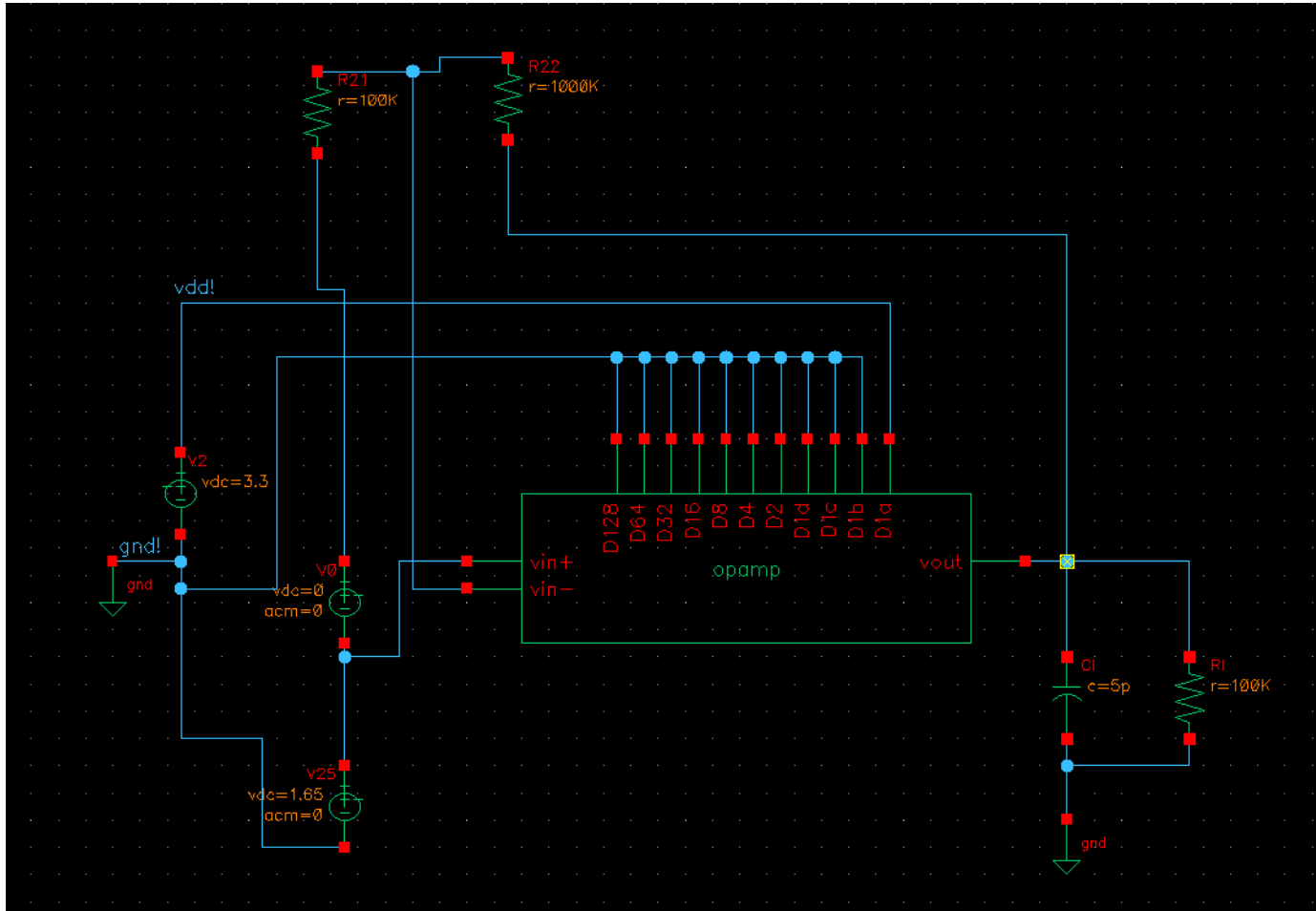

Results

	required	w/o scalable device	with scalable device	analog extracted
Open loop gain	> 75 dB	79.4 dB	79.5 dB	79.4 dB
Gain bandwidth	10 MHz	20.5 MHz	11.3 MHz	11.25 MHz
Phase margin	> 65°	65.6°	65.2°	65.4°
Settling time	< 1 μ s	< 0.1 μ s	< 0.1 μ s	< 0.1 μ s
Slew rate	1 V/ μ s	19.5 V/ μ s	10.3 V/ μ s	10.4 V/ μ s
Offset	1 μ V	4.5 μ V	0.16 μ V	0.16 μ V
Input CMR	+/- 0.5 V	-1.5 V / +1.2 V	-1.5 V / +1.4 V	-1.5 V / +1.4 V
Output Swing	+/- 0.35 V	-1.4 V / +1.6 V	-1.6 V / +1.5 V	-1.5 V / +1.5 V
CMRR	> 80 dB	87.6 dB	87 dB	87 dB
Power dissipation	< 1mW	3 mW	1.01 mW	1.1 mW