 




# InAmp with external $R_G$ and offset compensation based on Miller type OpAmp

*Aaron Speicher*  
*August, 2023*

Supervisor  
Prof. Dr.-Ing. Andreas König



---


# Overview

## **I. Miller OpAmp**

- 1. Schematic and minimum specifications**
- 2. Schematic simulation and parameter adjustments**
- 3. Layout design**
- 4. Post layout simulation**

## **II. InAmp**

 
- 1. Layout design**
- 2. Post layout simulation**




# Miller OpAmp

## Schematic and minimum requirements

### Schematic

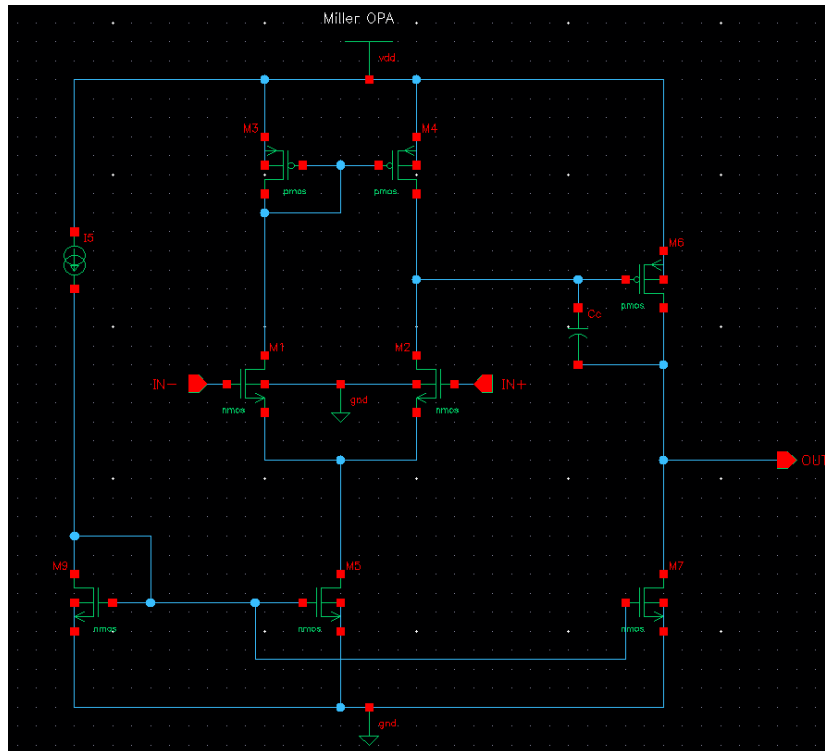

 - Stage 1: differential amplifier with pmos current mirror load and single-ended output
- Stage 2: common-source amplifier with a large miller capacitor
- M5 quiescent current set by separate biasing circuit
- Miller compensation capacitor improves stability at the cost of bandwidth




# Miller OpAmp

## Schematic and minimum requirements

### Minimum requirements


Open Loop Gain	80 dB
Gain Bandwidth	1 MHz
Phase Margin	60°
Common Mode Range +	0.75 V
Common Mode Range -	-0.75 V
Settling Time	< 1 $\mu$ s
Slew Rate	1 V/ $\mu$ s
Offset	minimum
CMRR	80 dB
Power Dissipation	minimum
Load Capacitance	10 pF

 - Minimum requirements for acceptable performance
- Miller OpAmp used to design InAmp in later stage of the project
  - Higher Open Loop Gain, Slew Rate and Settling time than minimum specification further improve InAmp performance



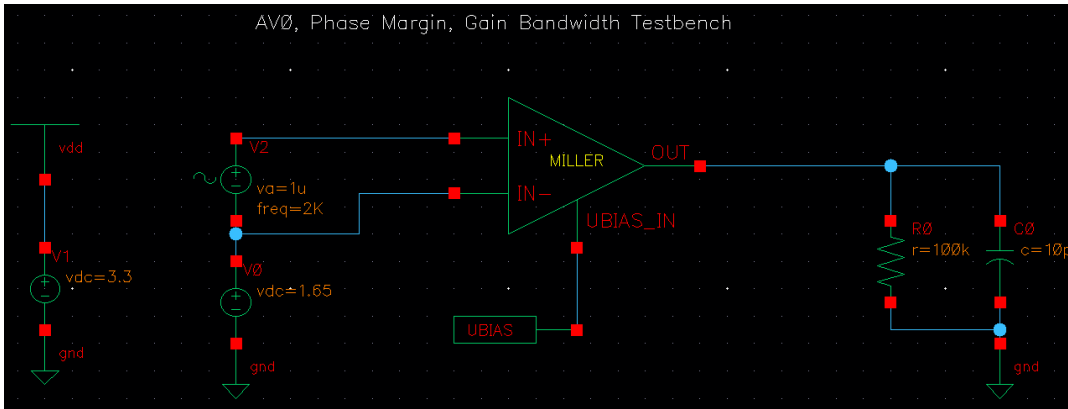
# Miller OpAmp Simulation schematics


AV<sub>0</sub>, Phase Margin, Gain Bandwidth Testbench





ICMR, Offset Testbench

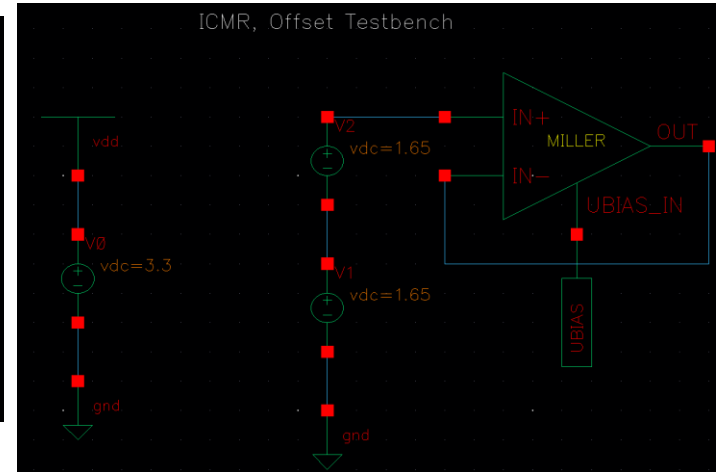

CMRR Testbench

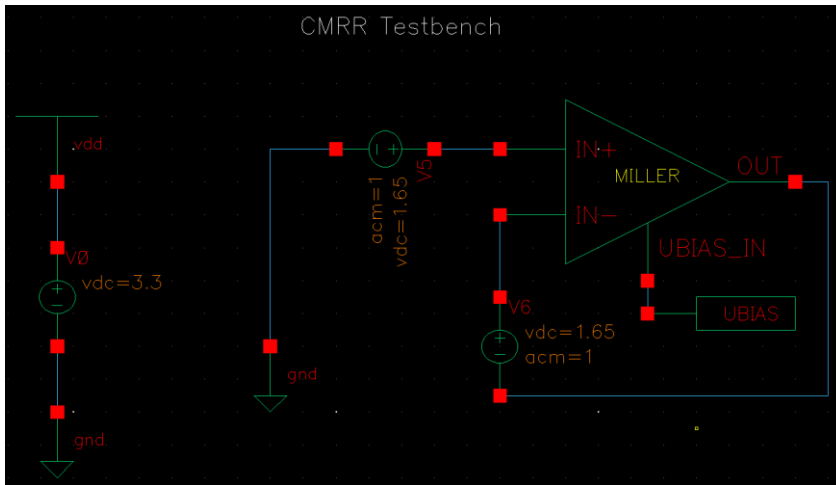

Slew Rate Testbench

 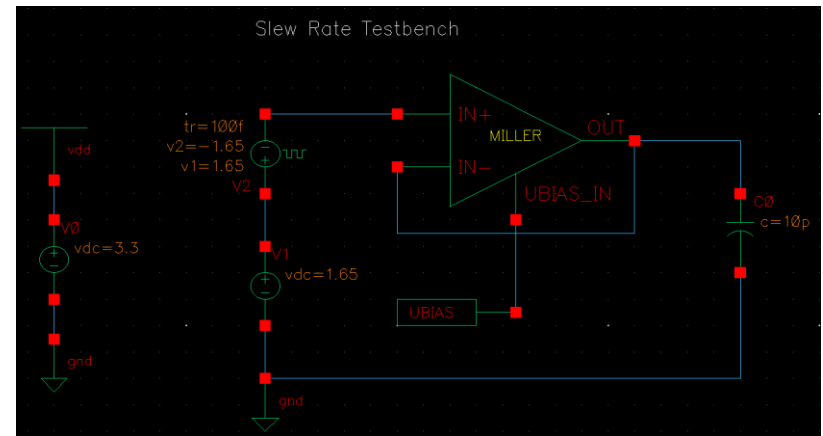

## Miller OpAmp

# Schematic simulation and parameter adjustments

Implementing the before calculated design parameters in the schematic and running all simulations resulted in the following specification:

Open Loop Gain	77 dB
Gain Bandwidth	976 kHz
Phase Margin	73°
Common Mode Range +	1.52 V
Common Mode Range -	-1.30 V
Settling Time	0.77 $\mu$ s
Slew Rate	1 V/ $\mu$ s
Offset	80 $\mu$ V
CMRR	86.64 dB

- Open Loop Gain and Gain Bandwidth below minimum spec, high Offset
- Excessive Phase Margin
- Slew Rate and Common Mode Rejection Ratio match minimum spec but improvement for better InAmp performance useful




# Schematic simulation and parameter adjustments

## Design Approach to improve simulation results

- Hand model transistor equations give hint on the effect of certain design parameters
- Simulator uses much more complex transistor models
  - Impact of certain parameters might differ from expectation
 
## Solution

- Combine hand model transistor equations with iterative circuit simulation and manual refinement based on experience with the circuit




# Miller OpAmp

## Schematic simulation and parameter adjustments

### Design route

Design change	Specification after Allen/Holberg	Cc -> 1.8pF	I5 -> 4	I5 -> 10	S6, S7 -> 30	S1, S2 -> 2	S1, S2 -> 3	S7 -> 35	S6 -> 31	Final simulation	
											Cc -> 1.6
Open Loop Gain in dB	77	*	78	77	79	82	83	-	-	81.6	
Gain Bandwidth in MHz	0.976	1.15	1.65	2.67	2.80	3.8	4.6	-	-	4.6	-
Phasemargin in °	73	71	69	66	72	66	62	-	-	63	5.05
Common Mode Range - in V	1.52	-	-	-1.3	-	-	*	-	-	*	60.7
Common Mode Range + in V	-1.30	-	-	1.3	-	-	*	-	-	1.22	-
Settling Time in µs	0.77	-	-	-	-	-	-	-	-	-	-
Slew Rate in µs	1	1.22	2.19	4.2	5.3	5.4	*	-	-	*	6.07
Common Mode Rejection Ratio in dB	86.64	-	-	82	*	91	100	-	-	99.83	-
Offset in µV	80	-	-	-	-	-	90	35	7.21	*	-
											-
S1, S2	1	*	*	*	*	2	3	*	*	*	
S3, S4	1	*	*	*	*	*	*	*	*	*	*
S6	20	*	*	*	30	*	*	*	31	*	*
S7	20	*	*	*	30	*	*	35	*	*	*
S5	2	*	*	*	*	*	*	*	*	*	*
I5 in µA	2.21	*	4	10	*	*	*	*	*	*	*
Cc in µF	2.21	1.8	*	*	*	*	*	*	*	*	1.6

 




# Miller OpAmp

## Schematic simulation and parameter adjustments

	Specification after Allen/Holberg	Design Result	Cc -> 1.6pF ?
Open Loop Gain in dB	77	81.6	81.6
Gain Bandwidth in MHz	0.976	4.59	5.05
Phasemargin in °	73	63°	60.7
Common Mode Range - in V	1.52	1.22	1.22
Common Mode Range + in V	-1.30	-1.3	-1.3
Settling Time in µs	0.77	0.21	0.22
Slew Rate in µs	1	5.42	6.07
Common Mode Rejection Ratio in dB	86.64	99.83	99.83
Offset in µV	80	7.22	7.22
S1, S2	1	3	3
S3, S4	1	1	1
S6	20	31	31
S7	20	35	35
S5	2	2	2
I5 in µA	2.21	10	10
Cc in µF	2.21	1.8	1.6

 
Further improvement but high chance of Phase Margin requirement not being met after layout and extract, Cc kept at 1.8pF



---

 
## Miller OpAmp Layout design

- Transistors must be designed to achieve acceptable W/L ratio in the complete layout
  - Folded layout for M6 and M7
  - Folded layout not necessary for M1 and M2 but would result in better matching, less parasitics
- Arranging the transistors to form a close to perfect square not necessary
  - Fill out space with large Miller capacitor to achieve desired chip level W/L ratio




# Miller OpAmp Layout design

## Layout without $C_c$

 


 - Arrangement should not have too many corners
- Minimize area by using minimum design rules



## Layout with Cc

# Miller OpAmp Layout design

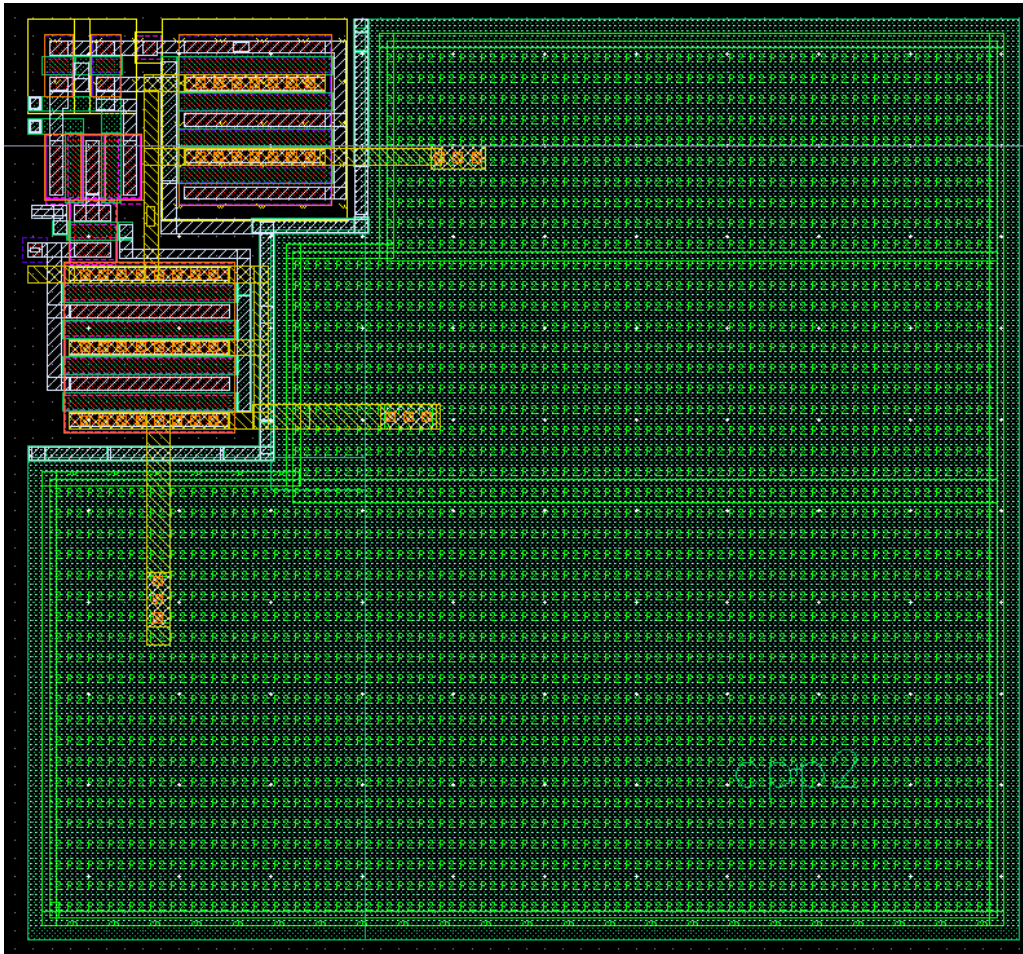

### Run: "MILLER\_LVS" (auf Iseserver002)

Run: "MILLER\_LVS" from  
/home/tl23\_speicher/AssuraLVS

Schematic and Layout Match.  
You currently have an open run (project).

Do you want to close current project and view the results of new run?

Summary of LVS Issues

Extraction Information:

0 cells have 0 mal-formed device problems  
0 cells have 0 label short problems  
0 cells have 0 label open problems

Comparison Information:

0 cells have 0 Net mismatches  
0 cells have 0 Device mismatches  
0 cells have 0 Pin mismatches  
0 cells have 0 Parameter mismatches

ELW Information:


Total DRC violations: 0

### Quantus Run (auf Iseserver002)

The Quantus run "MILLER\_LVS" completed successfully  
The output is in :

Library: TESYS\_PROJECT\_AS  
Cell: MILLER  
View: analog\_extracted


Close

 

# Miller OpAmp

## Post layout simulation



	Specification after Allen/Holberg	Design Result	Post Layout
Open Loop Gain in dB	77	81.6	79.4
Gain Bandwidth in MHz	0.976	4.59	4.40
Phasemargin in °	73	63°	60
Common Mode Range - in V	1.52	1.22	1.22
Common Mode Range + in V	-1.30	-1.3	-1.3
Settling Time in $\mu$ s	0.77	0.21	0.22
Slew Rate in V/ $\mu$ s	1	5.51	5.46
Common Mode Rejection Ratio in dB	86.64	99.83	99.35
Offset in $\mu$ V	80	7.22	13.83
S1, S2	1	3	3
S3, S4	1	1	1
S6	20	31	31
S7	20	35	35
S5	2	2	2
I5 in $\mu$ A	2.21	10	10
Cc in $\mu$ F	2.21	1.6	1.6

 

# Miller OpAmp

## Post layout simulation
  
### Open Loop Gain, Gain Bandwidth, Phase Margin







# Miller OpAmp

## Post layout simulation



### Common Mode Rejection Ratio

  

# Miller OpAmp

## Post layout simulation



### Input Common Mode Range, Offset

 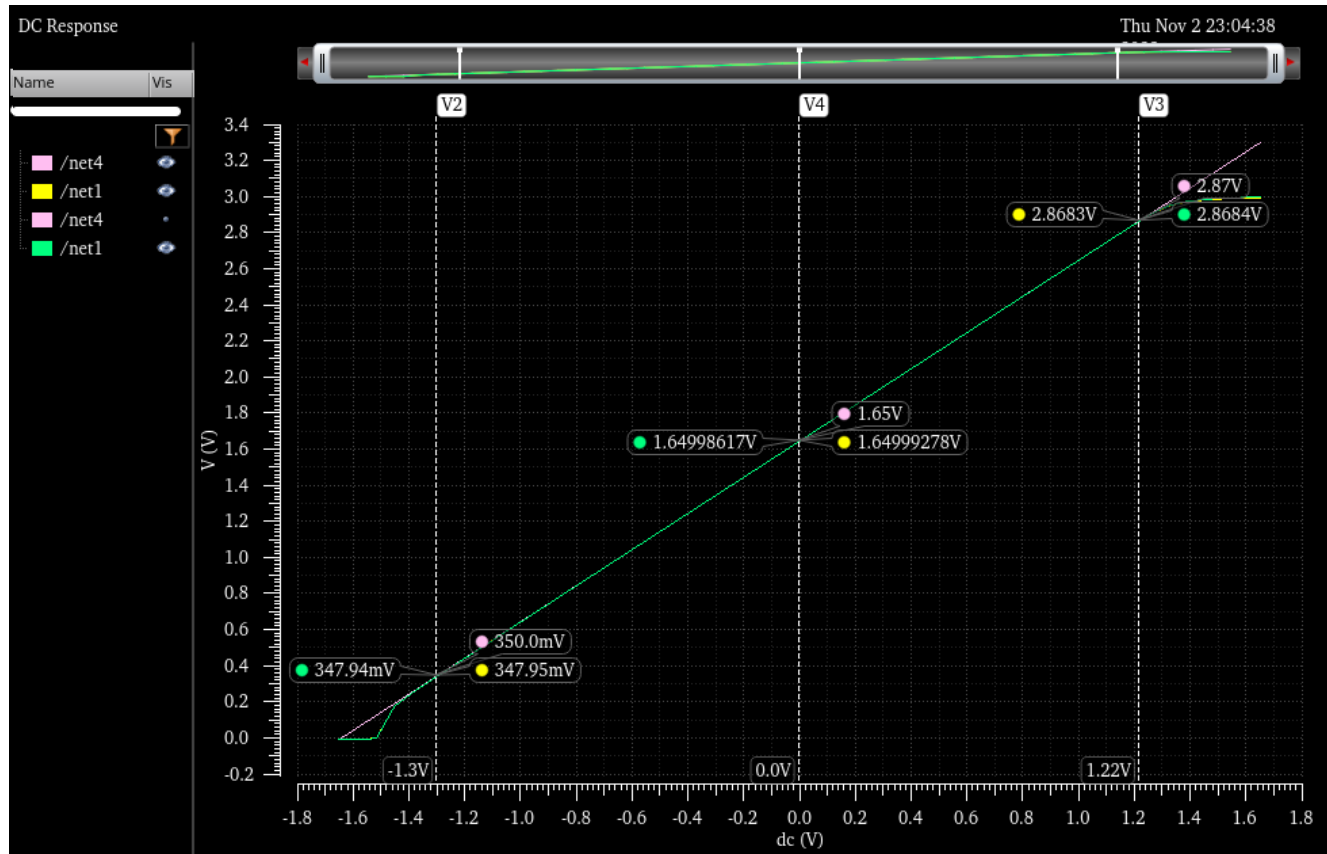




# Miller OpAmp Post layout simulation

## Slew Rate

  

# InAmp Layout design

 

- Find optimal arrangement for short signal paths
- Minimize area by using minimum design rules

Run: "InAmp\_LVS" (auf iseserver002)

Run: "InAmp\_LVS" from  
/home/tl23\_speicher/AssuraLVS

Schematic and Layout Match.  
You currently have an open run (project).

Do you want to close current project and view the results of new run?

Summary of LVS Issues

Extraction Information:

- 0 cells have 0 mal-formed device problems
- 0 cells have 0 label short problems
- 0 cells have 0 label open problems

Comparison Information:

- 0 cells have 0 Net mismatches
- 0 cells have 0 Device mismatches
- 0 cells have 0 Pin mismatches
- 0 cells have 0 Parameter mismatches

ELW Information:

Total DRC violations: 0


Quantus Run (auf iseserver002)

The Quantus run "InAmp\_LVS" completed successfully  
The output is in :



Library: TESYS\_PROJECT\_AS  
Cell: InAmp  
View: analog\_extracted

Close

Yes No Help

 


# InAmp Layout design

 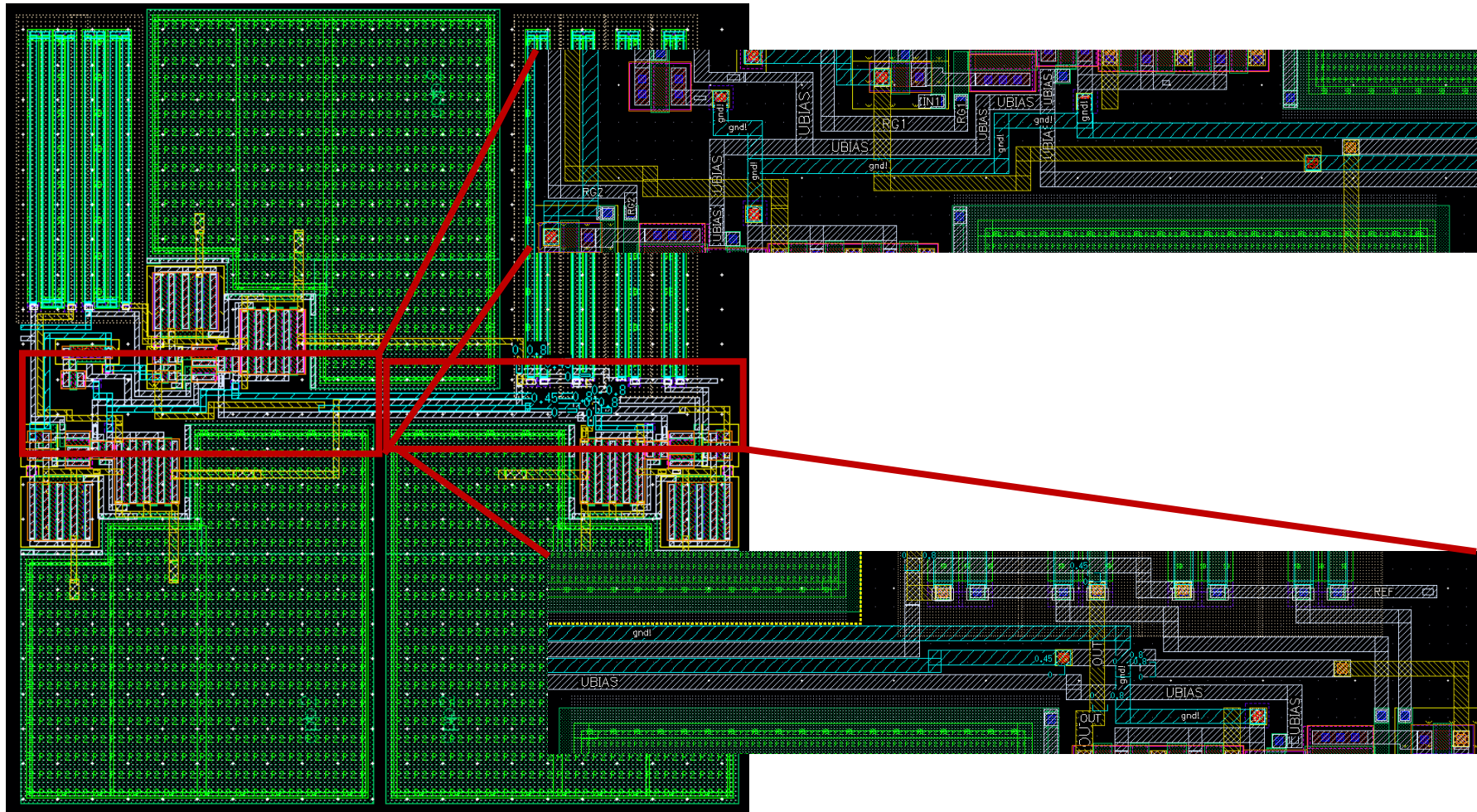






# InAmp Layout design

 




 
Current biasing circuit based on two diode connected transistors (one for all three OpAmps)



# InAmp Layout design

  


# InAmp Simulation schematics

 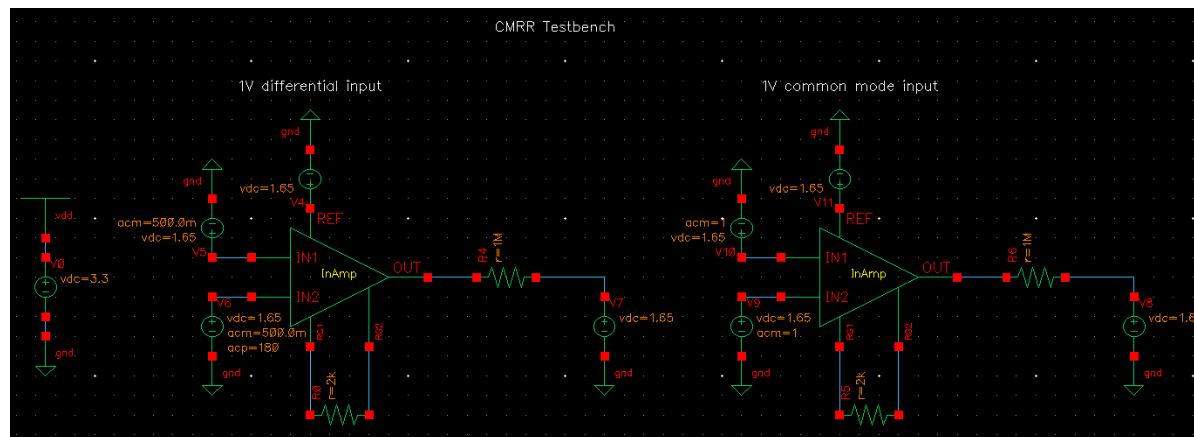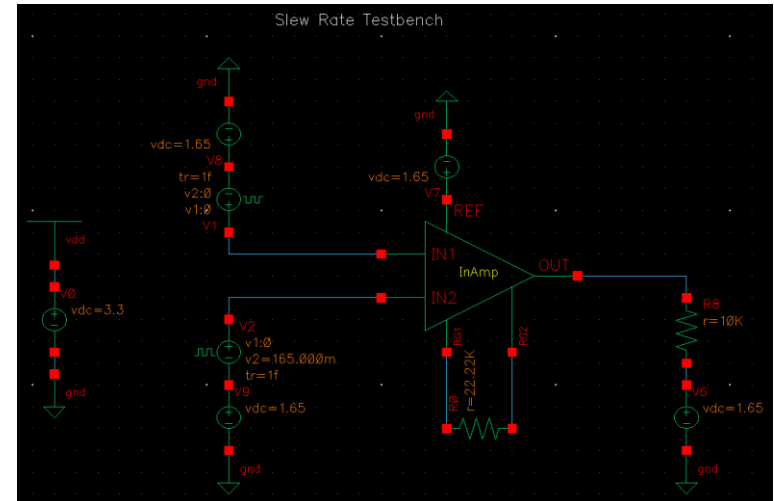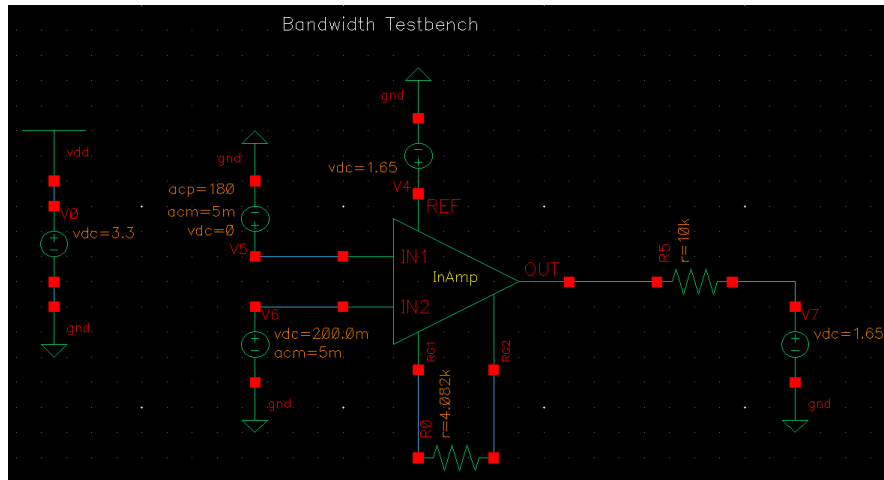

# InAmp



## Post layout simulation and comparison to commercial InAmp

	Design Result	Post Layout (ideal connections)	Post Layout	INA350
Output Resistance	7.88	8.12	6.78	-
Slew Rate in V/ $\mu$ s	1.97	1.93	1.92	0.24
Common Mode Rejection Ratio in dB	122	121.8	126.5	95
Bandwidth in kHz, G=10	473	467	467	100
Bandwidth in kHz, G=50	98.03	96.67	96.57	25
Gain Error in % G=10	0.095	0.095	0.105	0.05
Gain Error in % G=50	0.19	0.2	0.22	0.082

 

# InAmp Post layout simulation

Bandwidth  $G=50$

 
 




# InAmp

## Post layout simulation

### Common Mode Rejection Ratio

  

---


# Conclusion

- Miller type OpAmp reaches minimum specification, especially Phase Margin (after layout and extract)
- Successful design of current biasing circuit
- Final InAmp design outperforms commercially available INA350 (after layout and extract)
- Square footprint of final InAmp layout
- Possible improvements:
  - Matched resistors in InAmp layout



---

Thank You for your attention!

 

---

# References

- Lecture and lab material of Elektronik II subject by Prof. Koenig
- Lecture and lab material of TESYS subject by Prof. Koenig

