



Semester Project in TESIS, 2022

# 3-bit Flash Analogue to Digital Converter Design and Layout in XFAB 0.35 $\mu\text{m}$ CMOS Technology'

*Amira Ghezal*

*Jad Halabi*

*Anand Joshy*

*Kamal Baghirli*

**Supervisor: Prof. Dr.-Ing. Andreas König**



# Outline


## 1. Introduction

- *Motivation*

## 2. Parts of the Project



- ✓ *Amira Ghezal* -*Chip floor-plan and top-level hierarchical layout*  
-*Comparator and Bias circuit layouts*
- ✓ *Jad Halabi* -*Matched resistor: design and layout*
- ✓ *Anand Joshy* -*Logic gates design and layout*
- ✓ *Kamal Baghirli* -*Encoder design and layout using Logic gates*

## 3. Conclusion

 

  
# Motivation

- Analog signals are often fed into the computing systems for processing.
- As the computers can only handle digital data, there is a need to convert the analog data to a digital one.
- This project designs a Flash converter, which converts one word at a time (3-bit word in this case).




# Parts of Project

## Block diagram of a 3-Bit Flash ADC

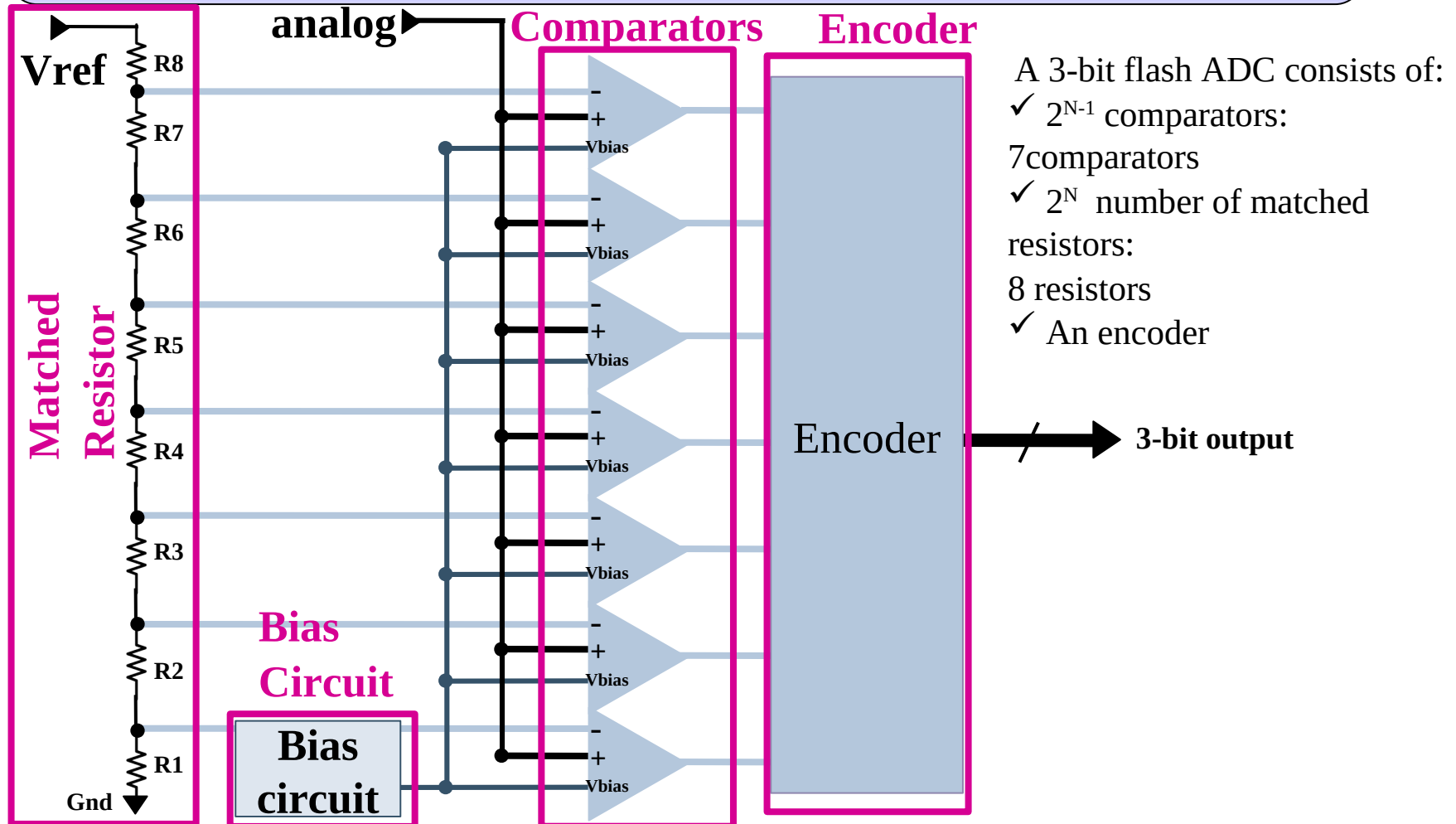


 - A 3-bit flash ADC consists of:
- ✓  $2^{N-1}$  comparators:  
7 comparators
  - ✓  $2^N$  number of matched resistors:  
8 resistors
  - ✓ An encoder



 
# 1. Matched Resistor

- Function: Provide fixed voltage levels to which an analog signal from a sensor will be compared
- Sensor output: 0~2V
- Comparator specification:  $CMR_{-/+} = 0.85$  from supply rails with  $v_{dd} = 3.3V$ , which means the comparator works dependably in the range [0.8, 2.5V]
- The sensor and comparator working range did not match
- The best solution was to go back to the comparator design and extract new parameters for transistor widths
- We decided on an adhoc solution (next slide) because of time limitations





 
# 1. Matched Resistor

- The adhoc solution was to modify the matched resistor to alter the reference voltages in a way that matches the CMR of the comparators
  - ➔ Effects the full scale voltage (FSV)
- The resistor chain was designed with two large resistors at the top and bottom of the chain




  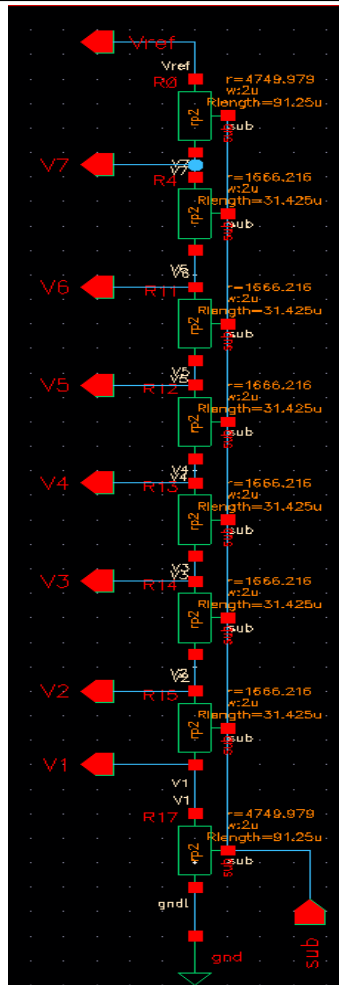
# 1. Matched Resistor Schematic and Layout



# 1. Matched Resistor


## Reference voltage levels

 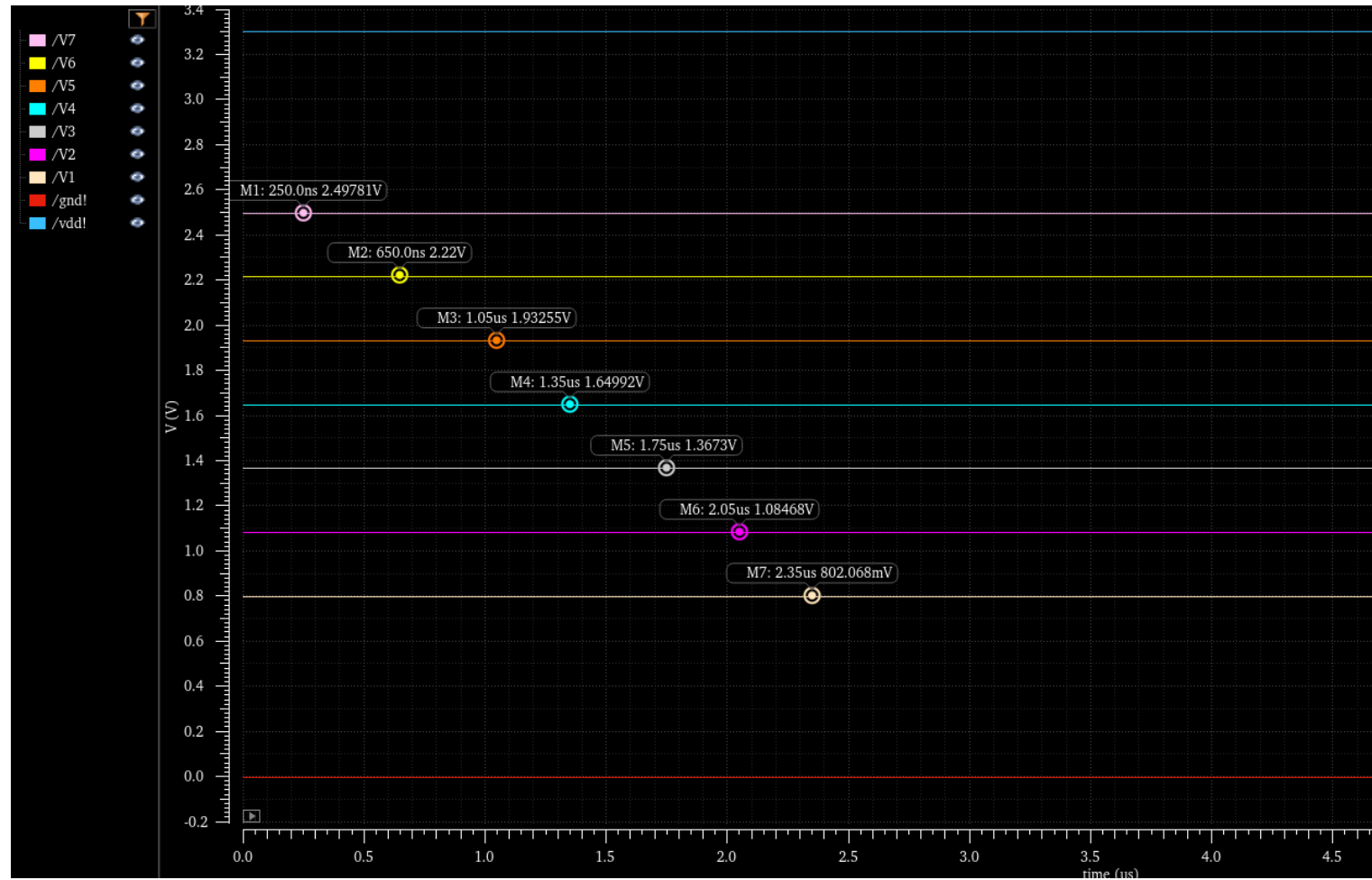


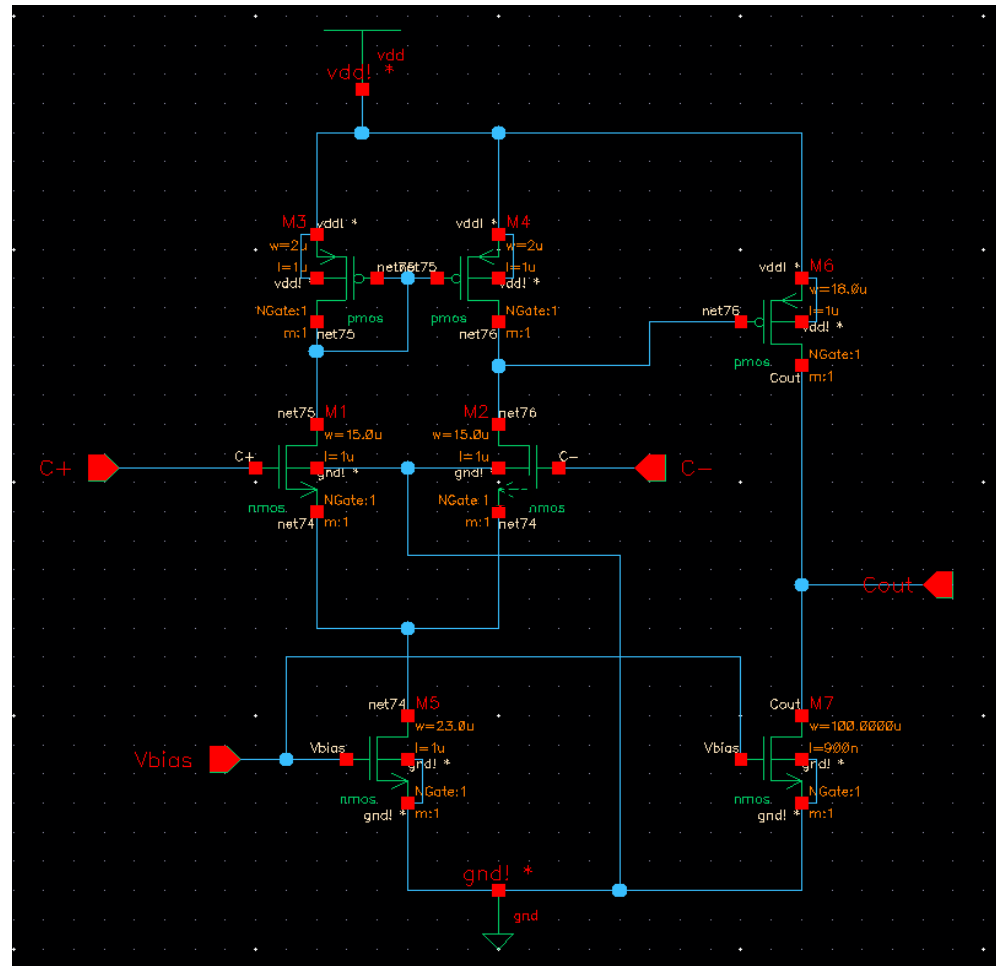
## 2. Comparator Schematic



- Two stage comparator
- Transistor ratios are found during the lab session(design steps)




## 2. Comparator
  
### Layout

- **Merging the common source to reduce area**





 - **Simple interdigitized matching**
  - More matching rules could be followed to improve the design





# 2. Comparator

Analogue extracted view

 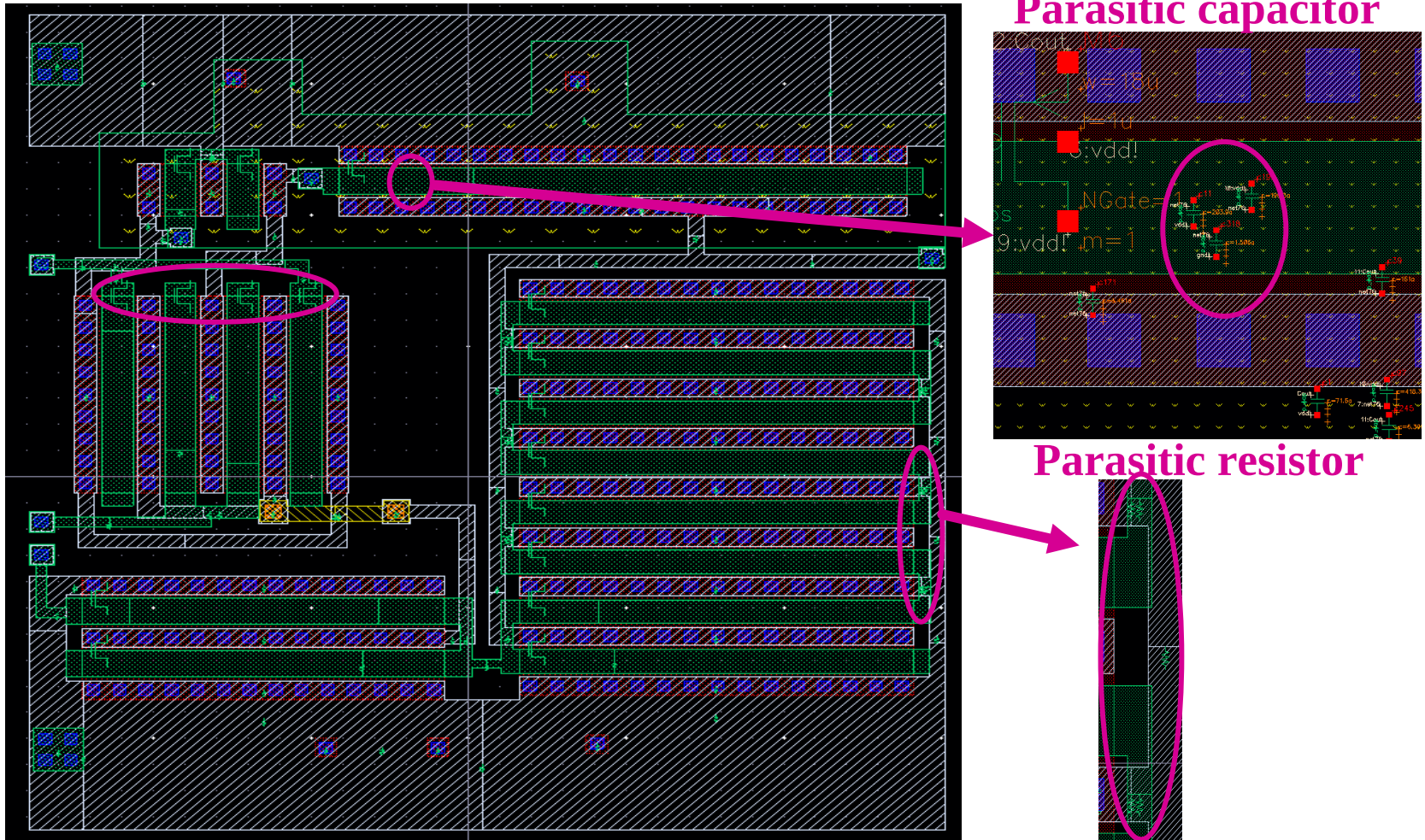


# 2. Comparator

## Transient analysis

 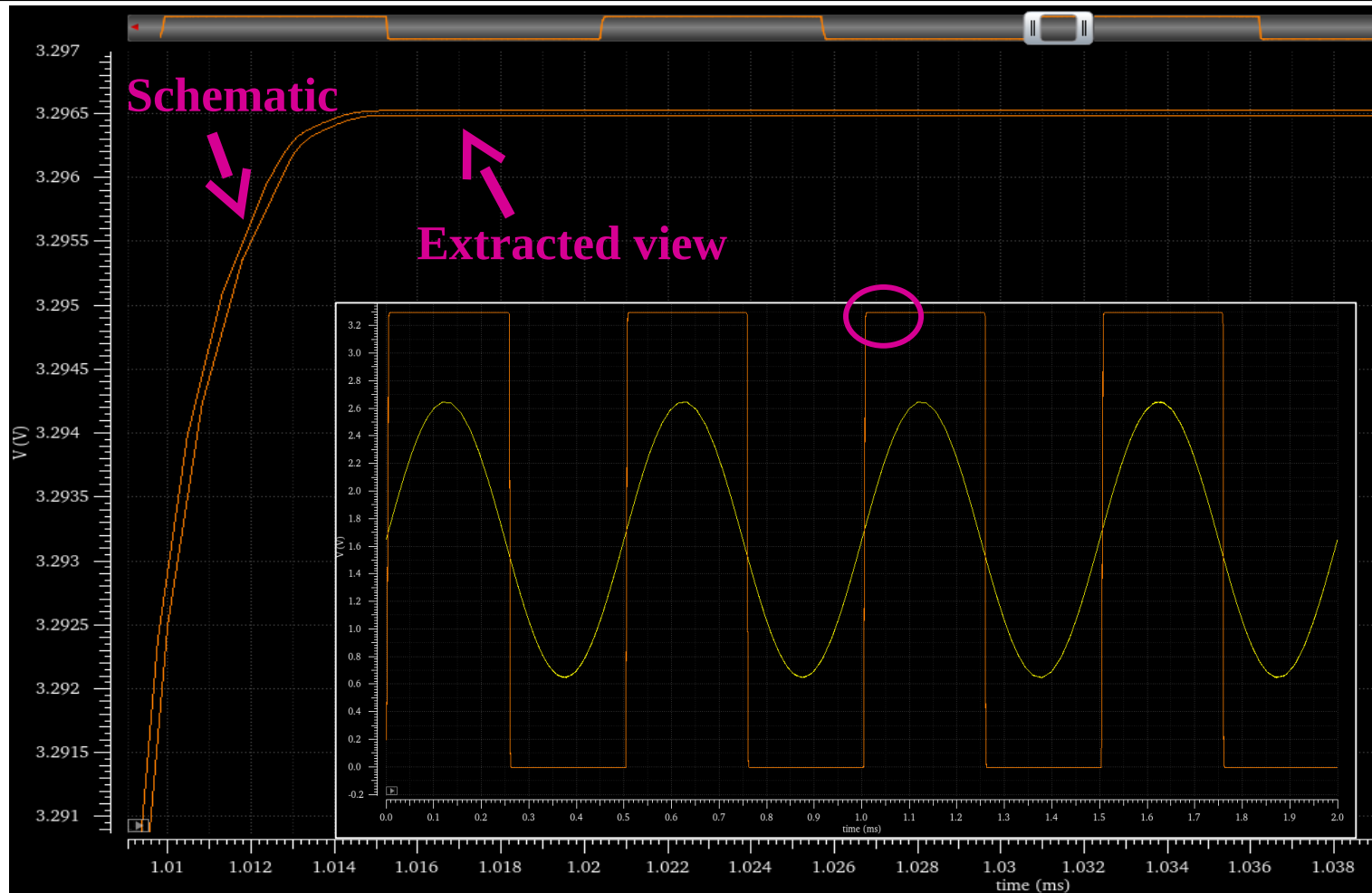

# 3. Bias Circuit


## • Schematic

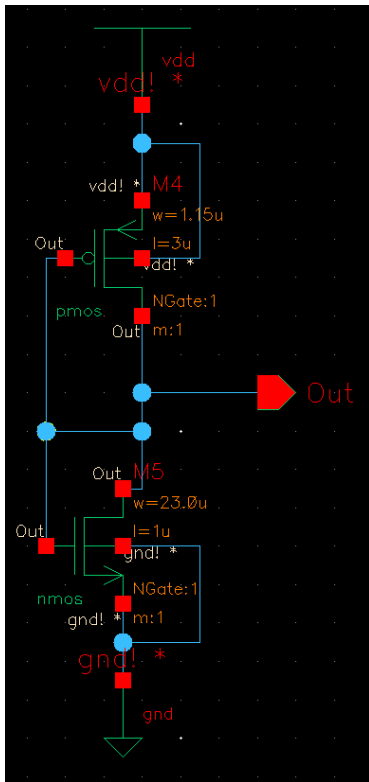

Current value Id from schematic	Current value Id from extracted view
NMOS (M5)	NMOS (M5)
20 uA	19.864 uA

- W/L ratio of the transistor M4 has tuned by simulation to achieve 20uA
- One bias cell is enough for the 7 comparators



## • Layout

 

# 3. Bias Circuit

Analog extracted view


- RC extraction by Xfab values defaults

 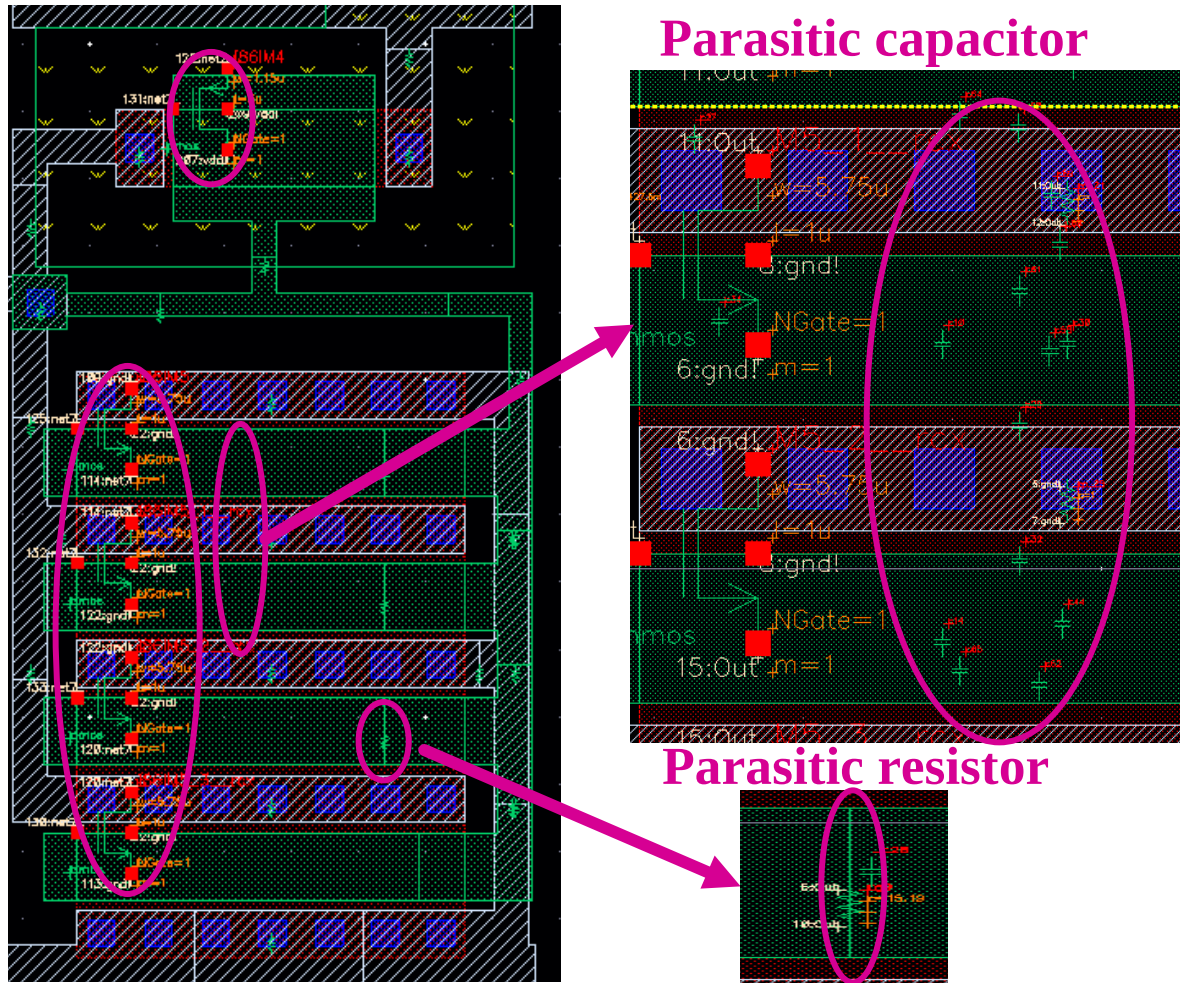

## 4. Logic Gates and Encoder
 
### Realization of encoder

- The behavioral model of the encoder in Verilog should be converted to a physical circuit.
- For this, firstly, the logic gates are created.
- Subsequently, the truth table of the Encoder is extracted, and using the created gates, the schematic and layout are built.
- The following slides follow the above-mentioned steps.



## 4. Logic Gates and Encoder

### Encoder Verilog code implementation

```
//Verilog HDL for "TL22", "Encoder" "functional"
```

```
module Encoder (DataIn_i7, DataOut_o3);  
  
    input [6:0] DataIn_i7;  
    output [2:0] DataOut_o3;  
    reg [2:0] DataOut_o3;  
  
    always @(DataIn_i7)  
    begin  
        casex (DataIn_i7)  
            8'b1XXXXXX : DataOut_o3 = 7;  
            8'b01XXXXX : DataOut_o3 = 6;  
            8'b001XXXX : DataOut_o3 = 5;  
            8'b0001XXX : DataOut_o3 = 4;  
            8'b00001XX : DataOut_o3 = 3;  
            8'b000001X : DataOut_o3 = 2;  
            8'b0000001 : DataOut_o3 = 1;  
            default : DataOut_o3 = 0;  
        endcase  
    end  
endmodule
```






---
 
## 4. Logic Gates and Encoder

- Logic gates are used as building blocks to realize the encoder operation.
- Encoder uses of NAND and NOT gates.
- Three different variants of NAND gate is used
  - 4 inputs to 1 output
  - 3 inputs to 1 output
  - 2 inputs to 1 output
- Encoder block, previously modelled using Verilog is illustrated using schematic and layout so as to represent it in manufacturable form.



# 4. Logic Gates and Encoder


## Logic Gates Truth Tables

In1_nand 4x1	In2_nand 4x1	In3_nand 4x1	In4_nand 4x1	Out_nand 4x1
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

In1_nand 3x1	In2_nand 3x1	In3_nand 3x1	Out_nand 3x1
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

In1_nand 2x1	In2_nand 2x1	Out_nand 2x1
0	0	1
0	1	1
1	0	1
1	1	0


inv_input0	inv_output
0	1
1	0

 


# 4. Logic Gates and Encoder

## NAND4x1

- Schematic


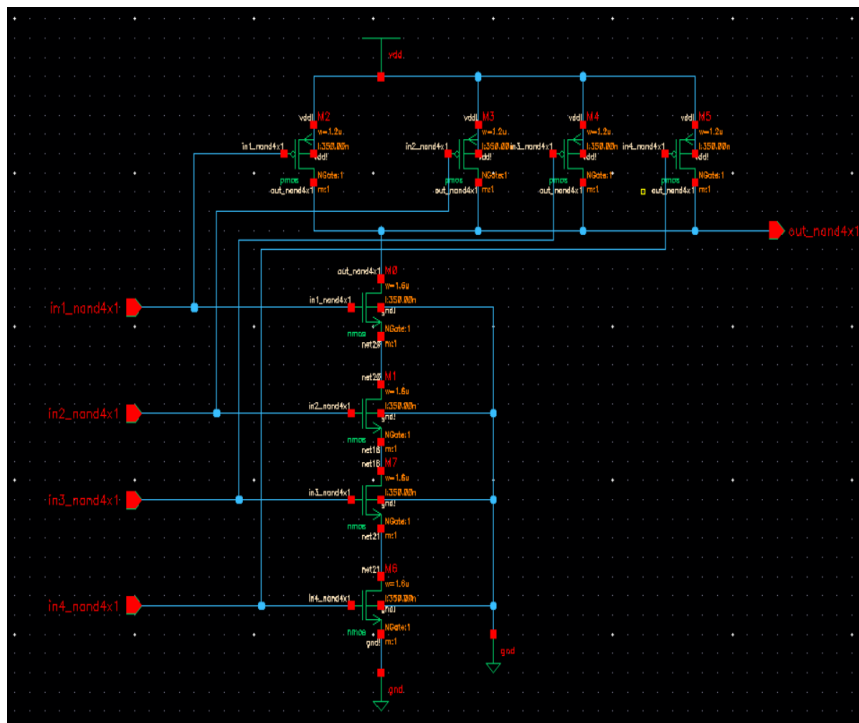


- Layout

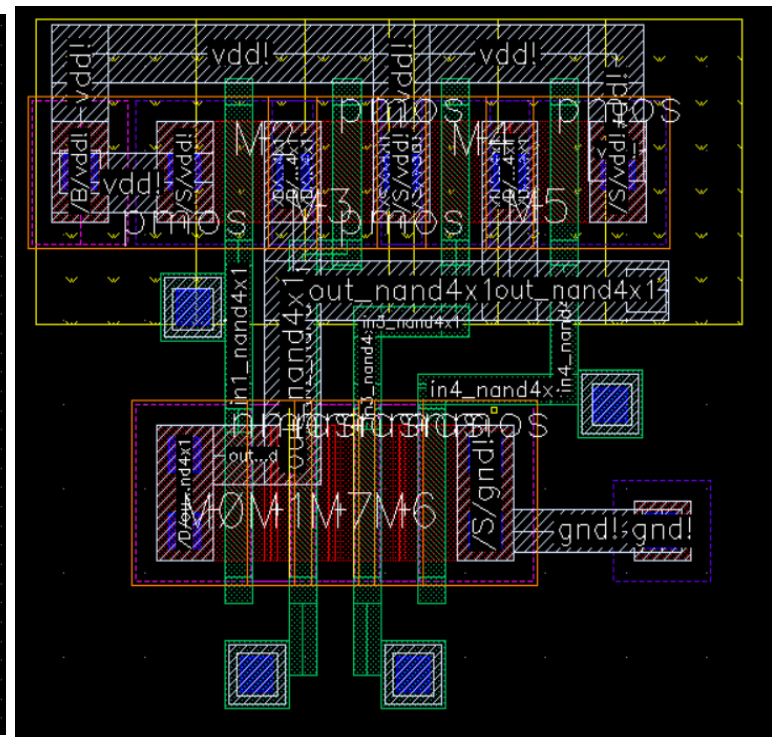

# 4. Logic Gates and Encoder


## Transient Response (NAND4x1)

  


# 4. Logic Gates and Encoder

## NAND3x1

- Schematic


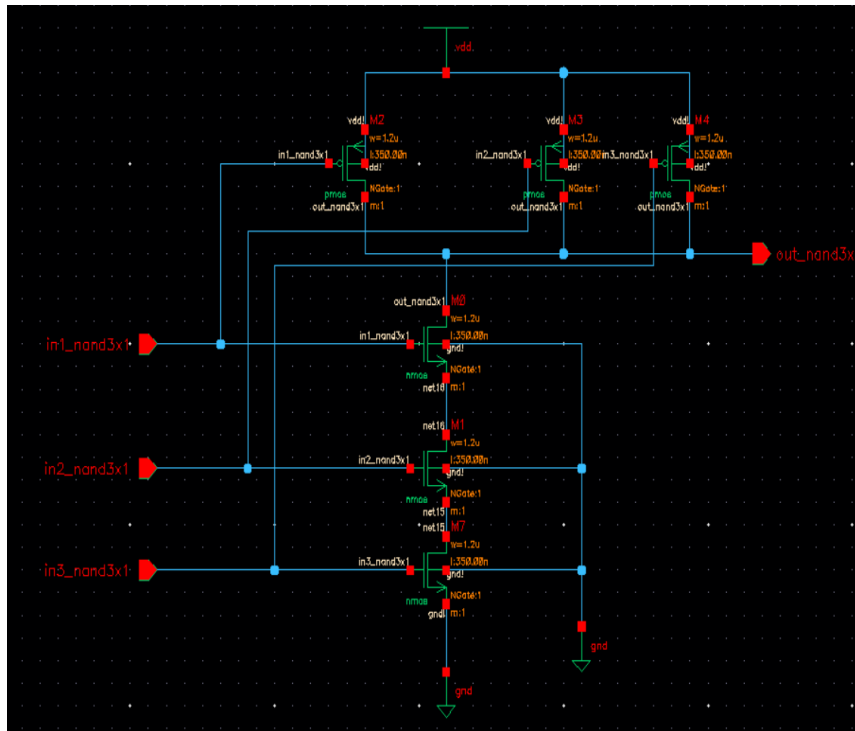


- Layout

 

# 4. Logic Gates and Encoder


## Transient Response (NAND3x1)

  


# 4. Logic Gates and Encoder

## NAND2x1

- Schematic

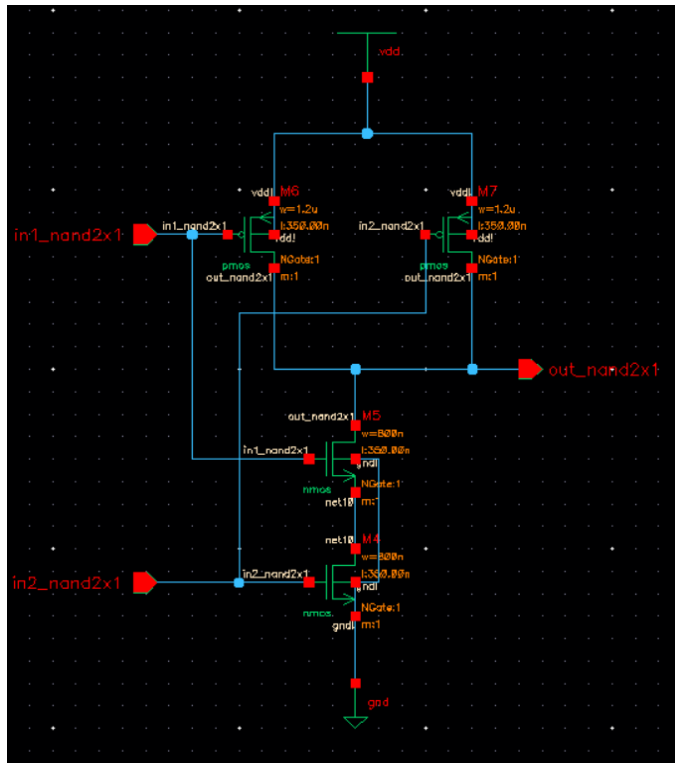


- Layout

 

# 4. Logic Gates and Encoder

## Transient Response (NAND2x1)

 






# 4. Logic Gates and Encoder

## NOT

- Schematic


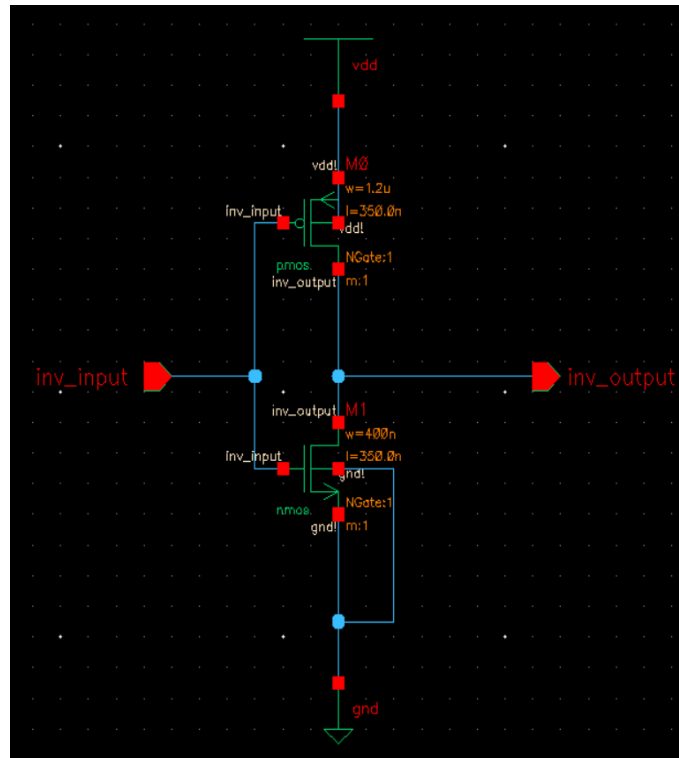


- Layout

  

# 4. Logic Gates and Encoder


## Transient Response (NOT)

  

# 4. Logic Gates and Encoder

## Encoder Truth Table

In7	In6	In5	In4	In3	In2	In1	Out2	Out1	Out0
0	0	0	0	0	0	0	0	0	0
0	0	0	0	0	0	1	0	0	1
0	0	0	0	0	1	X	0	1	0
0	0	0	0	1	X	X	0	1	1
0	0	0	1	X	X	X	1	0	0
0	0	1	X	X	X	X	1	0	1
0	1	X	X	X	X	X	1	1	0
1	X	X	X	X	X	X	1	1	1

 

## 4. Logic Gates and Encoder

### Logic functions


$$Q_2 = I_7 + I_6 + I_5 + I_4$$

$$Q_1 = \bar{I}_7 \bar{I}_6 \bar{I}_5 \bar{I}_4 \bar{I}_3 I_2 + \bar{I}_7 \bar{I}_6 \bar{I}_5 \bar{I}_4 I_3 + \bar{I}_7 I_6 + I_7$$

$$Q_0 = \bar{I}_7 \bar{I}_6 \bar{I}_5 \bar{I}_4 \bar{I}_3 \bar{I}_2 I_1 + \bar{I}_7 \bar{I}_6 \bar{I}_5 \bar{I}_4 I_3 + \bar{I}_7 \bar{I}_6 I_5 + I_7$$

The function can be simplified exploiting the Boolean identity:

$$\bar{A}B + A = A + B$$

 

## 4. Logic Gates and Encoder

### Simplification

$$Q_2 = I_7 + I_6 + I_5 + I_4$$

$$Q_1 = \overline{I_5} \overline{I_4} I_2 + \overline{I_5} \overline{I_4} I_3 + I_6 + I_7$$


$$Q_0 = \overline{I_6} \overline{I_4} \overline{I_2} I_1 + \overline{I_6} \overline{I_4} I_3 + \overline{I_6} I_5 + I_7$$

Further manipulation using De Morgan's law, to realize it with only inverters and NAND gates:



$$Q_2 = \overline{\overline{I_7} \cdot \overline{I_6} \cdot \overline{I_5} \cdot \overline{I_4}}$$

$$Q_1 = \overline{\overline{\overline{I_5} \overline{I_4} I_2} \cdot \overline{\overline{I_5} \overline{I_4} I_3} \cdot \overline{I_6} \cdot \overline{I_7}}$$
 
$$Q_0 = \overline{\overline{\overline{I_6} \overline{I_4} \overline{I_2} I_1} \cdot \overline{\overline{I_6} \overline{I_4} I_3} \cdot \overline{\overline{I_6} I_5} \cdot \overline{I_7}}$$




# 4. Logic Gates and Encoder Schematic

 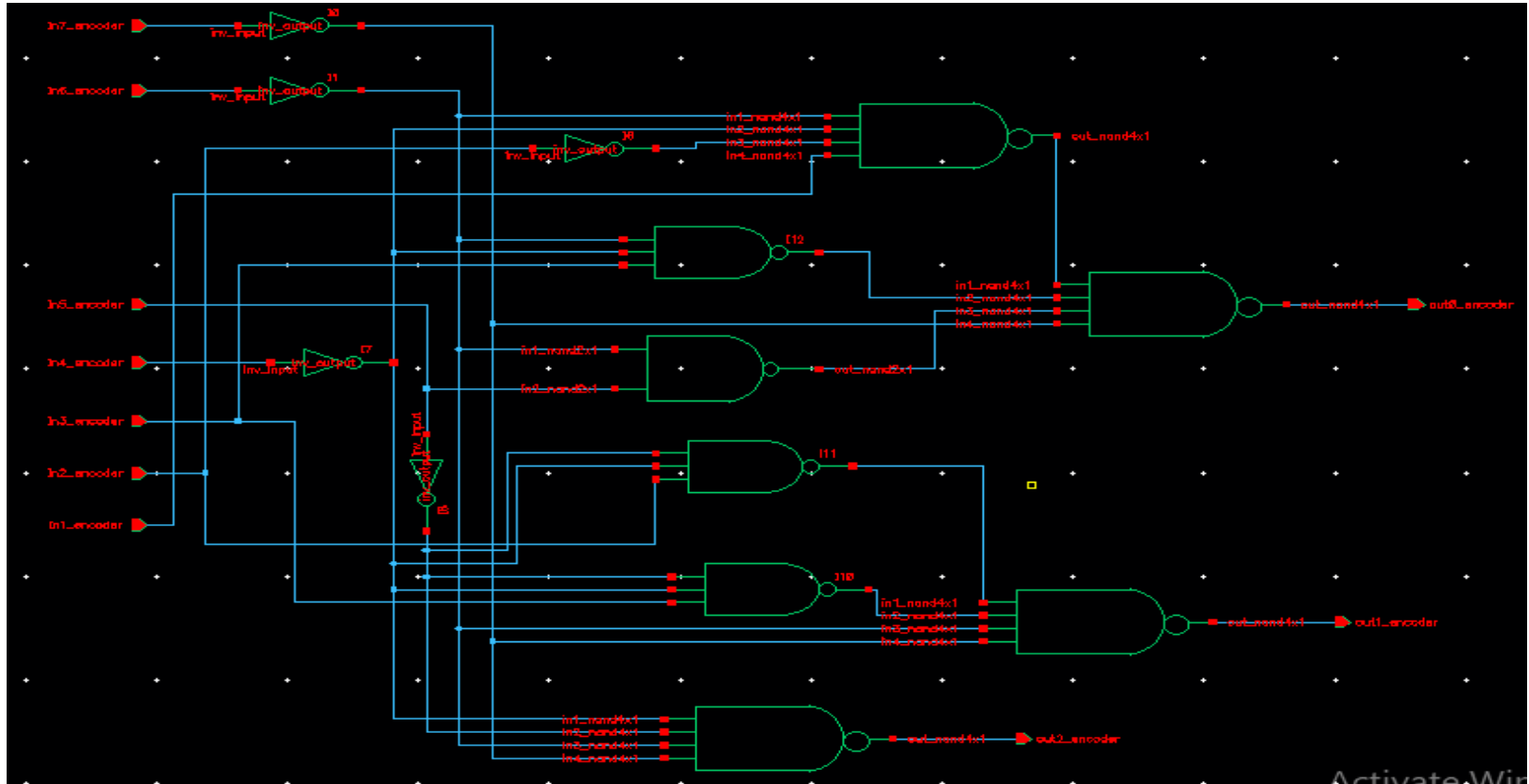

# 4. Logic Gates and Encoder

## Layout


 


# 4. Logic Gates and Encoder

Transient analysis (Analog extracted view)

Frequency: 2 kHz

 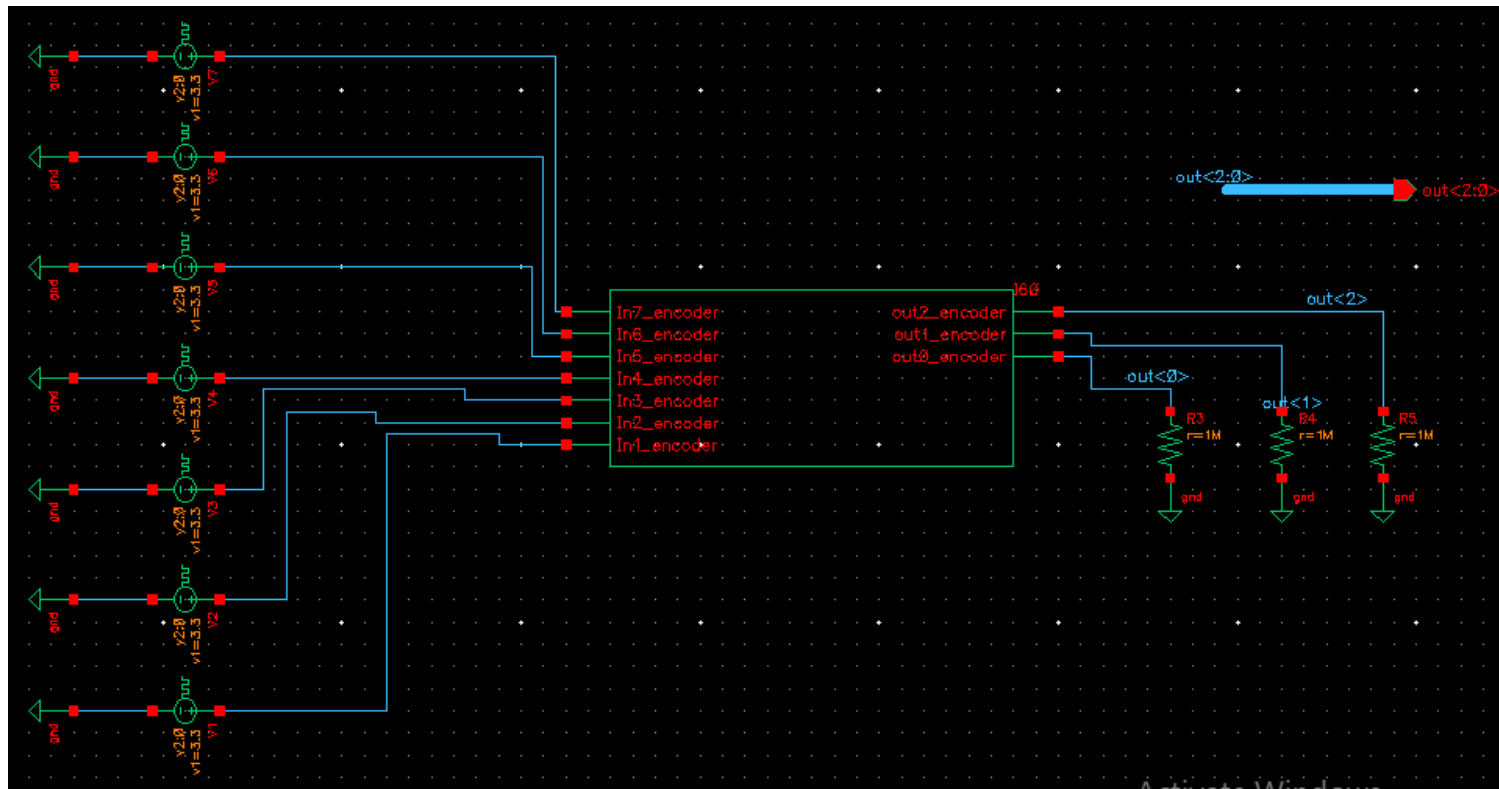
The inputs are switched from low to high in the order of their indices.






# 4. Logic Gates and Encoder
 
## Transient analysis (Analog extracted view)



# 4. Logic Gates and Encoder
 
## Transient analysis (Analog extracted view)




# 5. ADC

## Top Hierarchical level Schematic
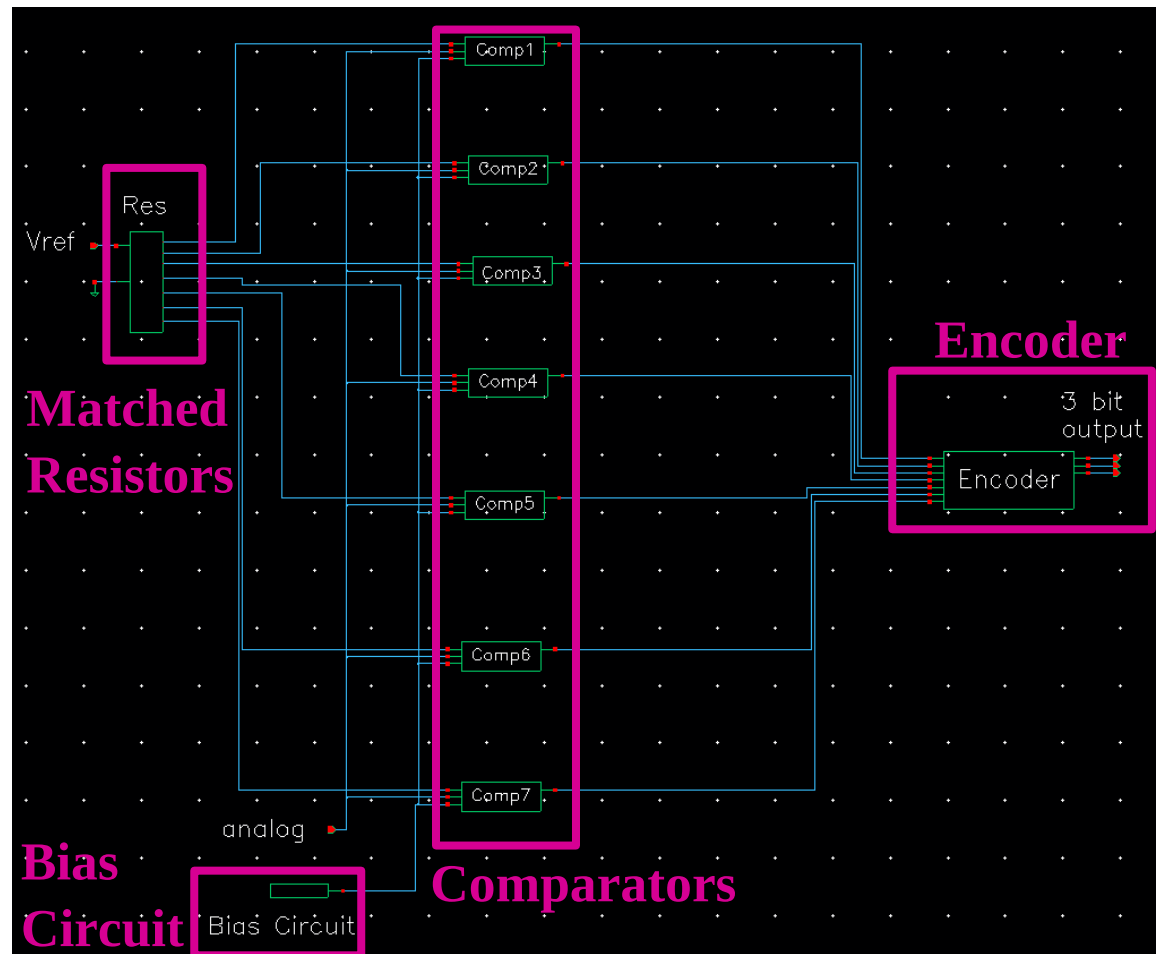
### ➤ Design specifications:

- Reference voltage:  
 $V_{ref} = V_{dd} = 3.3V$
- Input voltage range :  
3.3V and 0V
- Bias Current  $\approx 20\mu A$



# 5. ADC Layout

- Area of Flash cell:  
134.575um x  
141.325um

Run: "ADC\_LVS" (on iseserver002) ❌

Run: "ADC\_LVS" from  
/home/tesys\_2022\_ghezal/AssuraLVS

Schematic and Layout Match.  
Do you want to view the results of this run?

Summary of LVS Issues

Extraction Information:

- 0 cells have 0 mal-formed device problems
- 0 cells have 0 label short problems
- 0 cells have 0 label open problems

Comparison Information:

- 0 cells have 0 Net mismatches
- 0 cells have 0 Device mismatches
- 0 cells have 0 Pin mismatches
- 0 cells have 0 Parameter mismatches



ELW Information:

Total DRC violations: 0

(on iseserver002) ❌



No DRC errors found.

Close

 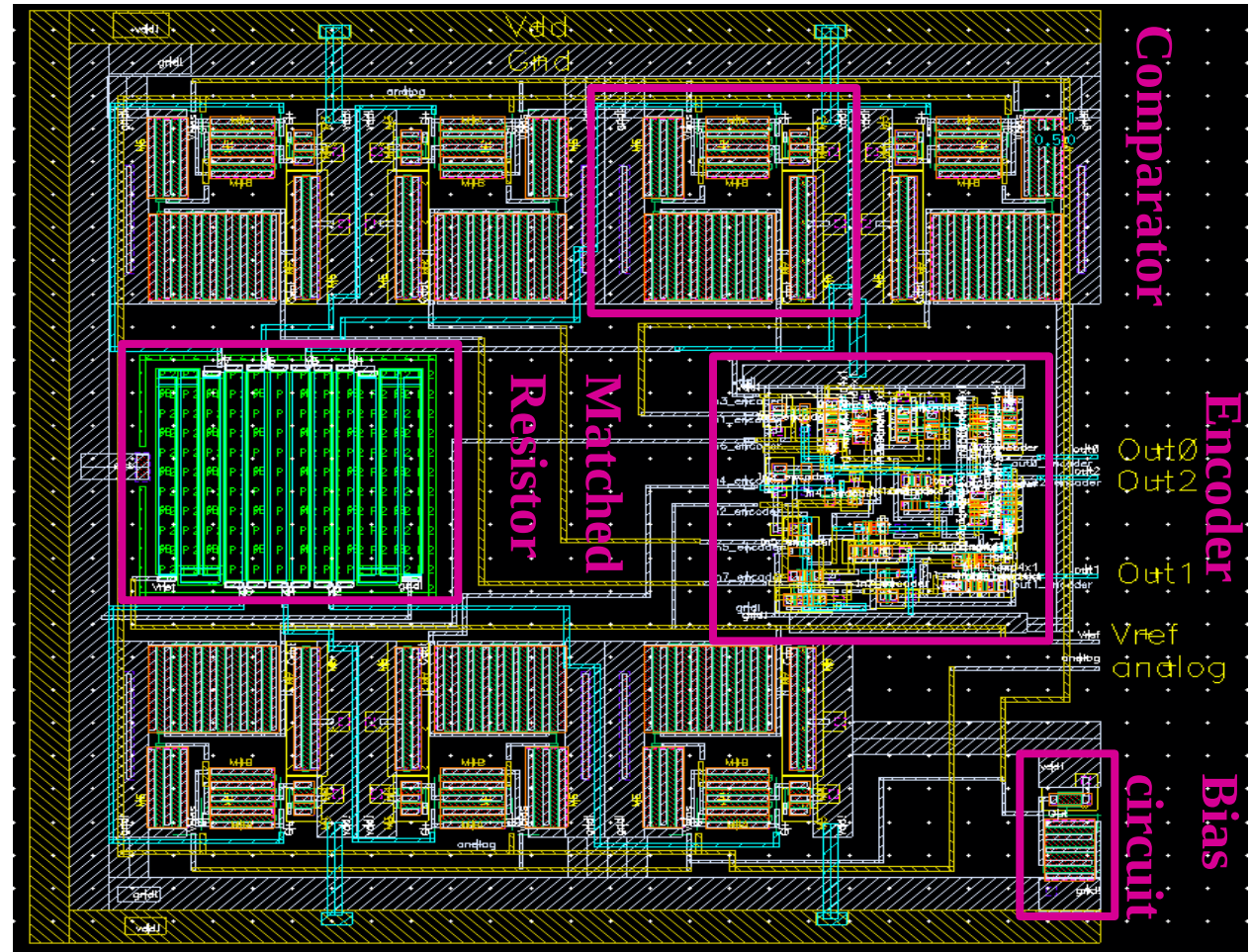


# 5. ADC

## Analog extracted view

  


# 5. ADC Test bench

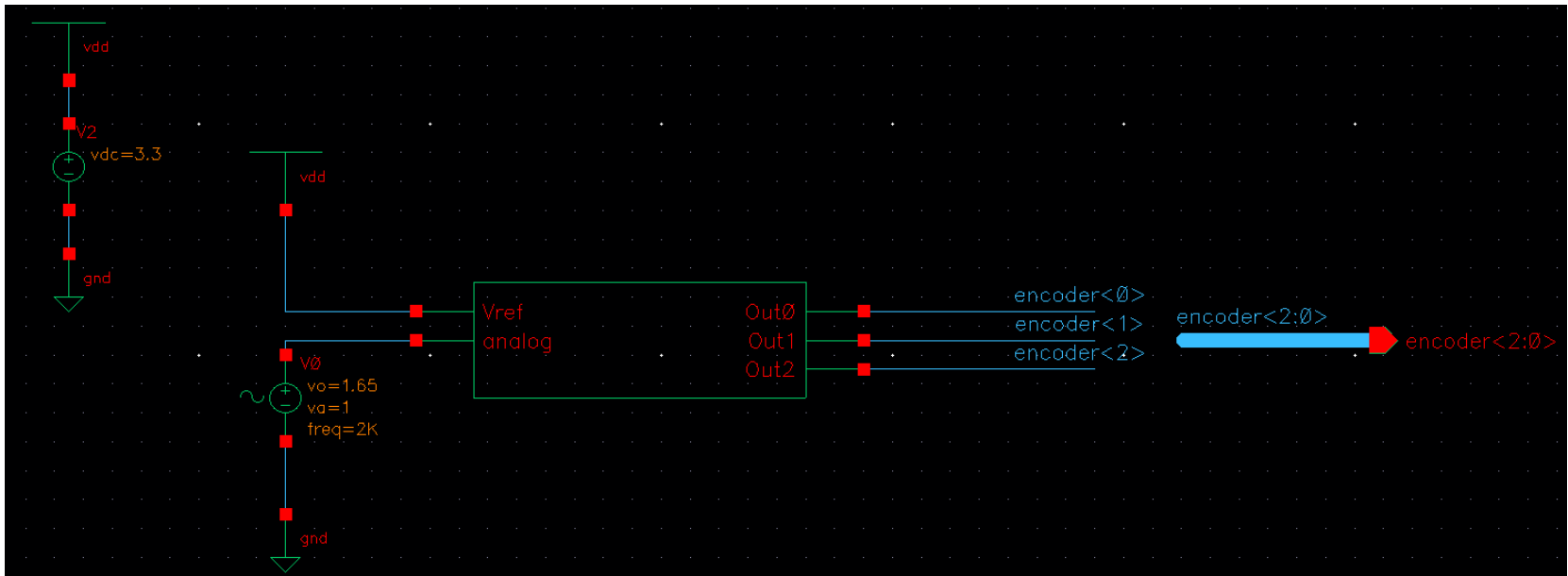


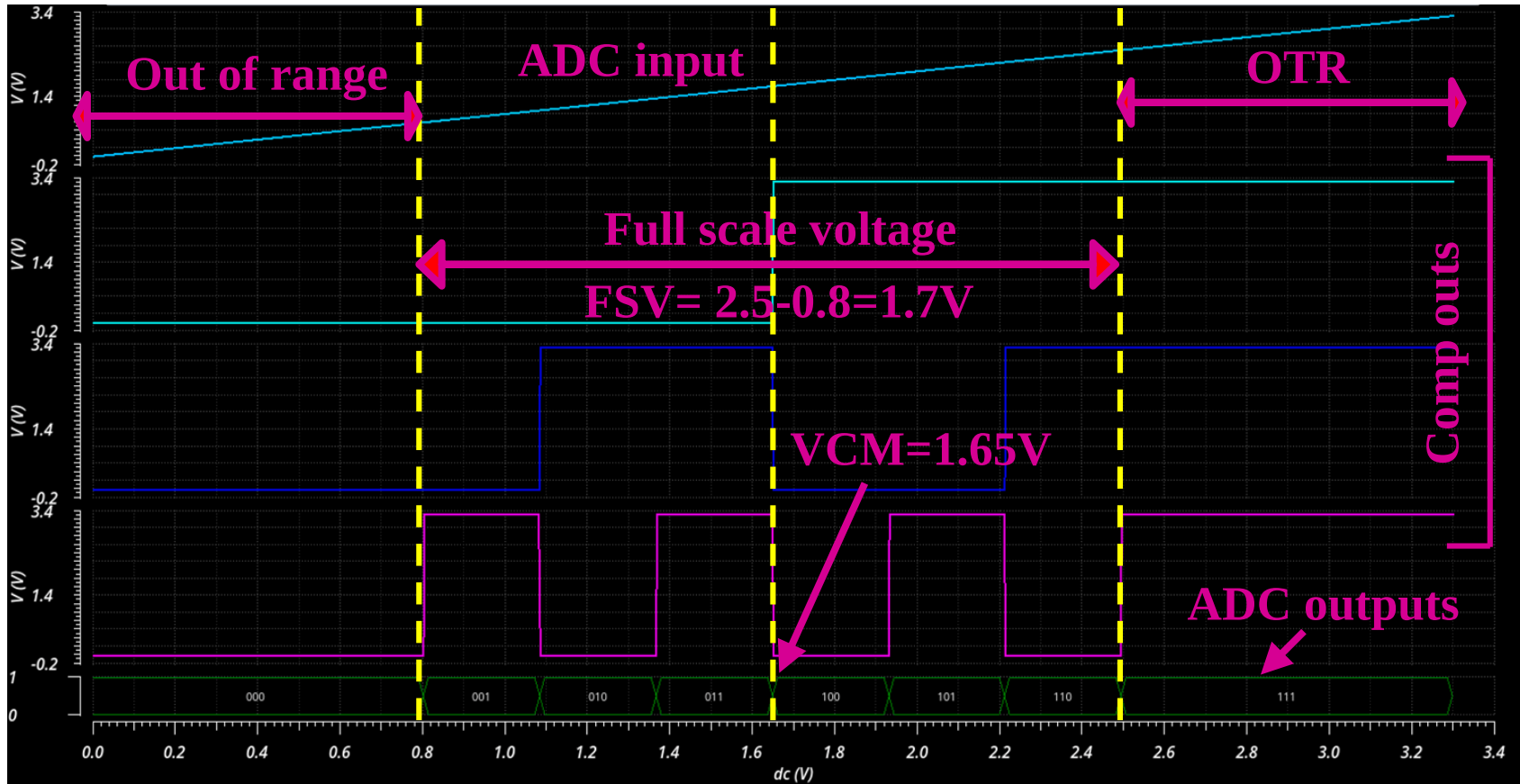
# 5. ADC

DC characteristic (Analog extracted view)



# 5. ADC

 
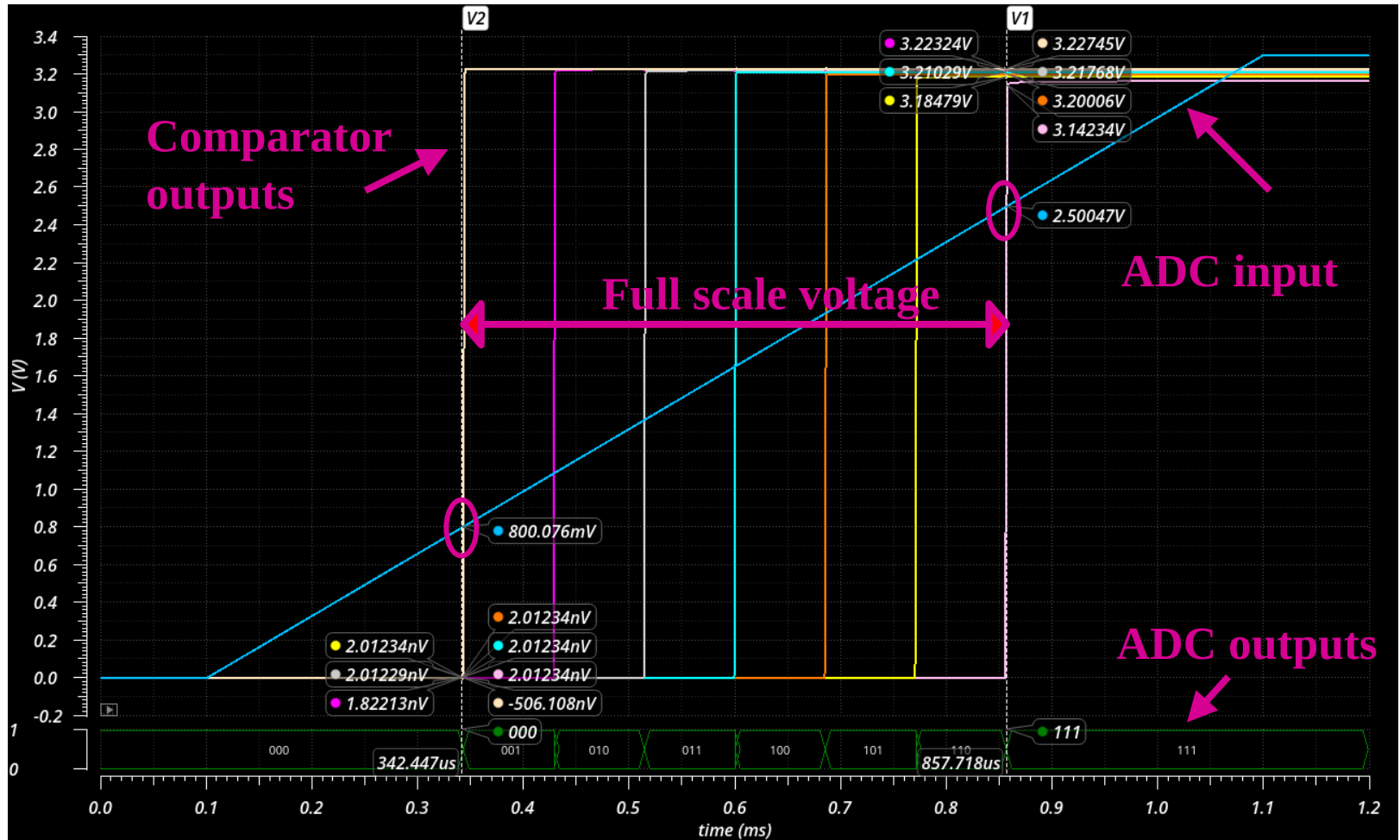
## Transient analysis (Analog extracted view)





# 5. ADC
  
## Transient analysis (analog extracted view)




# 5. ADC

## Transient analysis


- Design properties: Post layout simulation (extracted view)

Properties	Values
Quiescent power	2.4057 mW
Conversion Power @ max. freq.	2.9073 mW
Device statistics for ADC	115 Transistors
Maximum frequency	10 kHz

 
 
# Conclusion


- Nominal design of 3-Bit Flash ADC done
- Maximum frequency 10 kHz with 2.9073 mW conversion power and 2.4057 mW quiescent power
- Compact layout area of 134.575um x 141.325um
- MC, WC/corner simulations!
- Better matching
- Reference voltage circuit design.



---
 
# References

- ✓ Lecture and lab material of TESIS subject by Prof. Koenig used to prepare this project and the presentation slides



---



Thank you for your attention!

