



Tesys Project SS23

3-Bit Rail to Rail DAC Design and Layout in XFAB 0.35 um CMOS Technology

Janis Krieger

Conner Cordruwisch

Supervisor: Prof. Dr.-Ing. Andreas König



Overview

1. Introduction

1.1 Motivation

2. Topology

3. Component Design & Simulation

3.1 Operational Amplifier

3.2 Decoder Logic

3.3 Resistive Divider

4. DAC Design

4.1 Testbench and Simulation

4.2 Layout vs. Schematic

4.3 Final Specs

5. Conclusion




1.1 - Motivation

- ❖ Design methods for application-specific cells and blocks
 - Selection, dimensioning, simulation, layout
- ❖ Project contents:
 - Modeling, design, simulation, layout
 - Integration with analog structures in mixed-signal designs
 - Utilize state of the art software
 - Integration of industrial process parameters (XFAB 0.35 um)

⇒ **3-Bit Rail to Rail DAC Design and Layout**




2 - Topology

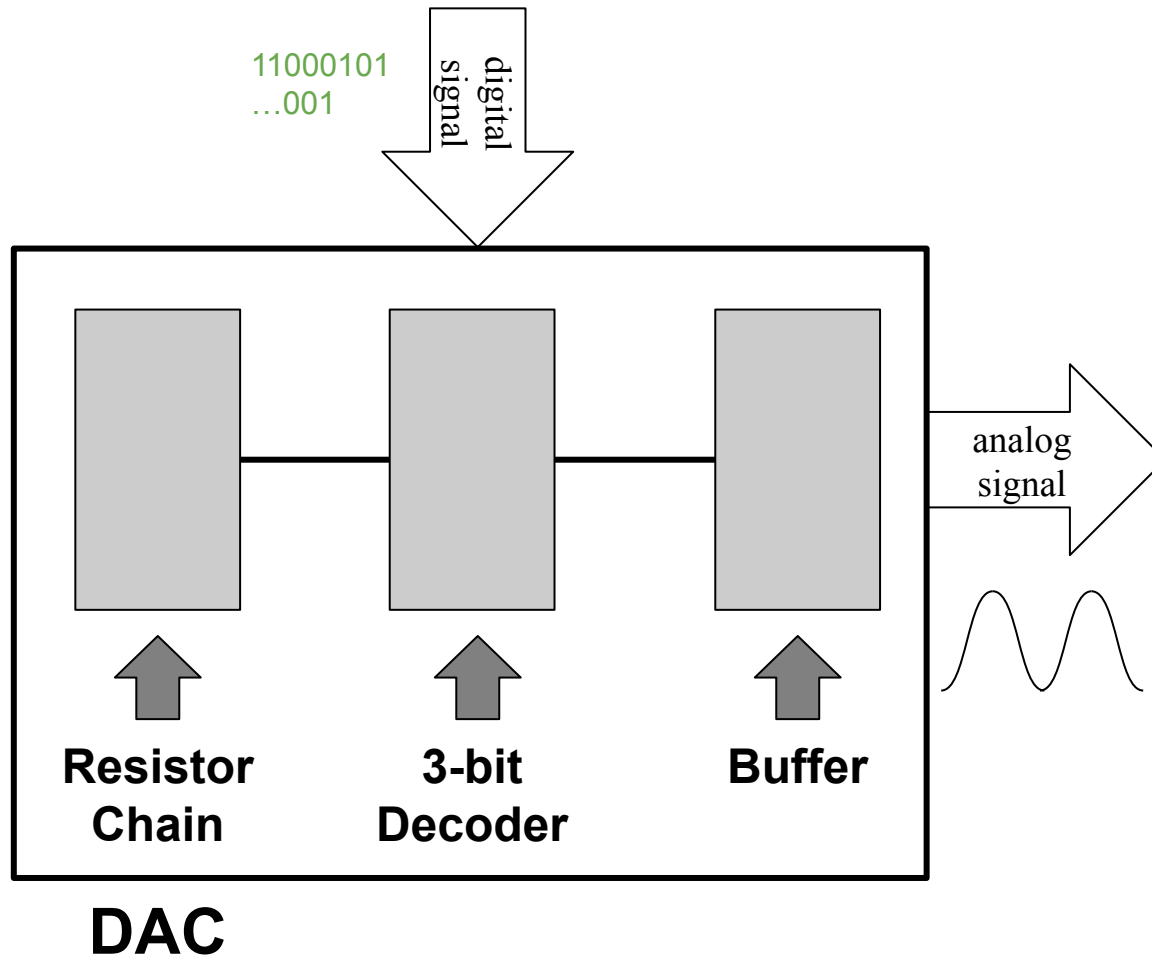

- ❖ 8 matched resistors
- ❖ PTL decoder
- ❖ Operational amplifier




3 - Component Design & Simulation

 

- ❖ Miller OpAmp configuration
- ❖ Designplan based on Allen/Holberg
- ❖ MATLAB implementation by Prof. Dr.-Ing. König
- ❖ Development of python adaption for extended parameter sweep



3 - Component Design & Simulation

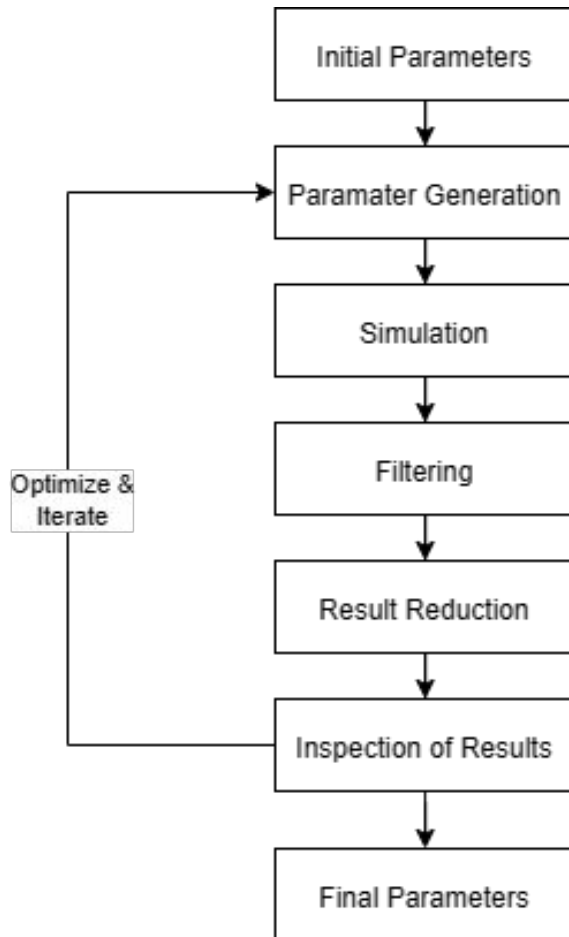

❖ Sweep parameters:

- AV0, GBW, CMRp, CMRm, ABp, ABm, SR

❖ Filtering:

- drop transistors with dimension greater than 100 μm
- Metric:
 - 0.999 quantile for CMR
 - 0.999 quantile for OR

❖ Manual simulation and inspection of final parameters



3 - Component Design & Simulation


Design Specification		Simulation Results	
AVO	60	I5	2.22E-06
GBW	2.00E+06	I7	2.25E-05
CMRp	1.45	S2	1
CMRm	-1.50	S3	2
ABp	0.70	S5	3
ABm	-0.80	S6	41
Phasemargin	1.05	S7	30
CMRR	80	Cc	2.22E-12
SR	1.00E+06	AV0_r	81.28063218
Ts	1.00E-09	Pdiss_r	8.16E-05
VDD	1.65	ABp_r	1.569649262
VSS	-1.65	ABm_r	-1.556066356
CL	1.00E-11	gm6	3.16E-04
RL	1.00E+05	gm2	3.63E-06
Pdiss	1	RI	1.43E+07
L	1.00E-06	RII	7.05E+05

- ❖ Optimized for:
 - small transistor dimensions
 - low power consumption



3.1 - Operational Amplifier

Schematic - Sizings

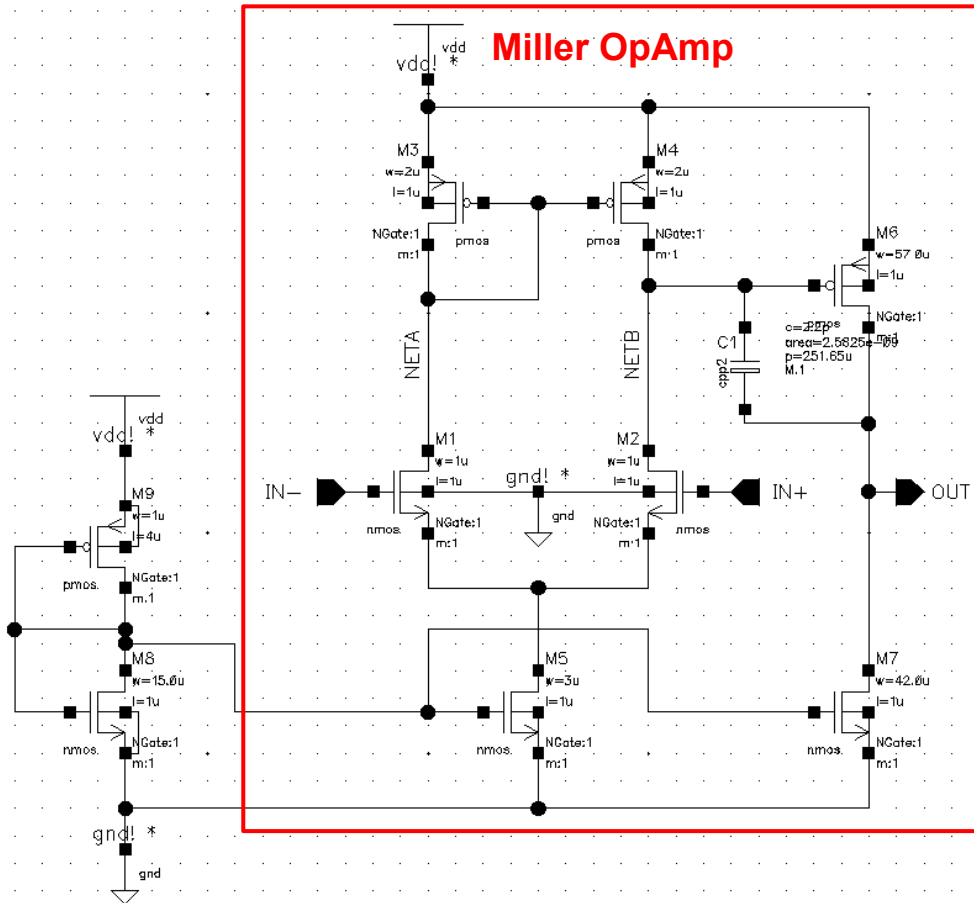


Transistor	W/L [um]
M1 / M2	1 / 1
M3 / M4	2 / 1
M5	3 / 1
M6	57 / 1
M7	42 / 1
M8	15 / 1
M9	1 / 4

❖ Optimization / Iteration of sizings for M6 & M7 to increase output driving capabilities



3.1 - Operational Amplifier

Schematic - Bias Circuit

 


- ❖ MOST-Diode voltage divider
- ❖ Current mirror for $I_5 = 2.22 \mu\text{A}$
- ❖ Optimized for low area
 - Parameter sweep of M8 & M9
 - Channel length adjustment
 - achieved current of $2.25 \mu\text{A}$



3.1 - Operational Amplifier

Layout - Differential Stage

 


- ❖ no matching for M1 & M2 due to small dimension width and length of 1 μm
- ❖ custom matched centroid transistor layout for M3 & M4



3.1 - Operational Amplifier

Layout - Folded Transistors

 


- ❖ Full custom folded transistor M8
- ❖ M6 & M7 generated from PRIMLIB template
- ❖ Advantages of folding
 - reduce area
 - flexibility of aspect ratio
 - minimize fabrication variation



3.1 - Operational Amplifier

Layout

 

3.1 - Operational Amplifier

Final Specs


Parameters	Design Plan	Final Results
Open loop gain AV0	60dB	81.54dB
Gain Band-Width	2MHz	1.10MHz
Common Mode Range p/m	1.45V -1.5V	1.61 V -1.43 V
Phasemargin	60°	78.57°
Slew Rate	1 V/us	1.02 V/us
Settling Time	1ns	0s
Output Range p/m	1.56V -1.56V	1.62 V -1.63V



 3.1 - Operational Amplifier

Simulation

Note: LSB not reachable due to limited ICMR.



Possible solutions:

- ❖ independent output stage for lower stages
- ❖ Non-inverting OpAmp circuit with small gain
- ❖ Rail to Rail OpAmp Designplan

In consultation with the supervisor, it was decided, due to the advanced timeline, to retain the imperfection and proceed with the layout



3.2 - Decoder Logic


Schematic

- ❖ Design based on “Analog integrated circuit design” by Johns David and Martin Kenneth W.
 - Pass Through Logic (PTL) design
 - area minimization

PMOS transistors


NMOS transistors

inverters

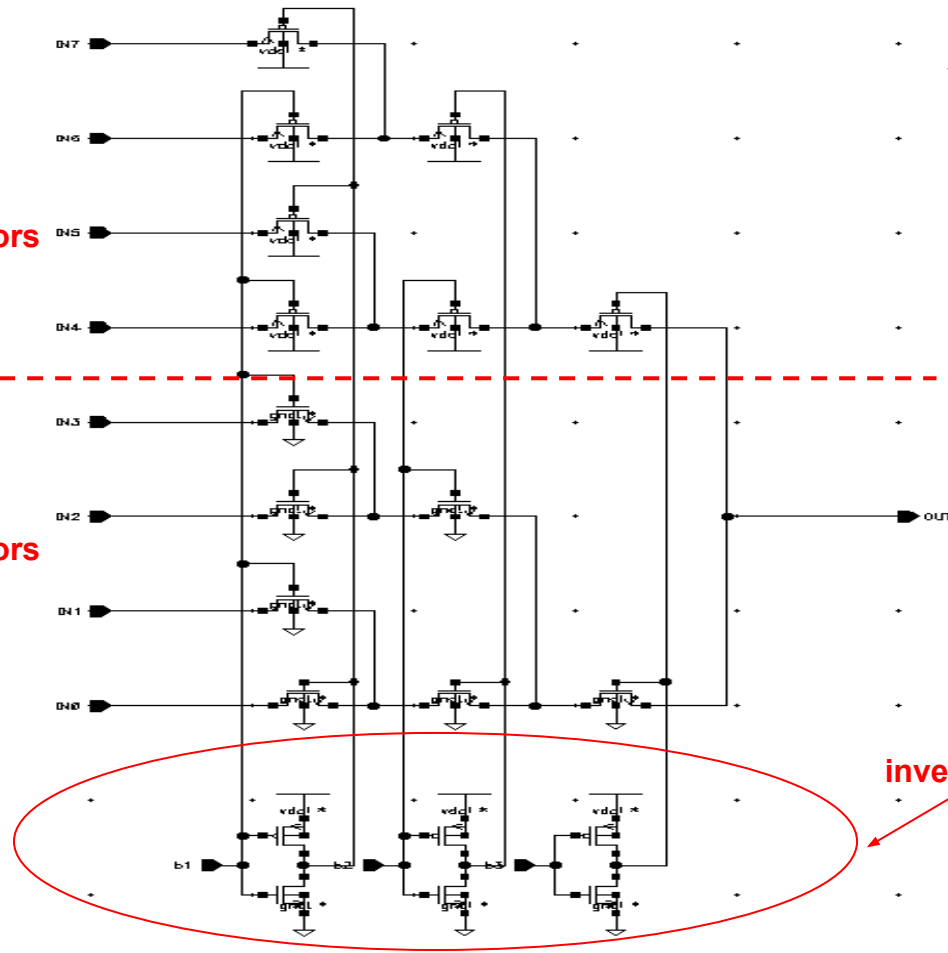


3.2 - Decoder Logic

Layout

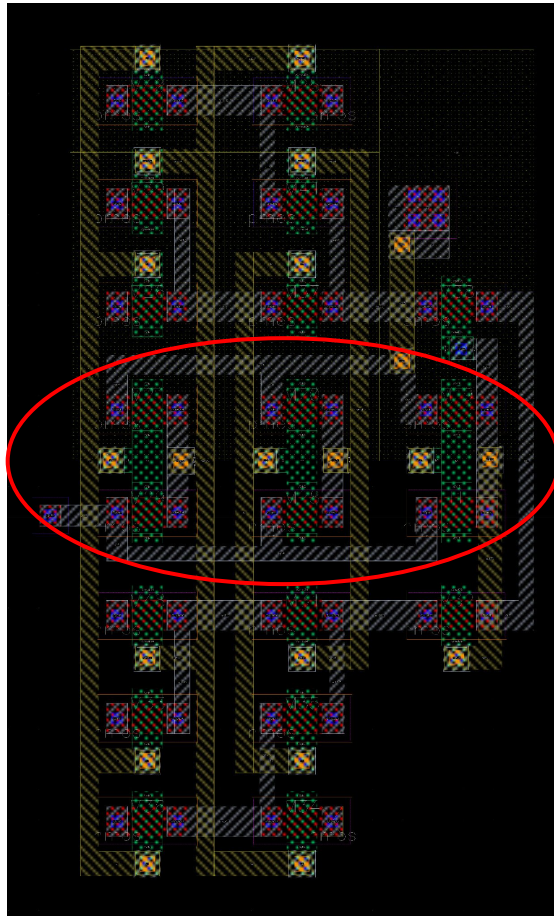


inverters

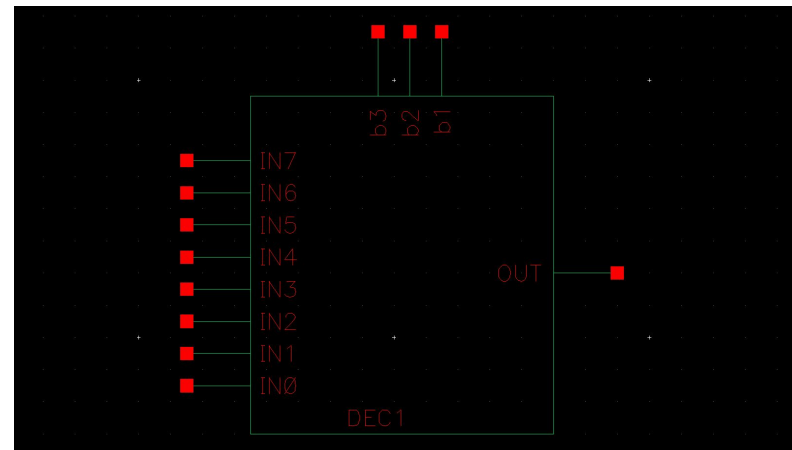- ❖ Layout for 3-Bit decoder
- ❖ Usage of uniform 1 um PRIMLIB transistors



3.2 - Decoder Logic

Simulation - Testbench

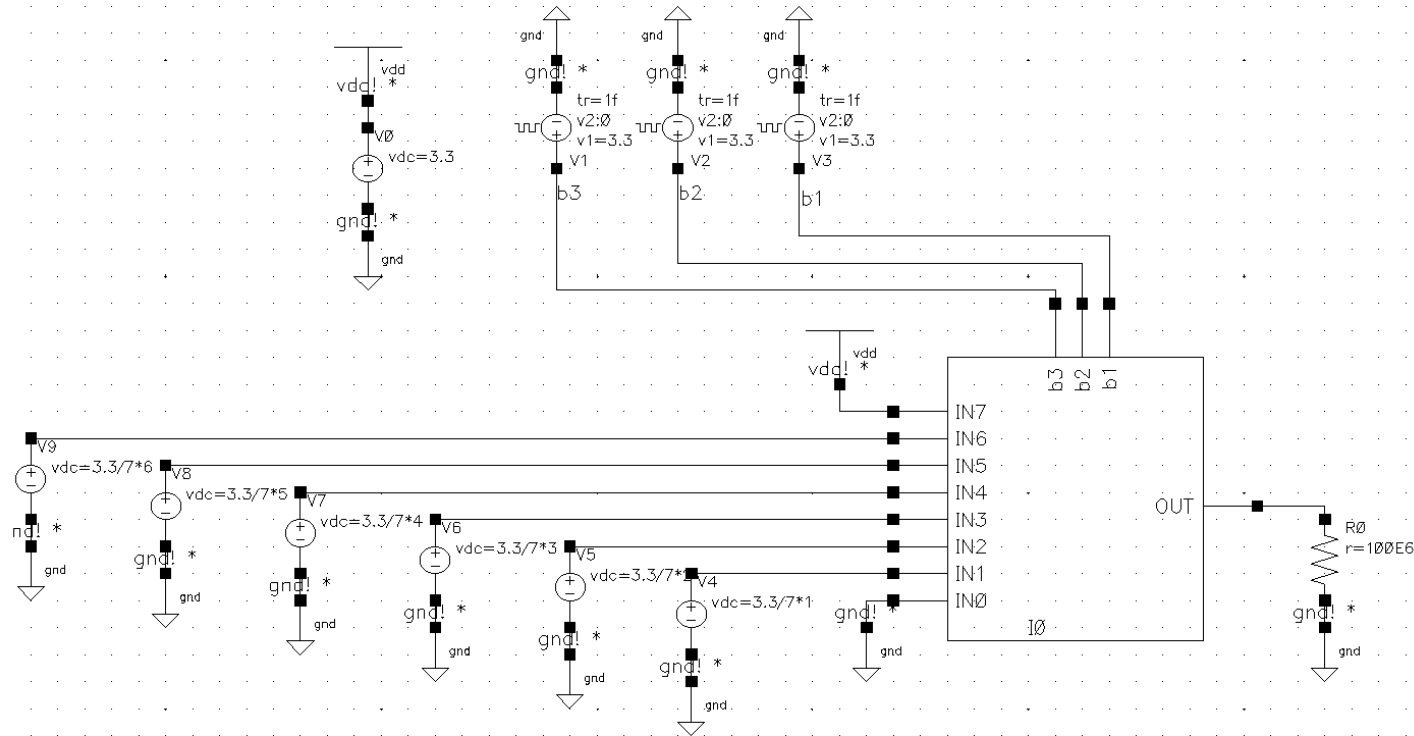


- ❖ Fixed input voltages
- ❖ Bit pattern for maximum decay and discrete rise



3.2 - Decoder Logic

Simulation - Layout vs. Schematic

 


Transition from NMOS to PMOS transistors



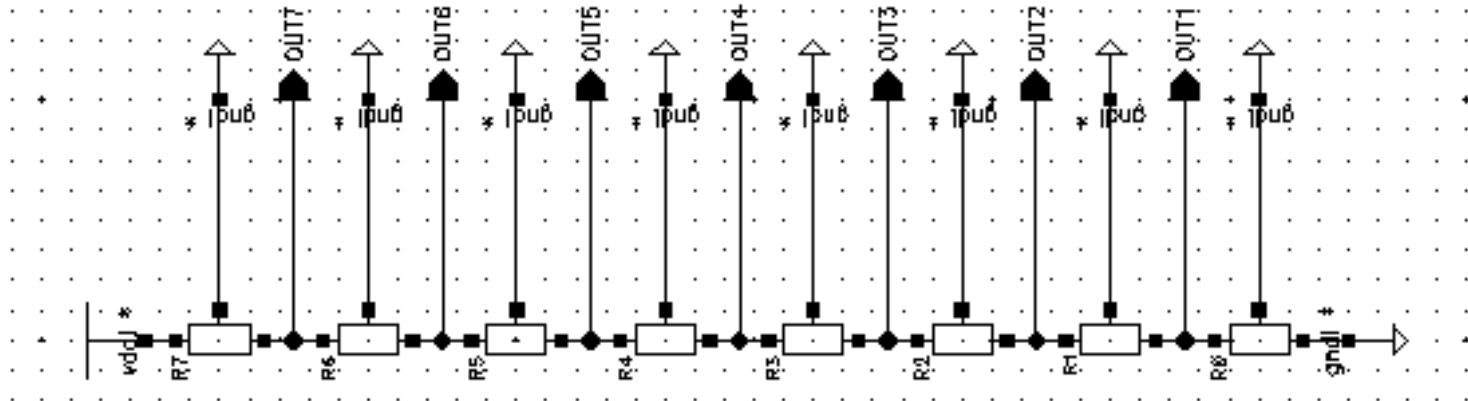3.3 - Resistive Divider

Schematic

- ❖ Goal: High impedance to minimize idle current
 - **PrimLib High-Res Poly2 Resistors**
- ❖ Dimensions:
 - $2^3 = 8$ Stages = 8 Resistors
 - 1um x 100um results in 10.734 kΩ
 - Power consumption: $(3.3 \text{ V})^2 / (8 \times 10.734 \text{ k}\Omega) = 0.13 \text{ mW}$




3.3 - Resistive Divider


Layout

Fully custom layout design using:

- ❖ POLY2 (high resistance per area)

 

4 - DAC Design

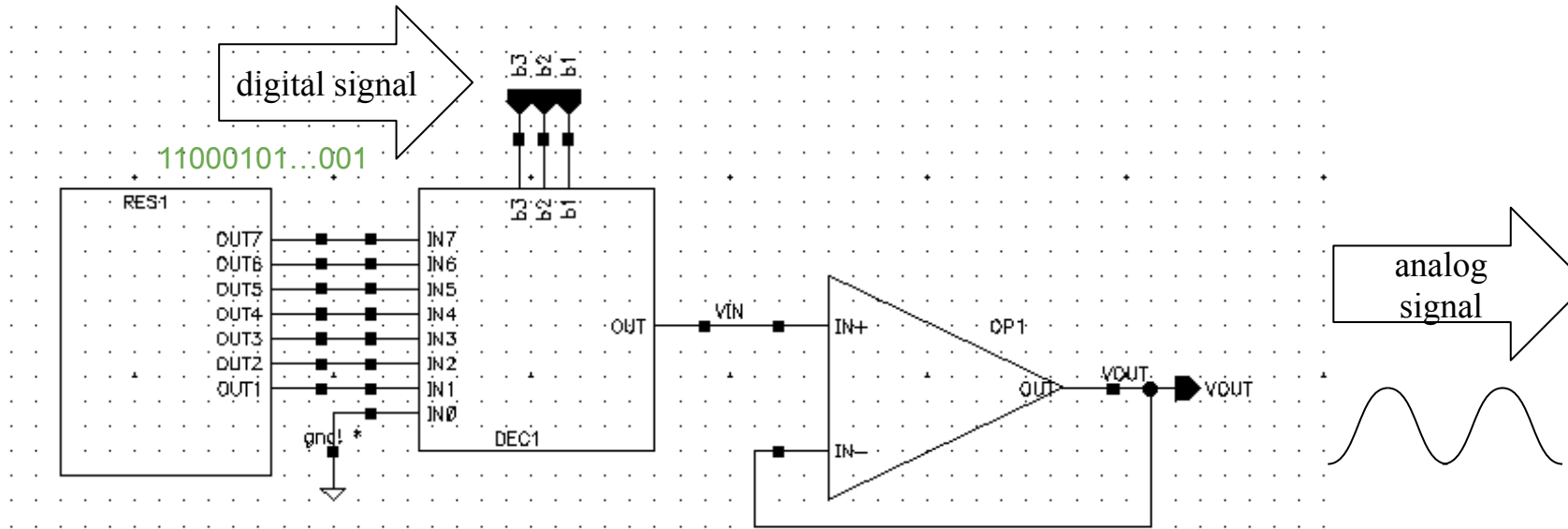

↑
**Resistor
Chain**


↑
**3-bit
Decoder**

↑
Buffer




4.1 - DAC Design

Testbench

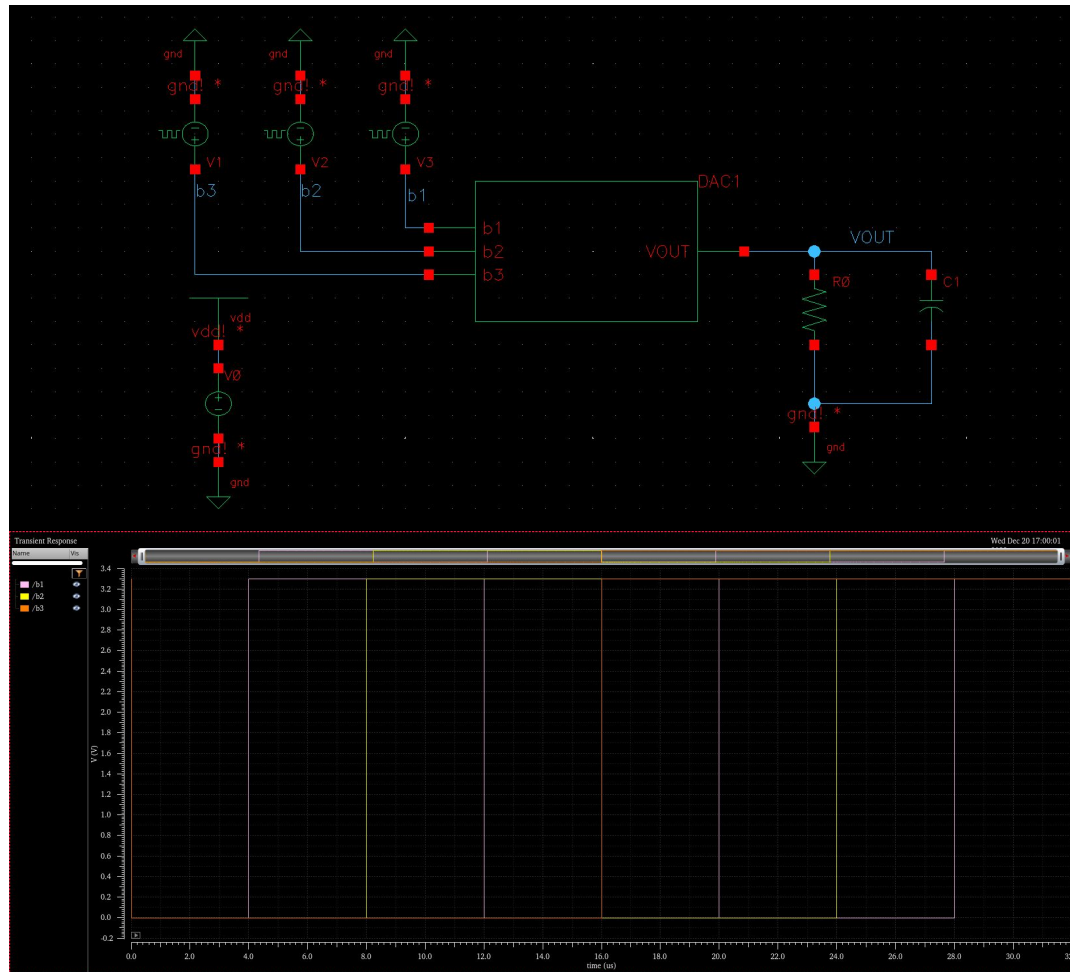

4.1 - DAC Design

Simulation

 


- ❖ Two lower bits cannot be reached due to limited ICMR
- ❖ Behaviour as expected with slew rate of 1 V/us



4.2 - DAC Design

Layout

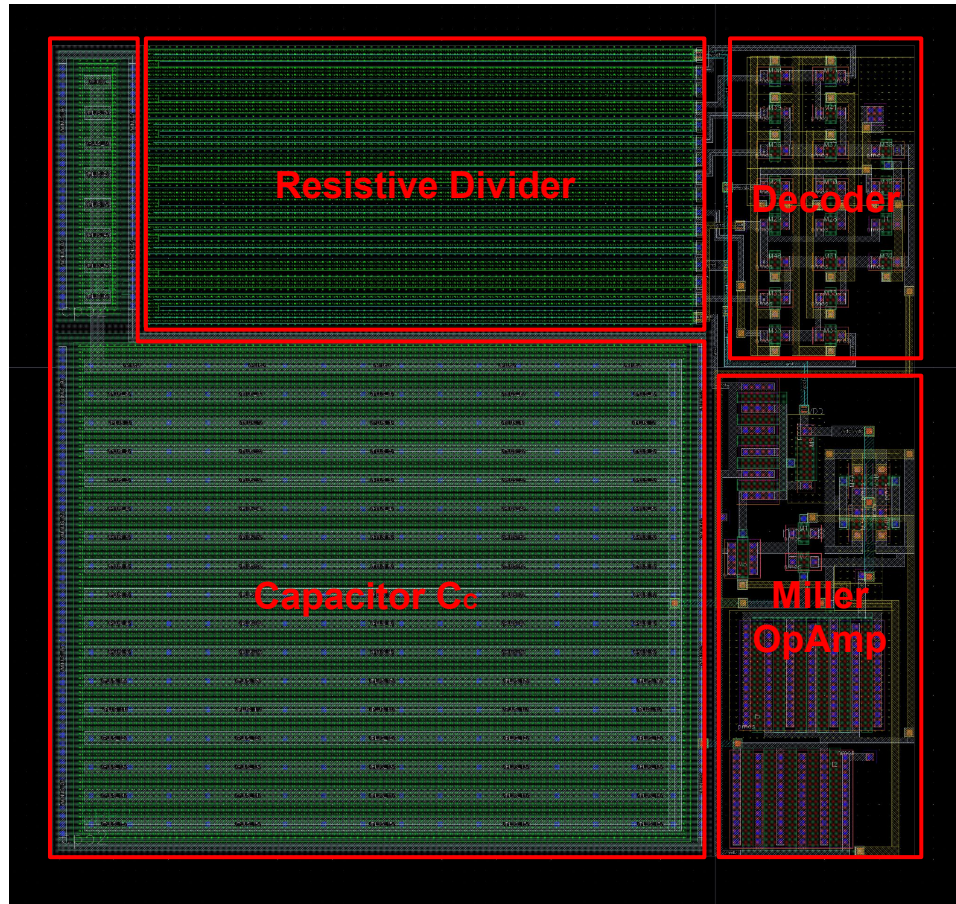

Run: "DAC3bit_LVS" (on iseserver... X)

Run: "DAC3bit_LVS" from /home/tl23_krieger/AssuraLVS

Schematic and Layout Match.
Do you want to view the results of this run?

Summary of LVS Issues

Extraction Information:

- 0 cells have 0 mal-formed device problems
- 0 cells have 0 label short problems
- 0 cells have 0 label open problems

Comparison Information:

- 0 cells have 0 Net mismatches
- 0 cells have 0 Device mismatches
- 0 cells have 0 Pin mismatches
- 0 cells have 0 Parameter mismatches





ELW Information:

Total DRC violations: 0




4.2 - DAC Design

Layout - Analog Extracted

 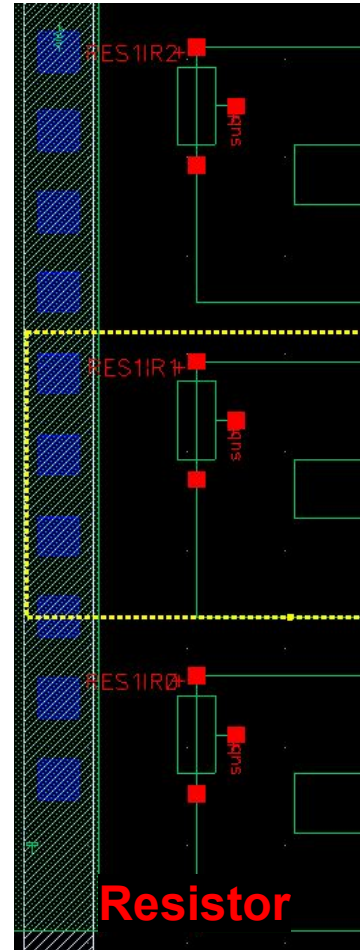 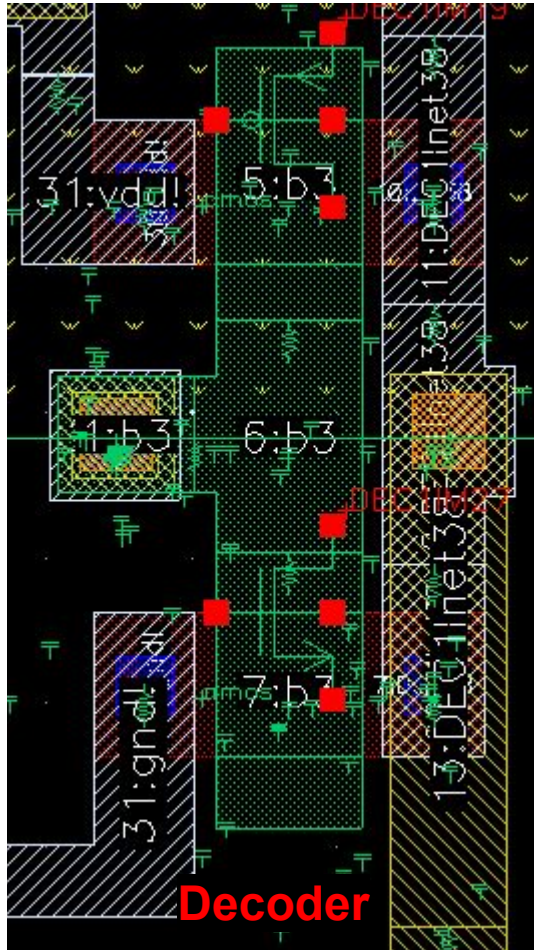


4.2 - DAC Design

Simulation - Layout vs. Schematic

 

 4.2 - DAC Design

Simulation - Monte Carlo Analysis (Layout)



- ❖ Maximum deviation of voltage level: 68 mV
- ❖ Optimization potential
 - Resistors
 - Transistors
 - Capacitors



4.3 - DAC Design

Final Specs

- ❖ **Area:** $78.825 \text{ um} \times 74.225 \text{ um} = 0.00585 \text{ mm}^2$
- ❖ **Static Power Consumption:** $P = 3.3 \text{ V} \times 167.05 \text{ uA} = 0.55 \text{ mW}$
- ❖ **Maximum Sampling Rate:** 378.63 kHz



5 - Conclusion

❖ Overview:

- Introduction to a state-of-the-art tool for semiconductor chip fabrication
- Design of an Operational Amplifier based on a specific design plan
- Design and construction of a Digital-to-Analog Converter
- Function simulation and verification
- Layout implementation in 0.35 μm technology
- Application of matched component techniques
- Layout validation through simulation and Monte Carlo simulations



5 - Conclusion

- ❖ Improvements:
 - Selection of a more sophisticated OpAmp layout for improved lower voltage representation
 - Mitigation of manufacturing variations impact on resistance divider voltage levels
 - Enhancement of bias circuit robustness



5 - Conclusion

Thank You for your attention!

Questions?



References

- ❖ Tesys Script
- ❖ Electronics 1/2 Script
- ❖ CMOS analog circuit design by Philip E. Allen and Douglas R. Holberg
- ❖ “Analog integrated circuit design” by Johns David and Martin Kenneth W.

