

Design of a Dedicated Miller-opAmp

Kuan Shang

Sommersemester , 2008

Prof. Dr.-Ing. Andreas König



Overview

1.Design Plan

--Calculation according to Allen/D. Holberg, *CMOS Analog Circuit Design*,
Oxford Uni.Press, 1987

2.Simulation Circuits

3.Layout and Post Layout Simulation

4.Results

5.Conculsion

Design Goals

Specifications

•0.35 μ m Austria Microsystems technology

•Design a 2 stage opAmp adjusted for high speed readout application

	Targeted values
Open Loop Gain	> 70 dB
Gain Bandwidth	10 MHz
Phase Margin	> 65°
Settling Time	< 1 μ s
Slew Rate	> 30 V/ μ s
Offset Voltage	< 10 μ V
Input CMR	+/- 1 V
Output Swing	+/- 1 V
CMRR	> 80 dB
Power Dissipation	minimum
Load Capacitance	5p F
Load Resistance	100k Ω

Design Plan

Compensation capacitance:

$$C_c > 0.22 C_L \Rightarrow C_c > 1.1 \text{ pF}$$

tail current:

$$I_5 = S_R \cdot C_c \Rightarrow I_5 = 33 \text{ uA}$$

Transistor M3, M4:

$$S_3 = \frac{W_3}{L_3} = \frac{I_5}{K'_3 [V_{DD} - V_{in}(\text{max}) - |V_{T03}|(\text{max}) + V_{T1}(\text{min})]^2} \geq 1$$

$$\Rightarrow S_3 = S_4 = 6$$

Transistors M1, M2:

$$g_{m1} = GB \cdot C_c \Rightarrow S_1 = S_2 = \frac{g_{m2}^2}{K_2' I_5}$$


$$\Rightarrow S_1 = S_2 = 1$$

Transistor M5:

$$V_{DSS}(\text{sat}) = V_{in}(\text{min}) - V_{SS} - \sqrt{\frac{I_5}{\beta_1}} - V_{T1}(\text{max}) \geq 100 \text{ mV}$$

$$S_5 = \frac{2I_5}{K_5' [V_{DSS}(\text{sat})]^2}$$

$$\Rightarrow S_5 = 2$$

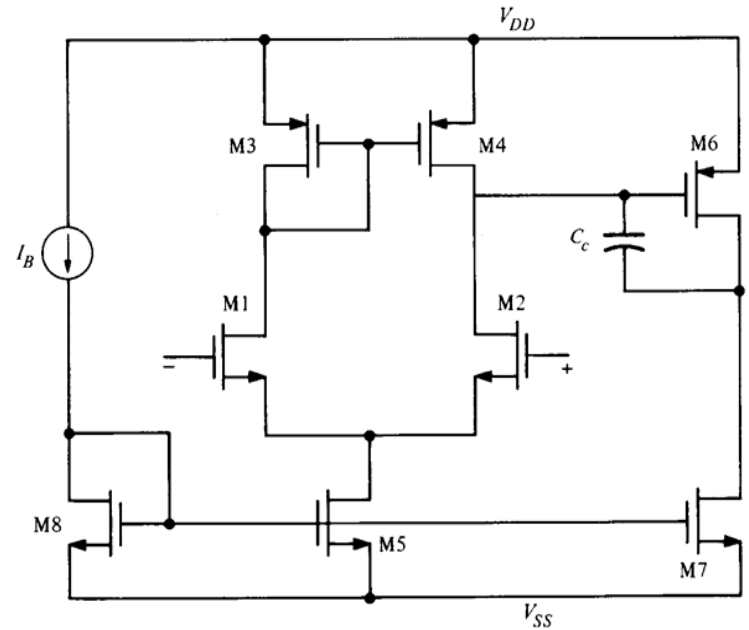

Design Plan

Transistor M6:

$$S_6 = \frac{g_{m6}}{K_6' V_{DS6}(sat)}$$

$$\Rightarrow S_6 = 40$$

Transistor M7:

$$I_6 = \frac{g_{m6}^2}{2K_6' V_{DS6}(sat)}$$


$$S_7 = \frac{I_6}{I_5} S_5$$

$$\Rightarrow S_7 = 7$$


gain and power dissipation:

$$A_V = \frac{2(g_{m2})(g_{m6})}{I_5(\lambda_2 + \lambda_3)I_6(\lambda_6 + \lambda_7)} \Rightarrow A_V = 67.1 \text{ dB}$$
 
$$P_{diss} = (I_6 + I_5)(V_{DD} - V_{SS}) \Rightarrow P_{diss} = 1.7 \text{ mW}$$



Design Plan

 

$C_c=500\text{fF}$, $SR=164.2\text{ V}/\mu\text{s}$, $PM=40^\circ$

$C_c=1.5\text{pF}$, $SR=60.37\text{ V}/\mu\text{s}$, $PM=65^\circ$

$C_c=500\text{fF}$,Open Loop Gain=72.4dB

$C_c=1.5\text{pF}$,Open Loop Gain=72.4dB

Decrease C_c will increase the SR, but also decrease PM. C_c doesn't change the open loop gain.

$S_s=16\mu$ SR=60.37 V/ μs , PM=54.63 $^\circ$


$S_s=32\mu$ SR=121.27 V/ μs , PM=85 $^\circ$

$S_s=16\mu$ Open Loop Gain=72.4dB

$S_s=32\mu$ Open Loop Gain=27.28dB

Increase S_s will increase the SR and PM, but decrease the open loop gain a lot

Design Plan

 

$S_1=4\mu$, $SR=60.37V/\mu s$, Open Loop Gain =72.44dB
 $PM=65^\circ$

$S_1=8\mu$, $SR=60.59 V/\mu s$, Open Loop Gain =75.52dB
 $PM=56.6^\circ$

Increase S_1, S_2 will increase Open Loop Gain but decrease PM . S_3, S_4 doesn't change the Slew Rate much

$S_3=12.5\mu$, Open Loop Gain=72.44 dB , $PM=65^\circ$


$S_3=25\mu$, Open Loop Gain=33.41 dB , $PM=85^\circ$

$S_3=12.5\mu$, $SR=60.37V/\mu s$

$S_3=25\mu$, $SR=60.68$

Increase S_3, S_4 will decrease Open Loop Gain, but increase the PM . S_3, S_4 doesn't change the Slew Rate much

Design Plan

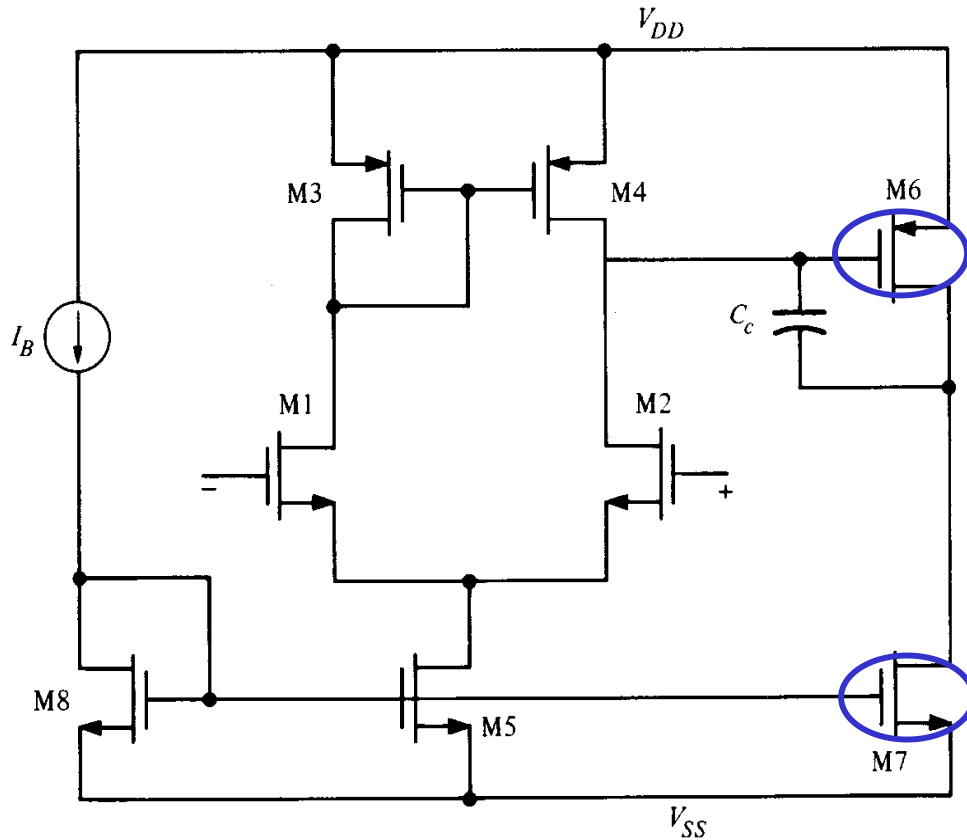

$S_6=75\mu$, $SR=59.6 \text{ V}/\mu\text{s}$, Open Loop Gain=30.4dB
 $S_6=150\mu$, $SR=60.4 \text{ V}/\mu\text{s}$, Open Loop Gain=72.4dB

$S_6=75\mu$, $PM=85.3^\circ$
 $S_6=150\mu$, $PM=65^\circ$


$S_7=50\mu$ Open Loop Gain=32.4dB, $PM=82^\circ$
 $S_7=95.2\mu$ Open Loop Gain=72.4dB, $PM=65^\circ$

$S_6=50\mu$, $SR=60.3 \text{ V}/\mu\text{s}$
 $S_6=95.2\mu$, $SR=60.4 \text{ V}/\mu\text{s}$

Increase S_6, S_7 will increase Open Loop Gain, decrease the PM, they will not change SR much

OpAmp Simulation Circuit

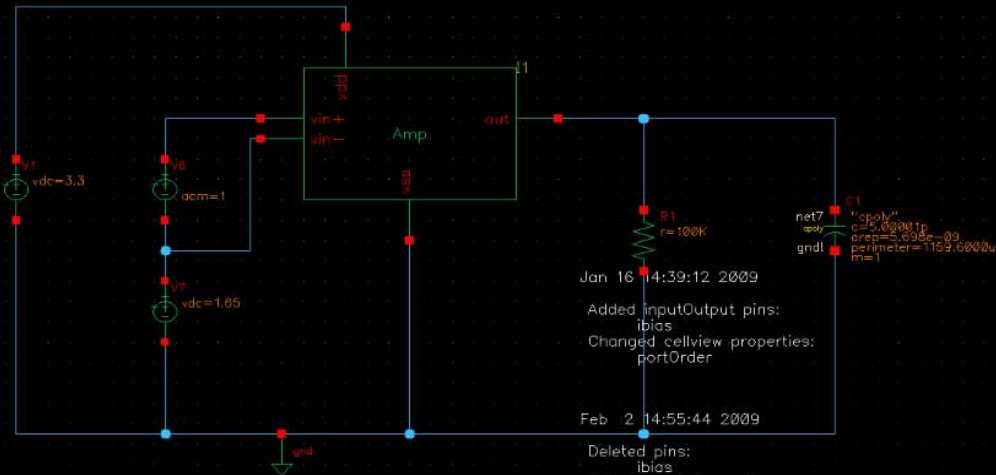OpAmp Open loop Gain ,Gain Bandwidth ,Phase Margin Simulation Circuit



Jan 16 4:39:12 2009

Added inputOutput pins:
ibias
Changed cellview properties:
portOrder

Feb 2 14:55:44 2009

Deleted pins:
ibias
Added inputOutput pins:
bias_v bias_c
Changed cellview properties:
portOrder

Feb 4 11:14:52 2009


Deleted pins:
bias_c bias_v
Added inputOutput pins:
bias
Changed cellview properties:
portOrder

Feb 8 20:25:57 2009

Deleted pins:
bias


OpAmp Simulation Circuit

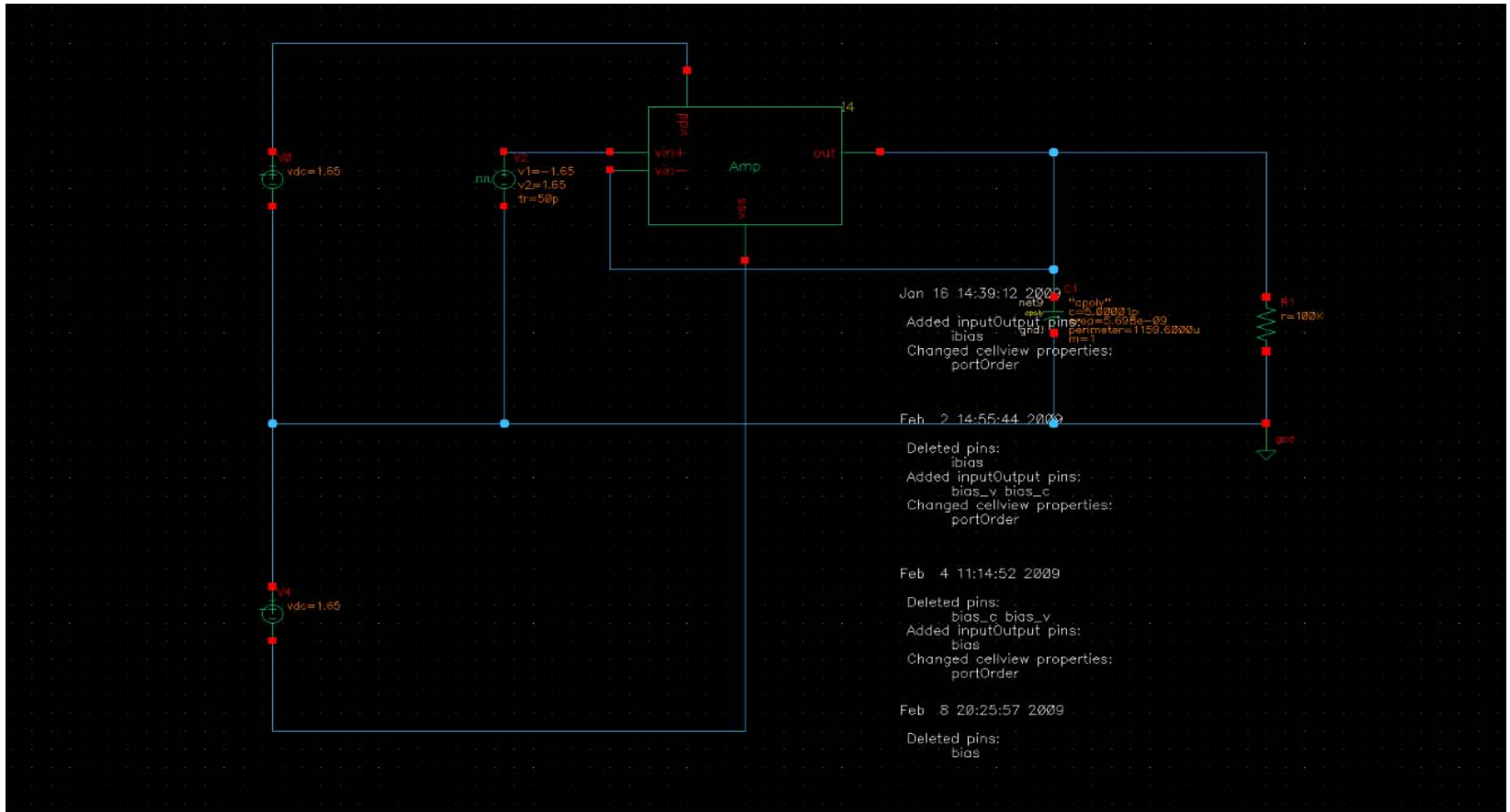OpAmp Slew Rate, Settling Time Simulation Circuit




OpAmp Simulation Circuit

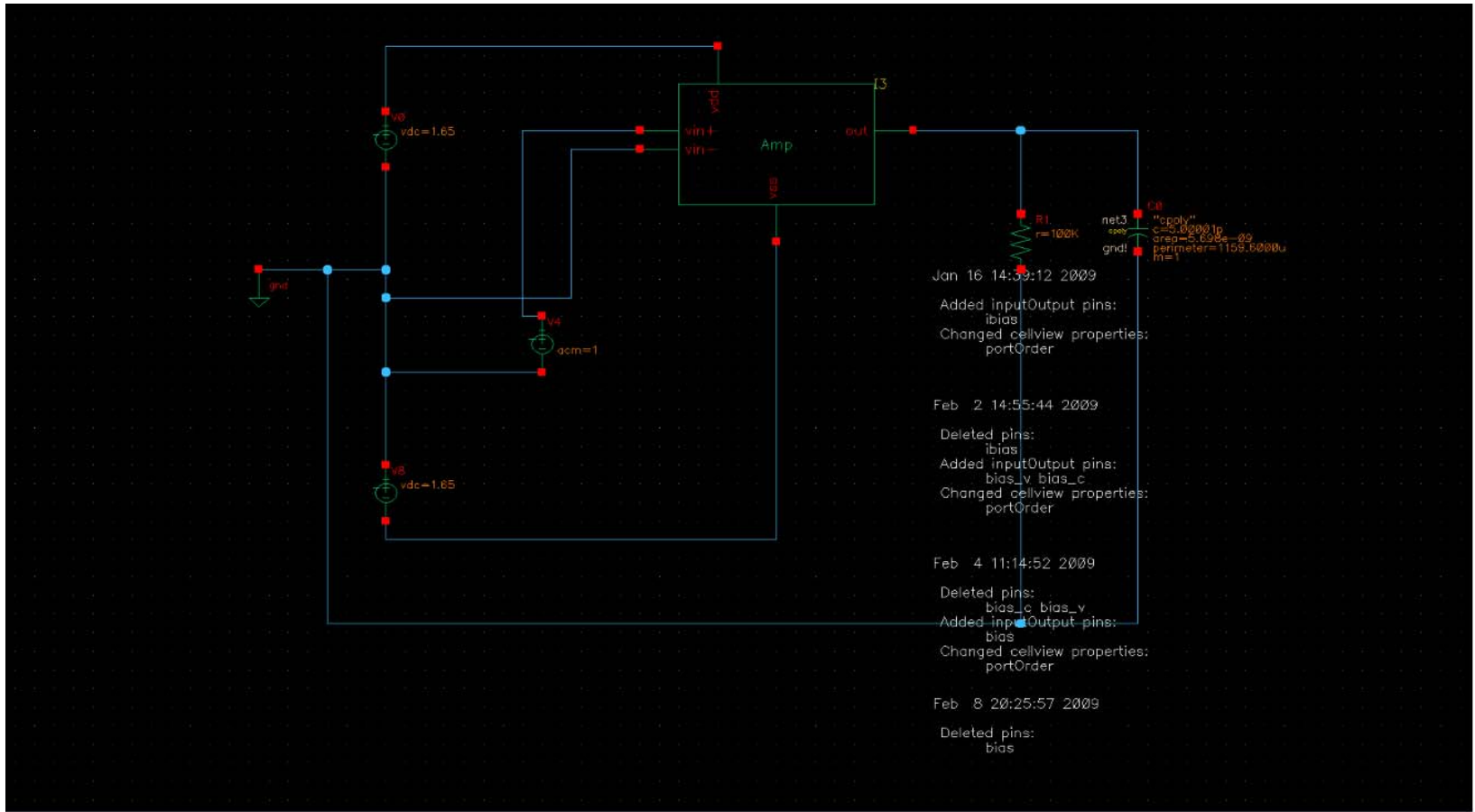OpAmp Differential Mode Gain Simulation Circuit




OpAmp Simulation Circuit

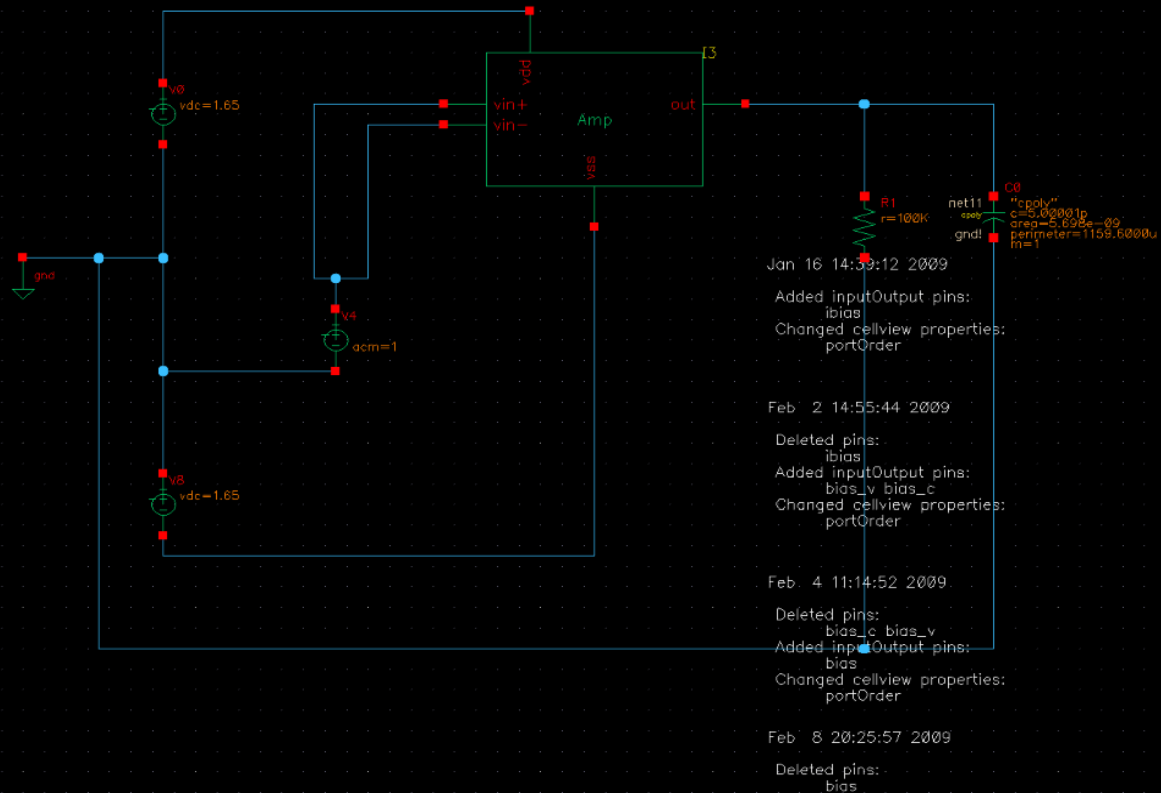OpAmp Common Mode Gain Simulation Circuit



OpAmp Simulation Circuit

OpAmp Input CMR Simulation Circuit

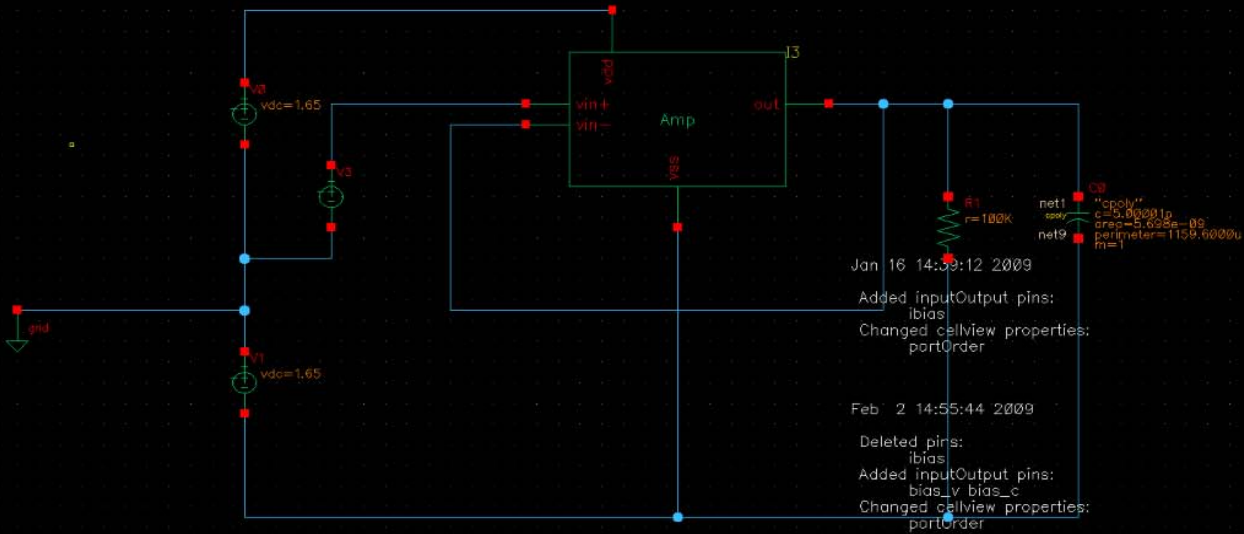

Jan 16 14:09:12 2009

Added inputOutput pins:
ibias
Changed cellview properties:
portOrder

Feb 2 14:55:44 2009

Deleted pins:
ibias
Added inputOutput pins:
bias_v bias_c
Changed cellview properties:
portOrder

Feb 4 11:14:52 2009


Deleted pins:
bias_c bias_v
Added inputOutput pins:
bias
Changed cellview properties:
portOrder

Feb 8 20:25:57 2009

Deleted pins:
bias


OpAmp Simulation Circuit

OpAmp Output Swing Simulation Circuit

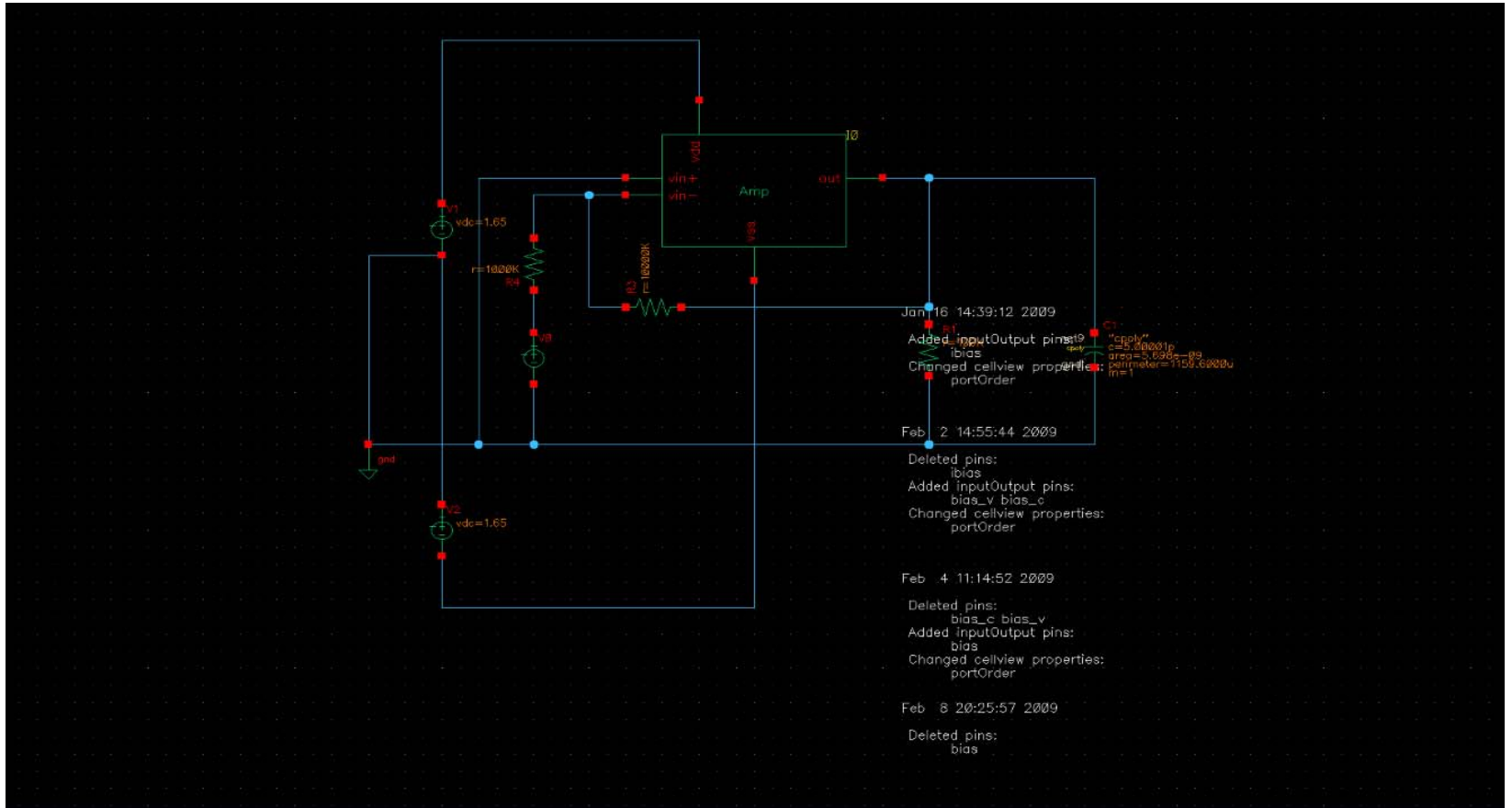


OpAmp Simulation Circuit

OpAmp Offset Voltage Simulation Circuit

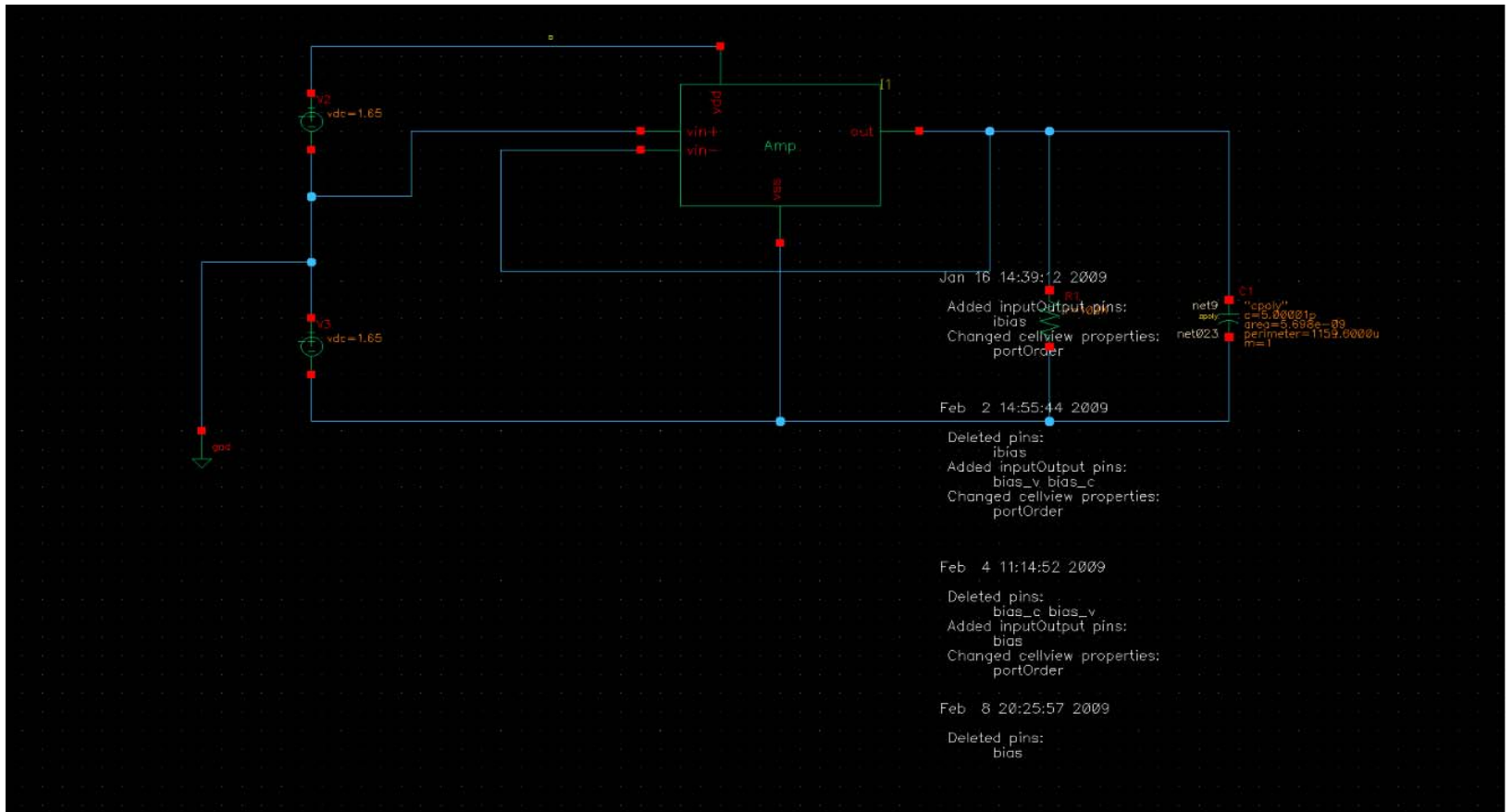


OpAmp Simulation Circuit

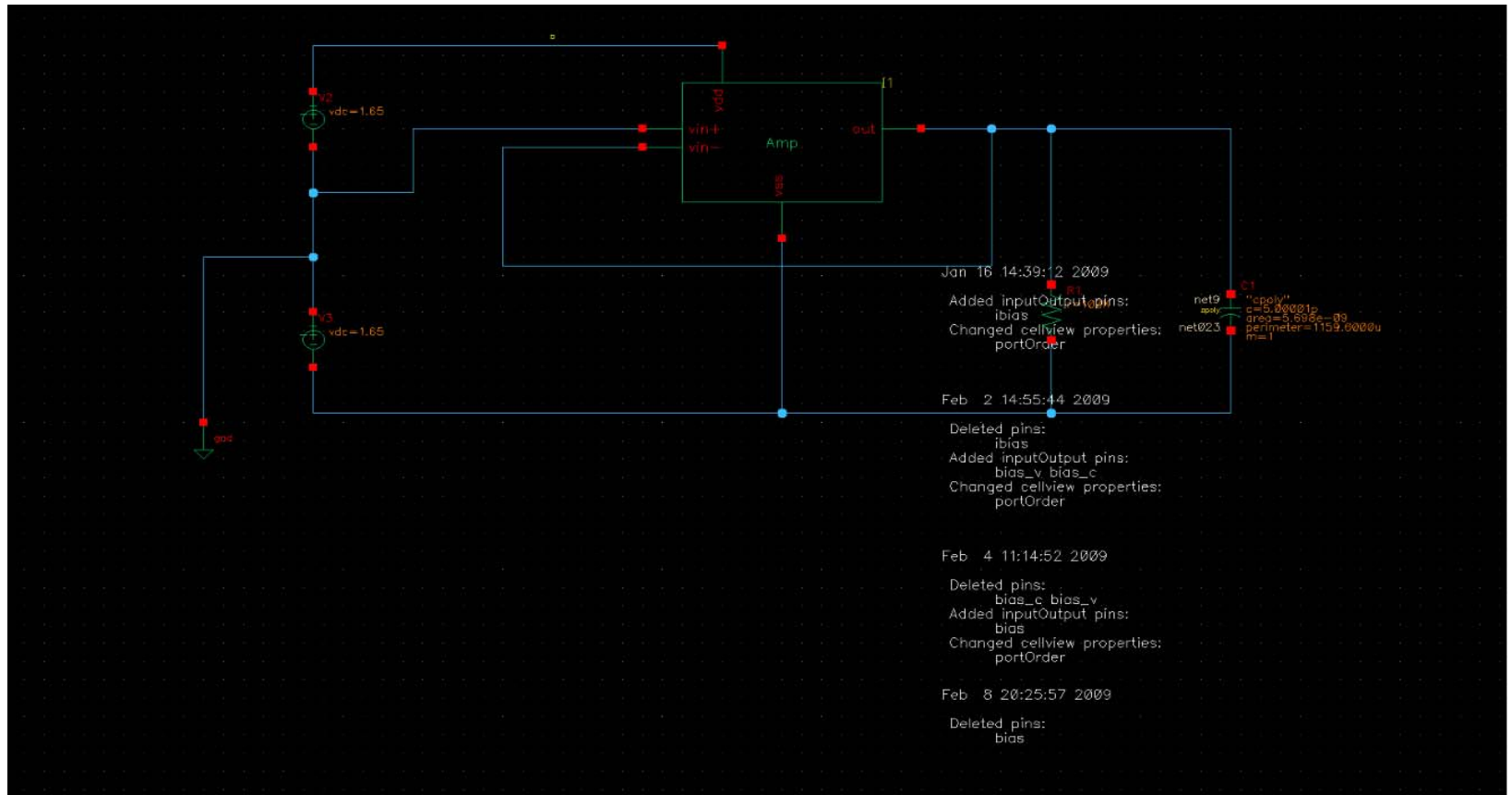
OpAmp Power Dissipation Simulation Circuit




OpAmp Schematic Design

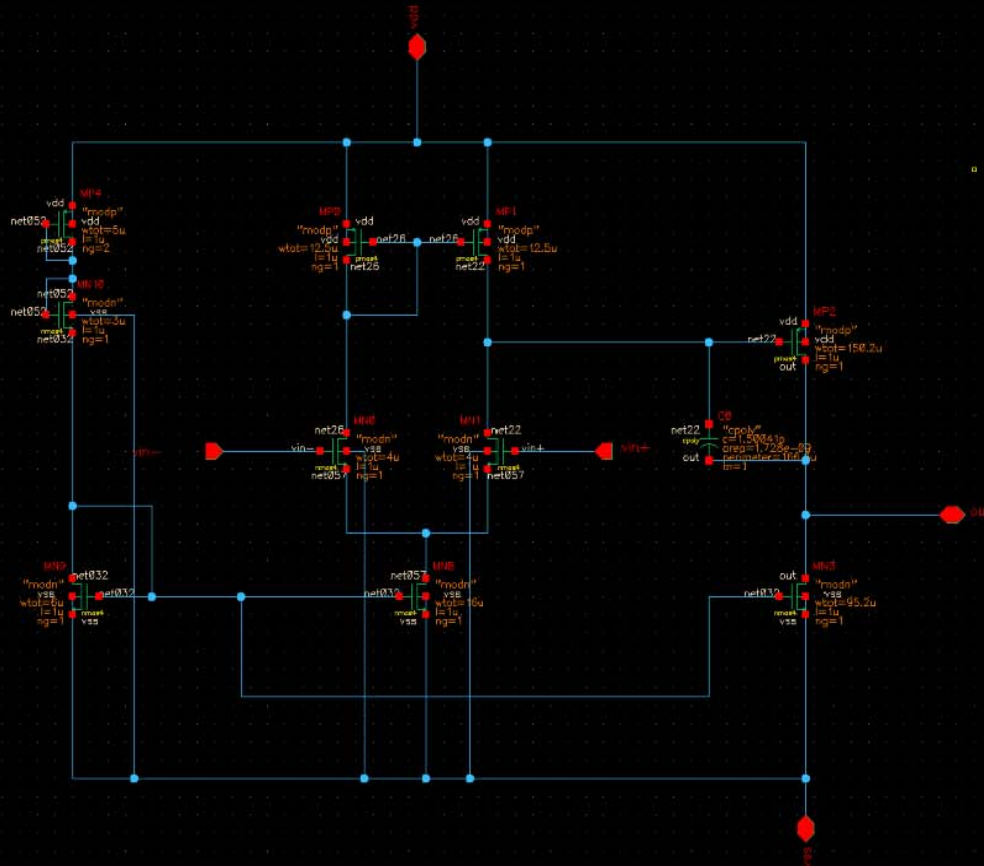


OpAmp Layout Design

 

OpAmp Layout Design

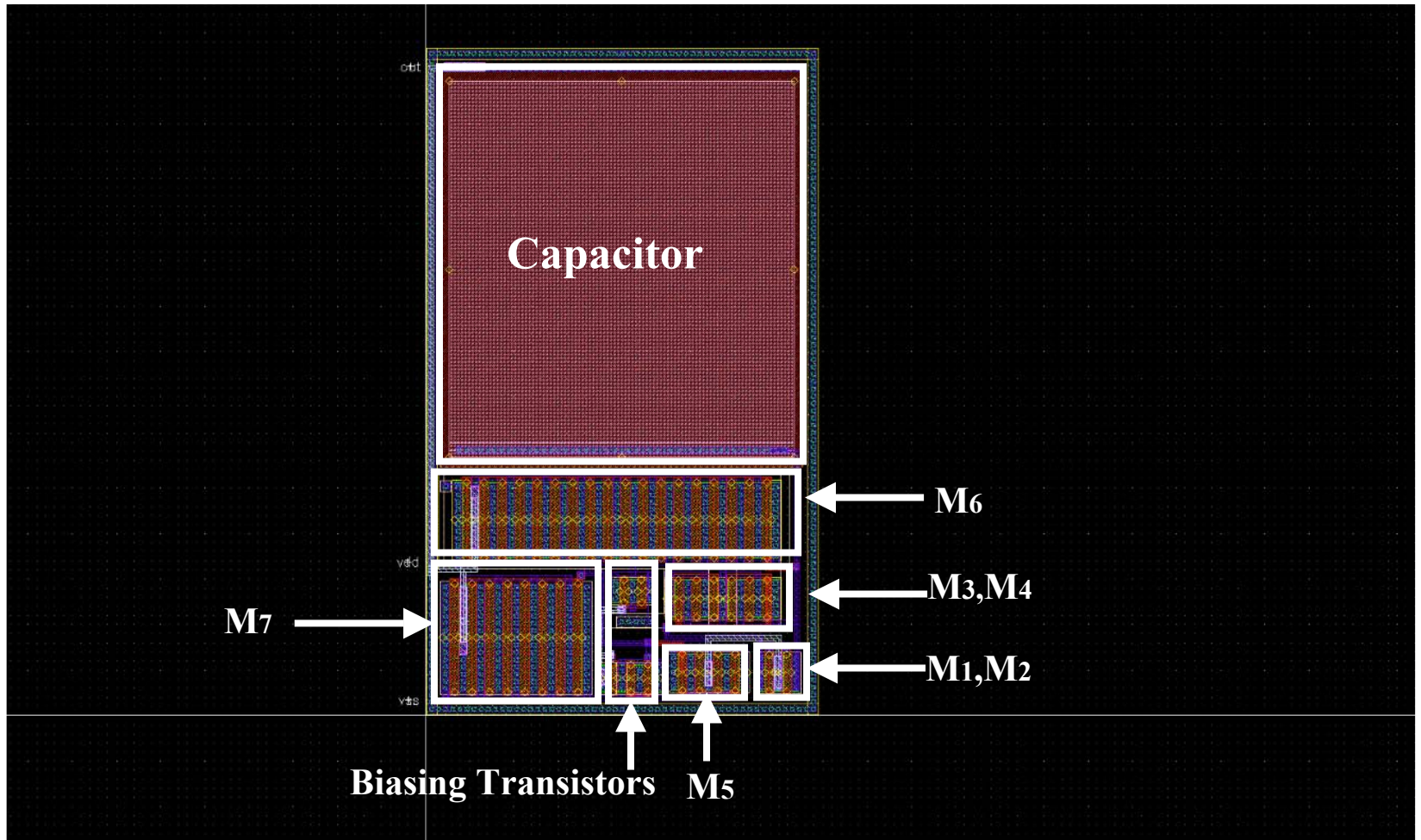

OpAmp Analog- Extracted View

 

OpAmp LVS Check

```
File /export/users/sens7/LVS/si.log Help 127
Warning: Unknown device "rpolyl" on a permuteDevice command.
Warning: Unknown device "lst3" on a permuteDevice command.
Warning: Unknown device "vert15" on a permuteDevice command.
Warning: Unknown device "vert10" on a permuteDevice command.
Warning: Unknown device "vert5" on a permuteDevice command.
Warning: Unknown device "pmosm4" on a permuteDevice command.
Warning: Unknown device "rmosm4" on a permuteDevice command.
Warning: Unknown device "rmosm4" on a permuteDevice command.
Warning: Unknown device "rmosh5" on a permuteDevice command.
Warning: Unknown device "rmosh4" on a permuteDevice command.
Warning: Unknown device "ng" on a permuteDevice command.
Warning: Unknown device "cvar" on a permuteDevice command.
Warning: Unknown device "csandvt" on a permuteDevice command.
Warning: Unknown device "cd2sm24" on a permuteDevice command.
Warning: Unknown device "pd" on a permuteDevice command.
Warning: Unknown device "nvd" on a permuteDevice command.
Warning: Unknown device "nd" on a permuteDevice command.

The net-lists match.

          layout schematic
          instances
un-matched      0      0
required       0      0
size errors     0      0
pruned         0      0
active        44     11
total         44     11


          nets
un-matched      0      0
merged         0      0
pruned         0      0
active        10     10
total         10     10

          terminals
un-matched      0      0
matched but
different type  0      0
total          5      5
End comparison:   Feb  9 20:42:17 2009

Comparison program completed successfully.
```


OpAmp Post Layout Simulation

Bode plot

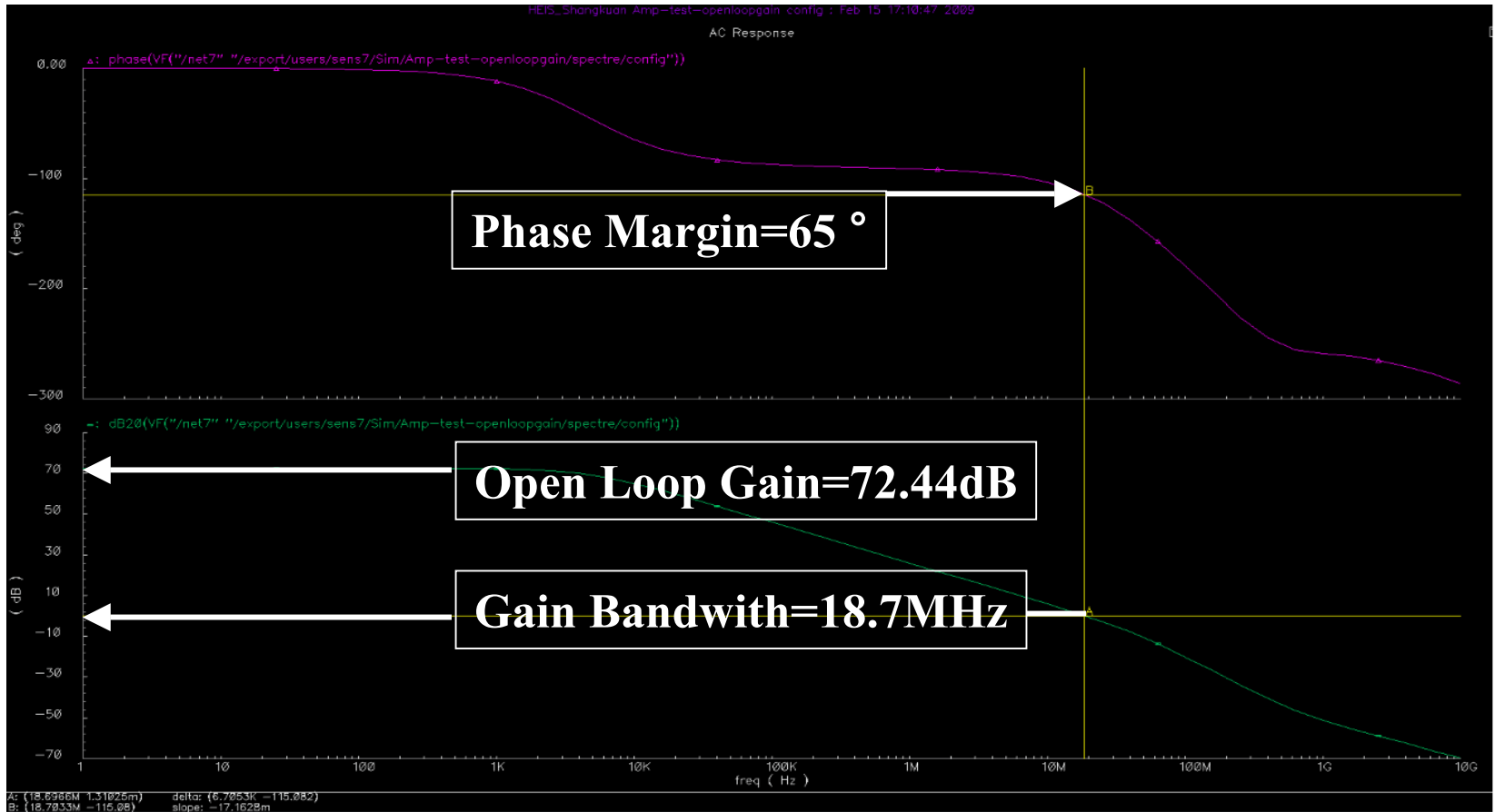


OpAmp Post Layout Simulation

Slew Rate

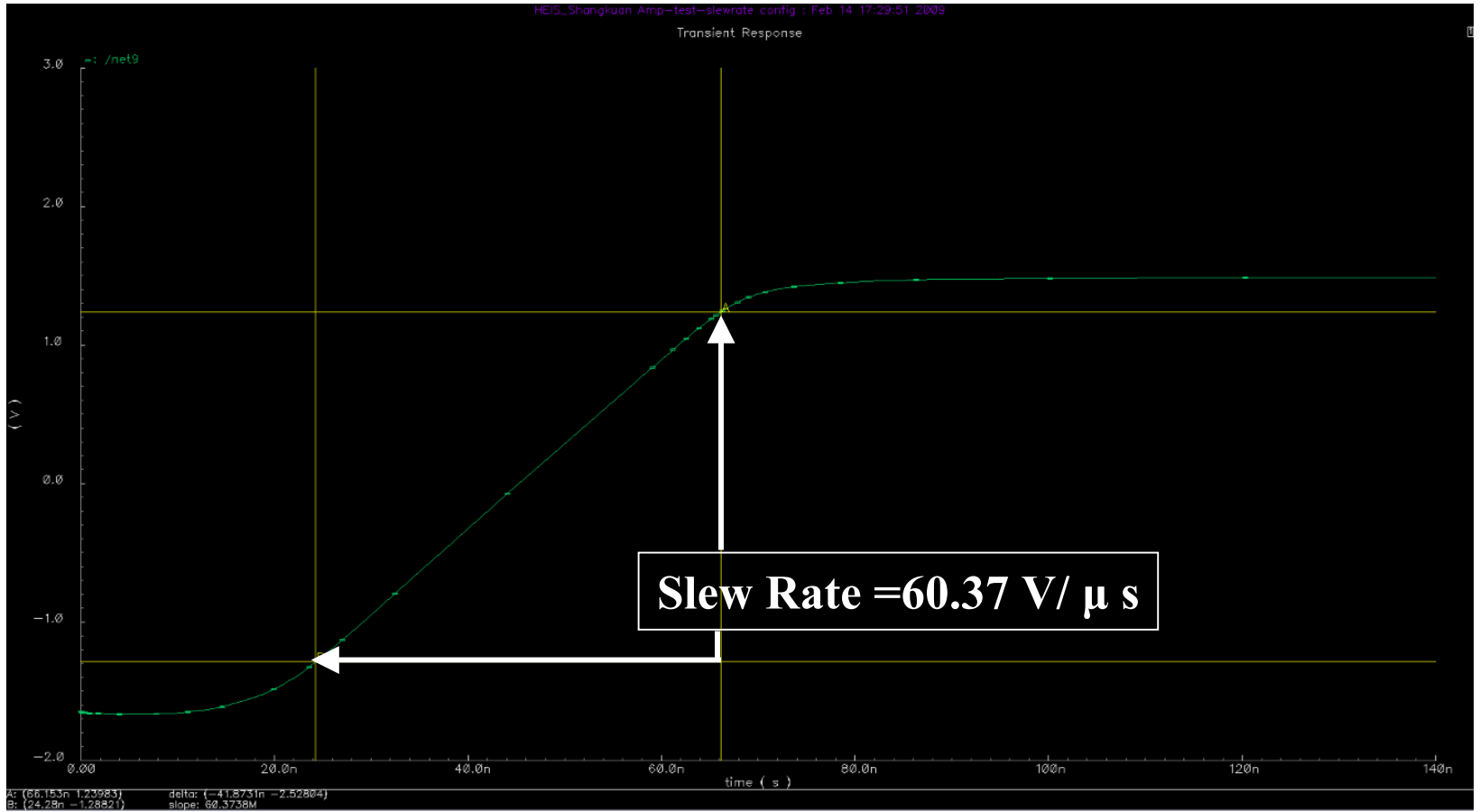


OpAmp Post Layout Simulation

Settling Time

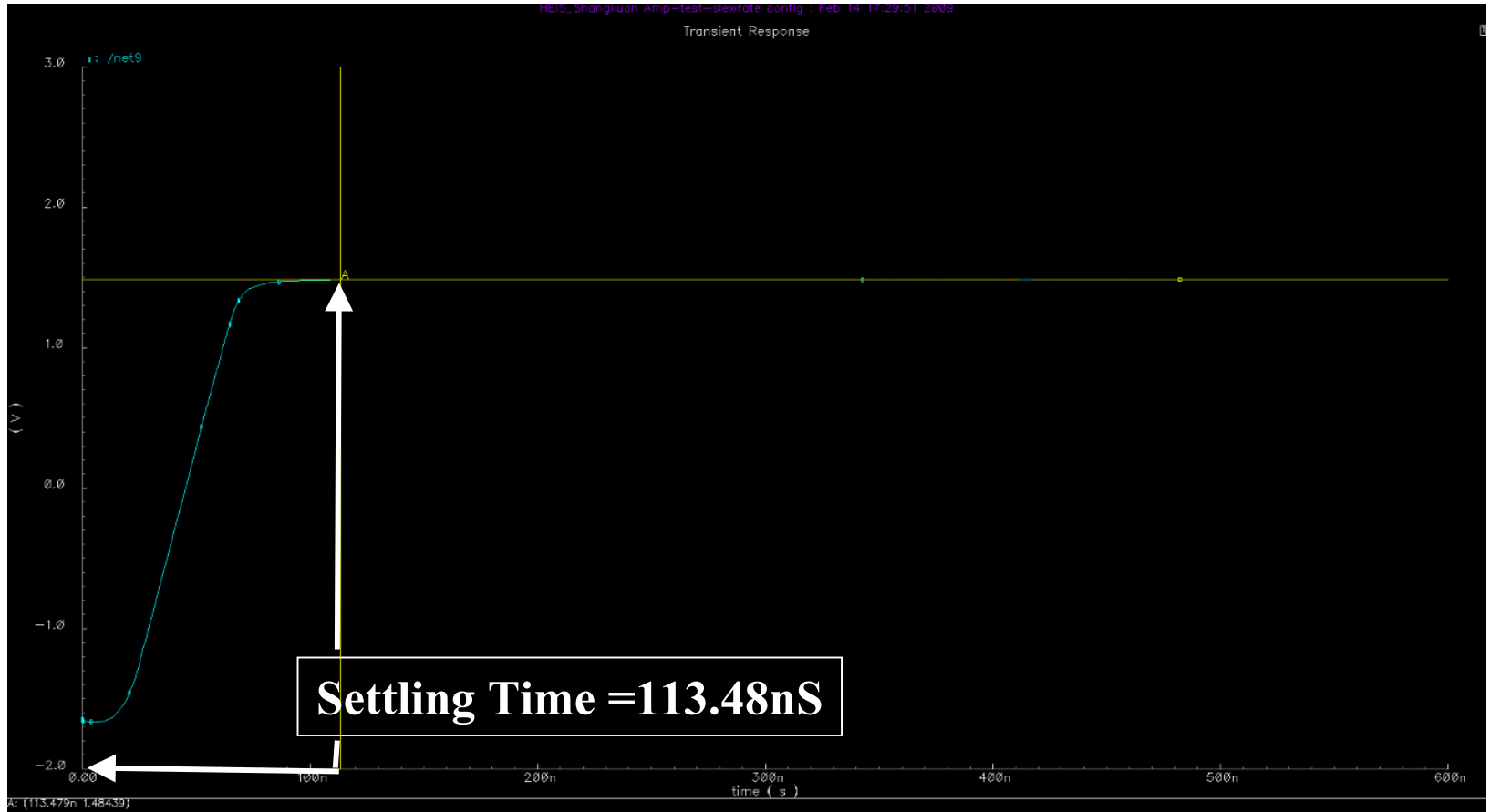


OpAmp Post Layout Simulation

Offset Voltage

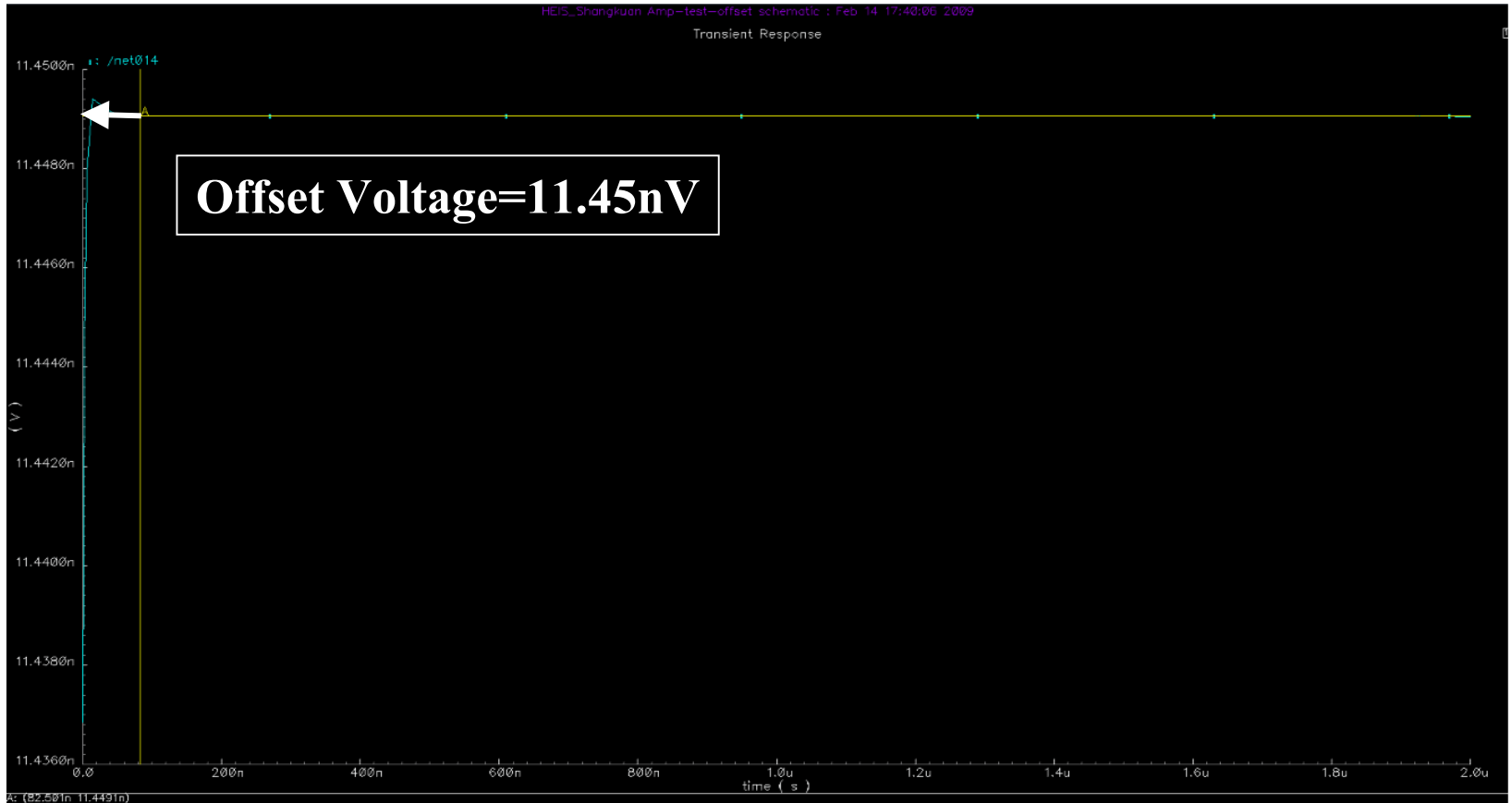



OpAmp Post Layout Simulation

Input CMR

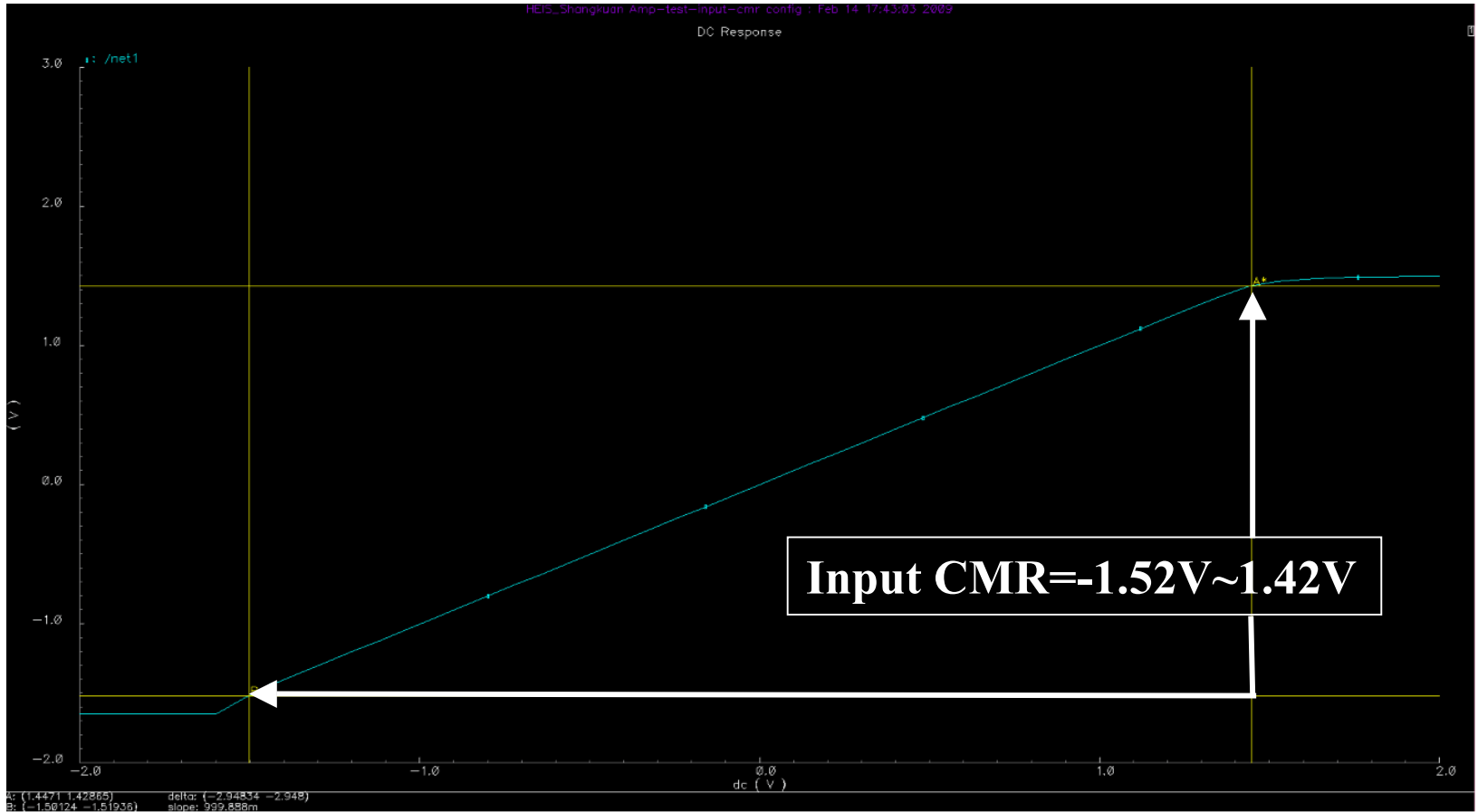

OpAmp Post Layout Simulation


CMRR

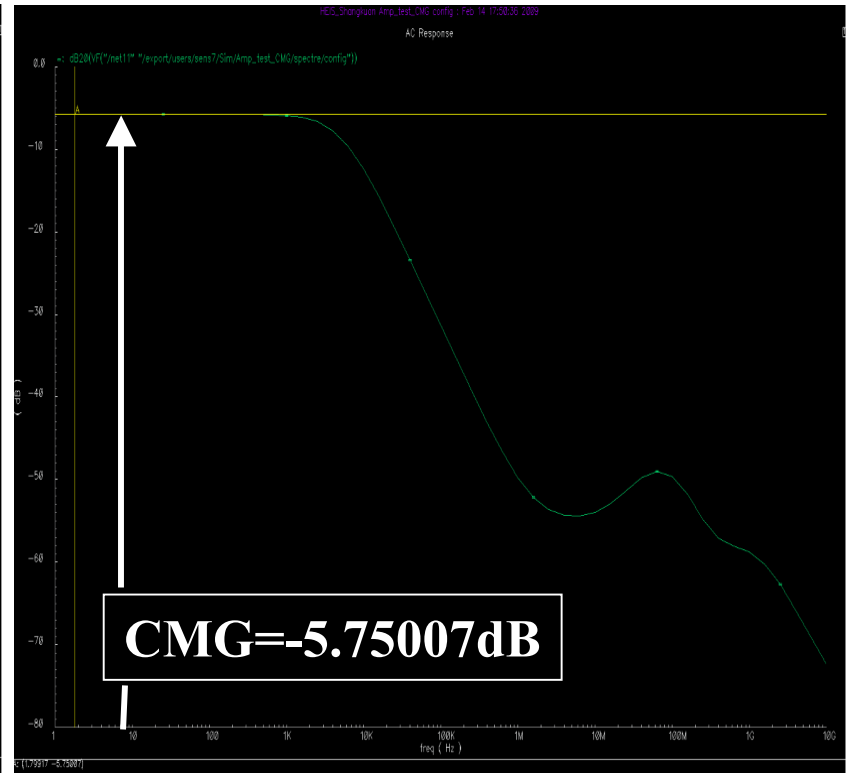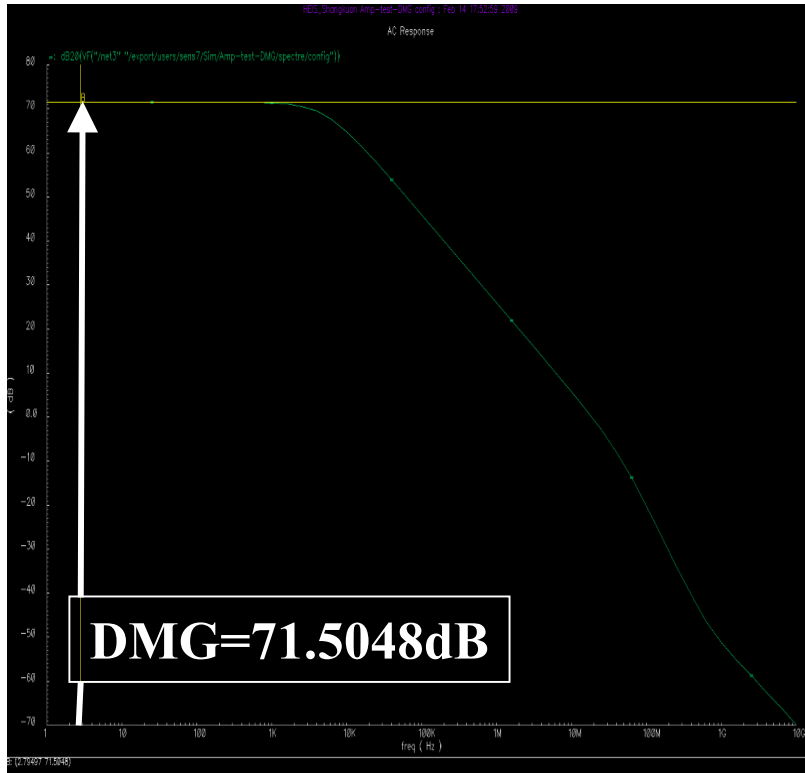

- differential mode gain
 - common mode gain
- $CMRR = (\text{differential-mode gain}) - (\text{common-mode gain})$


OpAmp Simulation

Output Swing

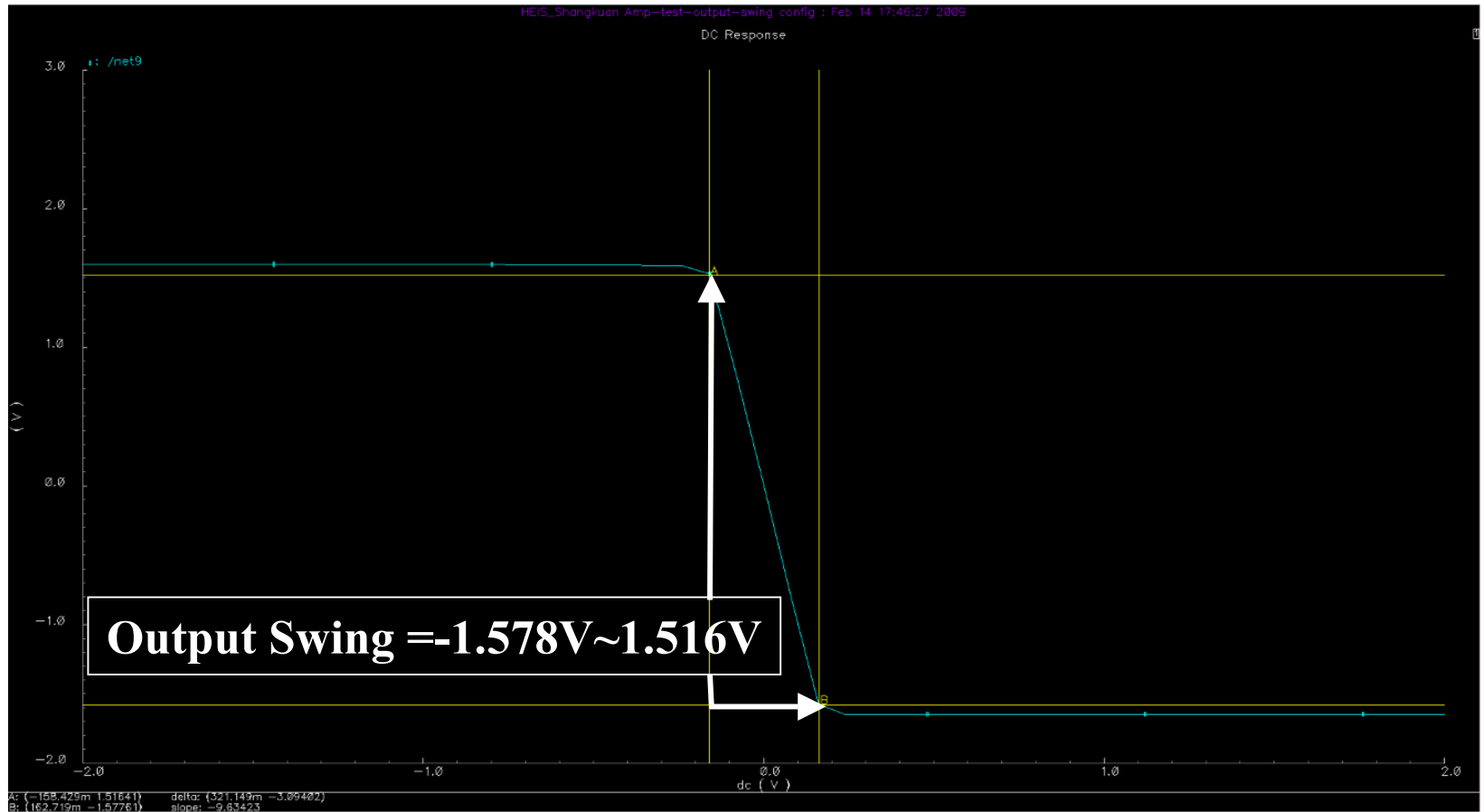

OpAmp Simulation

Power Dissipation

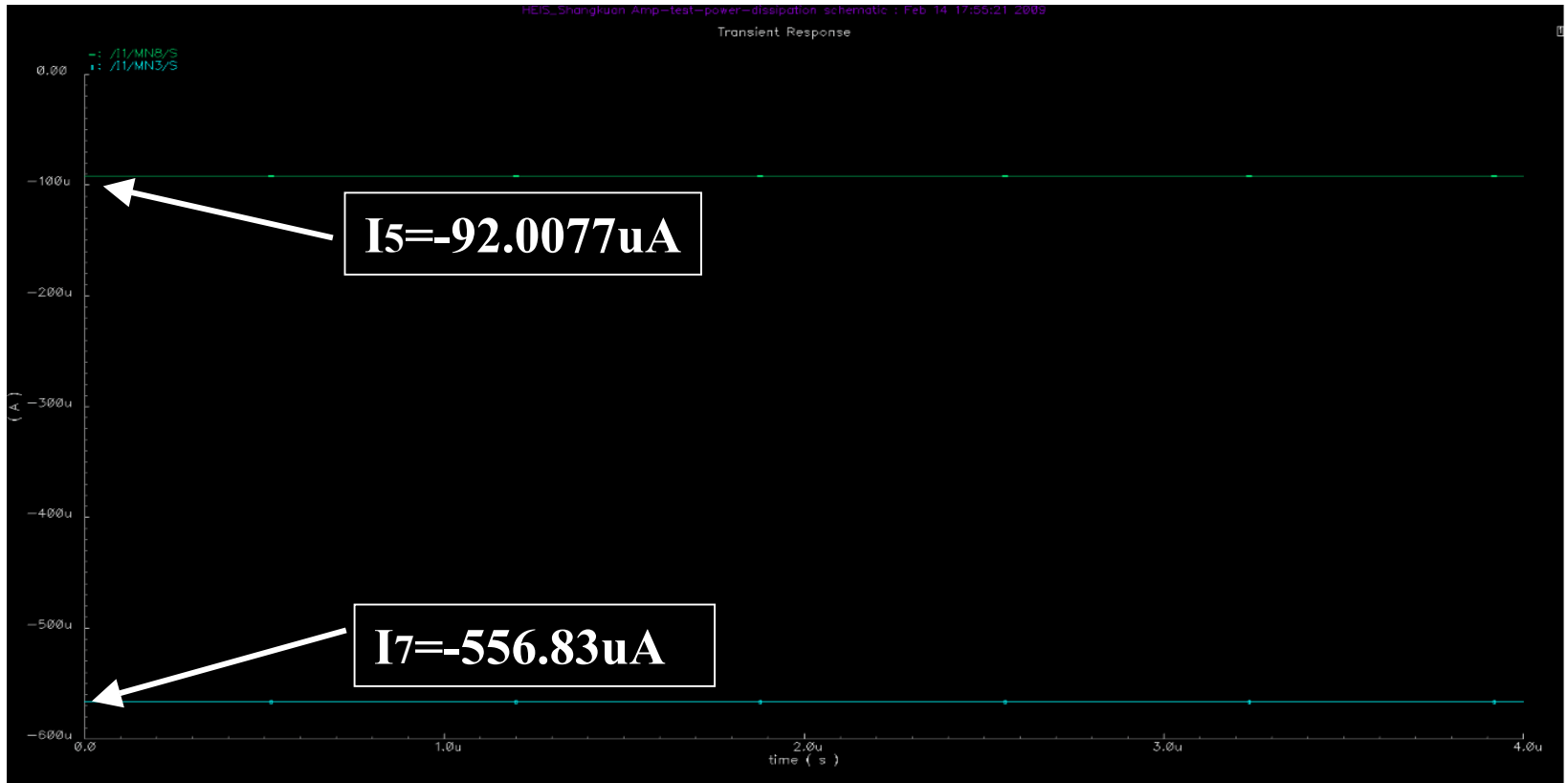

$$P_{diss} = 3.3V \cdot I_{diss}$$

Results

	Targeted values	Design Plan	Schematic	Analog-extracted
Open Loop Gain	> 70 dB	67.84dB	72.6 dB	72.44 dB
Gain Bandwidth	10 MHz	4.35MHz	18.97MHz	18.7 MHz
Phase Margin	> 65°	64 °	65.5 °	65 °
Settling Time	< 1 μ s	560.1ns	117.7 ns	113.5 ns
Slew Rate	> 30 V/ μ s	10V/ μ s	60.85V/ μ s	60.37V/ μ s
Offset Voltage	< 10 μV	98.21nV	11. 43nV	11.45nV
Input CMR	+/- 1 V	-1.642 V-1.52V	-1.54V~1.42V	-1.51V~1.43V
Output Swing	+/- 1 V	-1.538V~1.555V	-1.58V~1.52V	-1.58V~1.52V
CMRR	> 80 dB	88.03dB	77.1dB	77.3 dB
Power Dissipation	minimum	1.72mW	2.13mW	2.14mW

	s1	s2	s3	s4	s5	s6	s7	Cc
Calculated size (W/L)	1	1	6	6	2	40	7	1.1pF
Analog_extracted size (W/L)	4	4	12.5	12.5	16	150.2	95.2	1.5pF

Conclusion

- This design mainly focus on the high speed application ,so the slew rate and settling time are critical. other specifications eg:Input CMR, Output Swing sequentially get a desirable value when the circuit is finally adjusted and optimaized
- In the design the power dissipation is relatively high ,while I use large transistors ,eg:M5,M7 in order to get desiable specifications with high speed application.
- In the design plan I try to get phase margin around 70° ,but the trade off between slew rate and phase margin mainly depends on the compensation capacitance. Finally the Phase Margin is 65° ,and slew rate is $60.37\text{V}/\mu\text{s}$.



The End